

THE No 1 UK MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

# **EPE** EVERYDAY PRACTICAL ELECTRONICS

www.epemag.com



## **ColdAlert!**

**PIC-based hypothermia alarm**



**Win a  
PICkit 3 Debug  
Express Kit  
see Inside for  
details**



## **Swimming Pool Alarm**

- ★ **Very loud siren with adjustable alarm period**
- ★ **PIC-based system monitors wave height, avoiding false alarms**
- ★ **Weatherproof housing and safe plugpack power supply**



### **HOW TO SOLDER SURFACE-MOUNT DEVICES**

**'Afraid' of SMDs? Fear no more! Our comprehensive guide will soon have you soldering like never before**

**\$8.75US \$10.25CAN £3.95UK**  
**JULY 2010 PRINTED IN THE UK**





**0845 251 4363**

Catalogue Available

**velleman®****The UK's number 1 source of VELLEMAN® products.****Velleman Kits**

K1803	Universal Mono Pre-Amplifier Kit	4.34
K1823	1A Power Supply Kit	6.95
K2543	Electronic Transistor Ignition Kit	11.30
K2570	Universal 5 - 14VDC Power Supply Kit	9.42
K2572	Universal Stereo Pre-Amplifier Kit	7.95
K2573	Stereo Pre-Amplifier for MD Pick-Ups Kit	8.00
K2579	Universal Stop/Start Timer Kit	6.76
K2599	Windshield Wiper or Interval Timer Kit	10.90
K2601	Stroboscope Kit	13.14
K2604	Police Siren Kit	8.12
K2622	AM/FM Antenna Amplifier Kit	9.32
K2625	Digital Tachometer Kit	23.64
K2633	Relay Card Kit	14.28
K2634	Quad Triac Switch Card Kit	13.36
K2636	Speed Controller Kit	16.23
K2639	Liquid level Controller Kit	12.69
K2644	Frost Indicator Kit	8.31
K2649	Thermostat with LCD Kit	32.73
K2651	LCD Panel Meter Kit	19.31
K2655	Electronic Watchdog Kit	22.13
K2661	Dual Input Amplifier Module Kit	16.55
K3400	Dual Electronic Dice Kit	10.91
K3500	Multifunction car Courtesy Light Kit	10.01
K3502	Parking Radar Kit	27.35
K3504	Car Alarm Kit	13.41
K3505	Car Light Warning Alarm Kit	9.18
K4001	7W Mono Amplifier Kit	6.90
K4003	2 x 30W Audio Power Amplifier Kit	16.96
K4004B	200W Mono/Stereo Amplifier Kit	46.25
K4005B	400W Mono/Stereo Amplifier Kit	62.85
K4006	Power Supply for K4004B and K4005B Kit	10.45
K4010	300W Mono Mosfet Amplifier Kit	138.19
K4040	Stereo Valve Amplifier/Chrome Kit	765.92
K4040B	Stereo Valve Amplifier/Black Kit	809.94
K4102	Guitar Preamp with Headphone Output	19.85
K4301	Pink Noise Generator Kit	8.31
K4304	Mono VU Meter 10 LEDs Kit	9.95
K4305	Stereo VU Meter 2 x 10 LEDs Kit	15.95
K4306	Precision Stereo VU Meter 2 x 15 LEDs Kit	24.95
K4307	Audio Power Meter Kit	15.35
K4401	Sound Generator Kit	15.95
K4600	Video and RGB Converter/Processor Kit	95.61
K4601	Audio/Video TV Modulator Kit	25.89
K4700	2-Channel Loudspeaker Protection Kit	13.70
K4701	Loudspeaker DC-Protection Kit	10.00
K4900	Telephone Amplifier Kit	8.50
K5200	4-Channel Multi-Function Running Light Kit	18.08
K5201	Light Computer Kit	29.94
K5203	Dual Function Strobe Kit	18.29
K5600R	Advertisement LED Display (Red) Kit	42.63
K6001	Temperature Sensor (for K6002) Kit	13.75
K6002	Temperature Controller Kit	50.11
K6003	Temperature Sensor with LED Display Kit	46.40
K6200	0 to 60 Hours Start/Stop Timer Kit	12.17
K6400	Code Lock Kit	20.37
K6501	Remote Control by Telephone Kit	38.22
K6600	Multitone Chime Kit	11.95
K6712	IR Remote Controlled Dimmer Kit	29.15
K6714	Universal Relay Card (8 Relay's) Kit	36.34
K6714-16	Universal Relay Card (16 Relay's) Kit	51.79
K7000	Signal Tracer/Injector Kit	9.27
K7101	Mains Voltage Detector Kit	7.07
K7102	Metal Detector Kit	7.62
K7105	Handheld LCD Oscilloscope Kit	135.28
K7203	3-30V 3A Power Supply Kit	25.10
K7300	Universal Battery Charger/Discharger Kit	13.84
K7302	Low Cost Universal Battery Charger Kit	6.35
K8000	PC Interface Board Kit	74.95
K8004	DC to Pulse Width Modulator Kit	9.95
K8005	Stepper Motor Card Kit	25.90
K8006	Domotica Light System - Busprint Kit	25.52
K8008	Multifunction Relay Module Kit	12.90
K8009	Multifunctional Clock Kit	53.10
K8011	Mono 95W Valve Power Amplifier Kit	345.90
K8012	Lead Acid Battery Charger/Conditioner	27.98
K8015	Multifunction Relay Switch Kit	14.94
K8016	PC Function Generator 0 - 1MHz Kit	99.98
K8017	3-Channel Sound Light with Microphone	33.80
K8020	Valve Control Amplifier Kit	207.93
K8021	High-End Control Amplifier Kit	155.37
K8023	10-Channel, 2-Wire Remote Control Kit	24.41
K8026	Suppressed 3.5A Dimmer Kit	9.94
K8027	Relay Output Module (for K8006) Kit	9.95
K8028	Multifunction Dimmer Kit	22.20
K8029	Slow On-Off Dimmer Kit	13.60
K8031	One Channel Digital PC Scope Kit	100.99
K8032	4 channel Running Light Kit	20.58
K8033	Power Blinker Kit	13.04
K8035	Multifunctional Up/Down Counter Kit	17.85
K8036	Video Signal Cleaner Kit	20.58
K8037	Bus Dimmer for Home Light System Kit	12.70
K8038	Power Dimmer, Push-Button Controlled Kit	14.80
K8039	1 Channel DMX Controlled Power Dimmer	29.95

K8040	High-End MOSFET Power Amplifier Kit	181.45
K8041	Fan Timer Kit	10.57
K8042	Symmetric 1A Power Supply Kit	7.78
K8044	12V 10-Channel Light Effect Generator Kit	21.44
K8045	Programmable Message Board with LCD	32.92
K8046	User-Definable 8-Channel Touch Panel Kit	40.63
K8047	4-Channel Recorder/Logger Kit	29.01
K8048	PIC Programmer and Experiment Board	24.65
K8049	15-Channel IR Transmitter Kit	25.73
K8050	15-Channel IR Receiver Kit	18.38
K8051	15-Channel IR Remote Stick Kit	14.35
K8055	USB Experiment Interface Board Kit	24.80
K8056	8-Channel Relay Card Kit	30.45
K8057	2-Channel RF Remote Receiver	17.19
K8058	8-Channel RF Remote Control Kit	25.73
K8059	2-Channel RF Code-Lock Transmitter Kit	11.52
K8060	Discrete Power Amplifier 200W Kit	12.85
K8061	Extended USB Interface Board Kit	66.48
K8062	USB Controlled DMX Interface Kit	47.90
K8063	2 Modular Lights with Serial Interface Kit	21.60
K8064	DC Controlled Dimmer Kit	15.93
K8065	Packet Audio Generator Kit	13.41
K8066	3W Mono Amplifier Kit	6.86
K8067	Universal Temperature Sensor Kit	10.82
K8068	Dimmer for Electronic Transformers Kit	13.98
K8070	1-Channel RF Receiver (for K8058) Kit	16.85
K8071	1W/3W High Power LED Driver Kit	5.30
K8072	DMX Controlled Relay Kit	17.47
K8074	USB to Remote control Transmitter Kit	18.95
K8075	Power Saver/Timer Kit	11.52
K8076	PIC Programmer Board Kit	24.95
K8077	Subwoofer Kit	84.80
K8081	Powerblock Kit	59.15
K8082	Safe Style CodeLock Kit	16.56
K8084	Volume & Tone Control Pre-Amplifier Kit	13.60
K8086	Telephone Ring Detector & Relay Output	11.08
K8087	Telephone Ring with Buzzer and LED Kit	10.83
K8088	RGB Controller Kit	15.15
K8089	Big Digital Clock, Temp Display Kit	40.75
K8090	8 Channel USB Relay Card Kit	39.95
K8091	LED Clock with Light Dimmer Function Kit	22.49
K8092	Optical proximity switch Kit	17.45
K8095	SD/HCSM MP3 Player Kit	39.99
K8098	Audio Analyser Kit	31.65
K8099	Nixie Clock Kit	64.96
K8100	Video Digitiser Card for PC Kit	113.69


**Velleman Mini Kits**

MK100	Electronic Christmas Tree Minikit	5.63
MK101	Flashing LED Sweetheart Minikit	6.25
MK102	Flashing LED's Minikit	2.99
MK103	Sound to Light Minikit	4.21
MK104	Electronic Cricket Minikit	6.73
MK105	Signal Generator Minikit	4.21
MK106	Metronome Minikit	6.90
MK107	LED Running Light Minikit	4.75
MK108	Water Alarm Minikit	3.74
MK109	Electronic Dice Minikit	4.45
MK110	Simple One Channel Light Organ Minikit	5.84
MK111	Interval Timer Minikit	4.60
MK112	Brain Game Minikit	5.95
MK113	Siren Sound Generator Minikit	5.40
MK114	Low Voltage Light Organ Minikit	7.53
MK115	Packet VU Meter Minikit	4.25
MK116	Riding Santa Minikit	12.45
MK117	Delux Xmas Tree Minikit	12.68
MK118	FM Radio Minikit	14.73
MK119	Roulette Minikit	11.82
MK120	Light Barrier Minikit	6.90
MK121PAL	Classic TV Game Minikit	10.70
MK122	Animated Bell with 83 LED's Minikit	8.25
MK123	Rolling Clock Minikit	14.79
MK124	Rolling Message Minikit	11.91
MK125	Light Sensitive Switch Minikit	3.95
MK126	Car Alarm Simulator Minikit	4.22
MK127	Running Microbug Minikit	9.02
MK128	Kitchen Timer Minikit	11.55
MK129	Crawling Microbug Minikit	11.48
MK130	3D Xmas Tree Minikit	7.69
MK131	Traffic Light Minikit	6.85
MK132	Cable Polarity Checker Minikit	5.05
MK133	Quiz Table Minikit	6.85
MK134	Steam Engine Sound Generator Minikit	7.47
MK135	Electronic Decision Maker Minikit	3.38
MK136	Super Stereo Ear Minikit	7.44
MK137	IR Remote Checker Minikit	4.43
MK138	Thermostat Minikit	4.95
MK139	Clap On/Off Switch Minikit	10.80
MK140	Karaoke Minikit	8.67
MK141	SMD Happy Face Minikit	4.17
MK142	SMD Xmas Tree Minikit	5.29
MK143	White LED Flashlight Minikit	7.07
MK144	Flashing Heart Minikit	5.29
MK145	Halloween Pumpkin Minikit	7.63

MK146	Pocket VU Meter Minikit (with Enclosure)	7.44
MK147	Dual White LED Stroboscope Minikit	5.20
MK148	Dual Super Bright Flashing Red Lights	4.43
MK149	Love Tester Minikit	11.15
MK150	Shaking Dice Minikit	8.49
MK151	Digital LED Clock Minikit	15.09
MK152	Wheel of Fortune Minikit	3.95
MK153	Jumbo Single Digit Clock Minikit	12.53
MK154	5 in 1 Emergency Tool Minikit	11.84
MK155	Magic Message Minikit	11.84
MK157	LCD Mini Message Board Minikit	15.96
MK158	LCD Mini Message Board with Backlight	21.14
MK159	Brain Game Minikit	10.47
MK160	Remote Control via GSM Mobile Phone	8.93
MK161	2-Channel IR Remote Receiver Minikit	9.95
MK162	2-Channel IR Remote Transmitter Minikit	8.49
MK163	Electronic Stereo Volume Control Minikit	10.90
MK164	IR Electronic Volume Control Minikit	14.79
MK165	Crawling Bug Minikit	13.89
MK166	Animated Ghost Minikit	9.09
MK167	Electronic Candle Minikit	3.81
MK168	Alarm Sensor Simulator Minikit	5.95
MK169R	Flashing LED Star (Red) Minikit	6.20
MK169Y	Flashing LED Star (Yellow) Minikit	6.20
MK170	60 LED Multi-Effect Star Minikit	10.98
MK171	Voice Changer Minikit	6.71
MK172	Sound LED Star Minikit	7.83
MK173	Mini 6-LED Chaser Minikit	8.50
MK174	Single-Message Record/Playback Minikit	11.87
MK175	Animated LED Smiley Minikit	7.45
MK176	LED Chevron Arrow Minikit	8.49
MK177	Ding Dong Minikit	4.90
MK178	3rd Brake Light Flasher Minikit	6.30
MK179	Proximity Card reader Minikit	14.25
MK180	2 Channel Hi-power LED Flasher Minikit	10.50
MK181	AC Power voltage indicator LED Minikit	2.43
MK182	Digital Echo Chamber Minikit	11.43

**Velleman Modules - Assembled**

VM100	200W Power Amplifier Module	38.54
VM101	Multifunctional Dimmer Module	34.90
VM103	Blinking Module	34.43
VM105	AC Power Slave Module	34.43
VM106	Video Signal Cleaner Module	30.44
VM107	Multifunctional Counter Module	38.91
VM110	USB Interface Card Module	34.90
VM111	PIC Programmer and Experiment Module	32.60
VM112	Personal Animated Badge Module	19.95
VM113	Stereo Amplifier Module 2 x 30W	19.25
VM114	7W Mono Audio Amplifier Module	7.95
VM116	USB Controlled DMX Interface Module	67.15
VM118	8-Channel RF Remote Control Set Module	68.77
VM118R	8-Channel RF Remote Transmitter Module	36.02
VM119	One Channel Dual Output Receiver	19.40
VM120	10-Channel Light Effect Generator	32.02
VM121	15-Channel Infrared Transmitter Module	36.02
VM122	15-Channel Infrared Receiver Module	29.62
VM124	1A Power Supply Module	6.50
VM125	Ultrasonic Radar Module	26.54
VM129	8-Channel Relay Card Module	33.29
VM130	2-Channel RF Remote Control Set Module	35.45
VM130T	2-Channel RF Remote Control Transmitter	12.90
VM131	Dimmer for Electronic Transformers	24.04
VM132	Universal Temperature Sensor Module	13.04
VM133	Energy Saver Module	18.15
VM134	PIC Programmer Board Module	36.90
VM135	Magical Dimmer Module	13.58
VM136	Interval Timer Module	6.30
VM137	Thermostat Module 5° - 30°C Module	7.95
VM138	DMX Controlled Relay Module	21.74
VM139	IR Remote Checker Module	7.64
VM140	Extender USB Interface Board Module	79.95
VM141	Start/Stop Timer Module	12.95
VM142	Mini-Pic Application Module	26.00
VM143/1W	1W High Power LED Driver Module	9.85
VM143/3W	3W High Power LED Driver Module	9.95
VM144	Telephone Ring Detector & Relay output	14.65
VM145	Digital Panel Thermometer Min/Max	23.35
VM146	RGB Controller Module	22.52
VM147	Panel Counter Module	23.35
VM148	Panel Thermostat Module	26.80
VM150	RGB LED Dimmer for DIN rail (Due July)	31.00
VM151	RGB Controller Module & remote control	26.35
VM152	LED Dimmer with RF Remote Control	29.53
VM154	Fan Timer Module	17.55
VM156	Pocket Audio Generator Module	20.00
VM160	4 Channel RF Remote Control Set	47.50
VM160DT	4 Channel RF Desktop Transmitter	46.28
VM160T	4 Channel RF Replacement transmitter	17.05
VM161	RGB LED Strip Colour controller Module	22.75
VM162	RGB LED Strip Colour dimmer Module	30.86
VM163	Panel Clock Module	25.17
VM164	Mini Dimmer, Push button control (Due July)	14.78
VM165	0-10V DC Controlled Dimmer (Due June)	48.95
VM179	Proximity Card Reader Module	25.65
VM8090	8 Channel USB Relay Card (Due July)	58.40

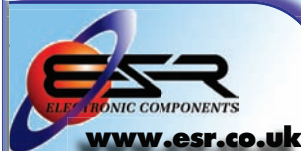**Over 300 Kits, Mini Kits & Modules - check web site for details**

**Tel: 0191 2514363**  
**Fax: 0191 2522296**  
**sales@esr.co.uk**

**Station Road**  
**Cullercoats**  
**Tyne & Wear**  
**NE30 4PQ**



Prices Exclude Vat @17.5%.  
 UK Carriage £2.50 (less than 1kg)  
 £5.50 greater than 1kg or >£30  
 Cheques / Postal orders payable to  
 ESR Electronic Components Ltd.  
 PLEASE ADD CARRIAGE & VAT TO ALL ORDERS



ISSN 0262 3617

- PROJECTS • THEORY •
- NEWS • COMMENT •
- POPULAR FEATURES •

VOL. 39. No 7

July 2010

# **EPE** EVERYDAY PRACTICAL ELECTRONICS

INCORPORATING ELECTRONICS TODAY INTERNATIONAL

[www.epemag.com](http://www.epemag.com)



## Projects and Circuits

- |  |           |
|--|-----------|
| <b>SWIMMING POOL ALARM</b> by John Clarke                                  | <b>10</b> |
| Reduce the possibility of a drowning in your swimming pool                 |           |
| <b>DSP MUSICOLOUR - PART 3</b> by Mauro Grassi                             | <b>22</b> |
| Calibrating and operating this ingenious unit                              |           |
| <b>HOW TO SOLDER SURFACE-MOUNT DEVICES</b> by Jim Rowe                     | <b>32</b> |
| Indispensable guide to successfully tackling these tiny components         |           |
| <b>COLDALERT HYPOTHERMIA ALARM</b> by David Clark                          | <b>42</b> |
| Low-cost PIC-based alarm to help an elderly or vulnerable person stay warm |           |
| <b>INGENUITY UNLIMITED</b>   | <b>58</b> |
| Clock Generator - Time Out   |           |

## Series and Features

- |   |           |
|---|-----------|
| <b>TECHNO TALK</b> by Mark Nelson   | <b>20</b> |
| What's That?  |           |
| <b>RECYCLE IT!</b> by Julian Edgar  | <b>48</b> |
| Fax Machines and Hair Trimmers  |           |
| <b>CIRCUIT SURGERY</b> by Ian Bell  | <b>53</b> |
| Regulators - A Hot Topic  |           |
| <b>PRACTICALLY SPEAKING</b> by Robert Penfold   | <b>56</b> |
| Back to basics: from nuts and bolts to soldering  |           |
| <b>MAX'S COOL BEANS</b> by Max The Magnificent  | <b>63</b> |
| So much to do, so little time; NASA and the JPL;<br>The Embedded conference; It doesn't slow down |           |
| <b>NET WORK</b> by Alan Winstanley  | <b>66</b> |
| A 3D view; The sound of beating TomToms; Too much information                                     |           |

## Regulars and Services

- |   |           |
|---|-----------|
| <b>EDITORIAL</b>  | <b>7</b>  |
| <b>NEWS</b> - Barry Fox highlights technology's leading edge                  | <b>8</b>  |
| Plus everyday news from the world of electronics                              |           |
| <b>BACK ISSUES</b> Did you miss these?  | <b>40</b> |
| <b>WIN A MICROCHIP PICKIT 3 DEBUG EXPRESS KIT</b>                             | <b>46</b> |
| An <i>EPE</i> exclusive <i>FREE</i> entry competition                         |           |
| <b>SUBSCRIBE TO <i>EPE</i></b> and save money                                 | <b>52</b> |
| <b>CD-ROMS FOR ELECTRONICS</b>  | <b>60</b> |
| A wide range of CD-ROMs for hobbyists, students and engineers                 |           |
| <b>READOUT</b> Matt Pulzer addresses general points arising                   | <b>64</b> |
| <b>DIRECT BOOK SERVICE</b>  | <b>67</b> |
| A wide range of technical books available by mail order,<br>plus more CD-ROMs |           |
| <b><i>EPE</i> PCB SERVICE</b>   | <b>70</b> |
| PCBs for <i>EPE</i> projects  |           |
| <b>ADVERTISERS INDEX</b>  | <b>72</b> |

**PLEASE NOTE: AS OF THE 1 JULY 2010 OUR OFFICES  
WILL BE AT:**

**113 LYNWOOD DRIVE, MERLEY, WIMBORNE, DORSET, BH21 1UU**

© Wimborne Publishing Ltd 2010. Copyright in all drawings, photographs and articles published in *EVERYDAY PRACTICAL ELECTRONICS* is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our August 2010 issue will be published on  
Thursday 8 July 2010, see page 72 for details.

*Everyday Practical Electronics*, July 2010

**Readers' Services • Editorial and Advertisement Departments**

**7**

**1**

**Copyright © 2010, Wimborne Publishing Ltd**  
**(Sequoia House, 398a Ringwood Road, Ferndown, Dorset BH22 9AU, UK)**  
**and TechBites Interactive Inc.,**  
**(PO Box 857, Madison, Alabama 35758, USA)**  
**All rights reserved.**

## **WARNING!**

The materials and works contained within *EPE Online* — which are made available by Wimborne Publishing Ltd and TechBites Interactive Inc — are copyrighted. You are permitted to make a backup copy of the downloaded file and one (1) hard copy of such materials and works for your personal use.

International copyright laws, however, prohibit any further copying or reproduction of such materials and works, or any republication of any kind. TechBites Interactive Inc and Wimborne Publishing Ltd have used their best efforts in preparing these materials and works. However, TechBites Interactive Inc and Wimborne Publishing Ltd make no warranties of any kind, expressed or implied, with regard to the documentation or data contained herein, and specifically disclaim, without limitation, any implied warranties of merchantability and fitness for a particular purpose. Because of possible variances in the quality and condition of materials and workmanship used by readers, *EPE Online*, its publishers and agents disclaim any responsibility for the safe and proper functioning of reader-constructed projects based on or from information published in these materials and works. In no event shall TechBites Interactive Inc or Wimborne Publishing Ltd be responsible or liable for any loss of profit or any other commercial damages, including but not limited to special, incidental, consequential, or any other damages in connection with or arising out of furnishing, performance, or use of these materials and works.



**01279**

**Credit Card  
Sales**

**467799**

## PIC & ATMEL Programmers

We have a wide range of low cost PIC and ATMEL Programmers. Complete range and documentation available from our web site.

### Programmer Accessories:

40-pin Wide ZIF socket (ZIF40W) £14.95  
18Vdc Power supply (PSU120) £19.95  
Leads: Parallel (LDC136) £3.95 / Serial (LDC441) £3.95 / USB (LDC644) £2.95

### NEW! USB & Serial Port PIC Programmer



USB/Serial connection.  
Header cable for ICSP.  
Free Windows XP software. See website for PICs supported. ZIF Socket and USB lead extra. 18Vdc.

Kit Order Code: 3149EKT - £49.95  
Assembled Order Code: AS3149E - £59.95  
Assembled with ZIF socket Order Code: AS3149EZIF - £74.95

### NEW! USB 'All-Flash' PIC Programmer

USB PIC programmer for all 'Flash' devices. No external power supply making it truly portable. Supplied with box and Windows XP Software. ZIF Socket and USB lead not incl.  
Assembled Order Code: AS3128 - £49.95  
Assembled with ZIF socket Order Code: AS3128ZIF - £64.95



### ATMEL 89xxx Programmer



Uses serial port and any standard terminal comms program. 4 LED's display the status. ZIF sockets not included. Supply: 16Vdc.

Kit Order Code: 3123KT - £27.95  
Assembled Order Code: AS3123 - £37.95

### Introduction to PIC Programming

Go from complete beginner to burning a PIC and writing code in no time! Includes 49 page step-by-step PDF Tutorial Manual, Programming Hardware (with LED test section), Win 3.11—XP Programming Software (Program, Read, Verify & Erase), and 1 re-writable PIC16F84A that you can use with different code (4 detailed examples provided for you to learn from). PC parallel port.  
Kit Order Code: 3081KT - £16.95  
Assembled Order Code: AS3081 - £24.95



### PIC Programmer Board

Low cost PIC programmer board supporting a wide range of Microchip® PIC™ microcontrollers. Requires PC serial port. Windows interface supplied.

Kit Order Code: K8076KT - £39.95



### PIC Programmer & Experimenter Board

The PIC Programmer & Experimenter Board with test buttons and LED indicators to carry out educational experiments, such as the supplied programming examples. Includes a 16F627 Flash Microcontroller that can be reprogrammed up to 1000 times for experimenting at will. Software to compile and program your source code is included.  
Kit Order Code: K8048KT - £39.95  
Assembled Order Code: VM111 - £59.95



## Controllers & Loggers

Here are just a few of the controller and data acquisition and control units we have. See website for full details. 12Vdc PSU for all units: Order Code PSU445 £7.95

### USB Experiment Interface Board

5 digital input channels and 8 digital output channels plus two analogue inputs and two analogue outputs with 8 bit resolution.

Kit Order Code: K8055KT - £38.95  
Assembled Order Code: VM110 - £64.95



### Rolling Code 4-Channel UHF Remote

State-of-the-Art. High security. 4 channels. Momentary or latching relay output. Range up to 40m. Up to 15 Tx's can be learnt by one Rx (kit includes one Tx but more available separately). 4 indicator LED's. Rx: PCB 77x85mm, 12Vdc/6mA (standby). Two & Ten Channel versions also available.  
Kit Order Code: 3180KT - £49.95  
Assembled Order Code: AS3180 - £59.95



### Computer Temperature Data Logger



Serial port 4-channel temperature logger. °C or °F. Continuously logs up to 4 separate sensors located 200m+ from board. Wide range of free software applications for storing/using data. PCB just 45x45mm. Powered by PC. Includes one DS1820 sensor.  
Kit Order Code: 3145KT - £19.95  
Assembled Order Code: AS3145 - £26.95  
Additional DS1820 Sensors - £3.95 each

### Remote Control Via GSM Mobile Phone

Place next to a mobile phone (not included). Allows toggle or auto-timer control of 3A mains rated output relay from any location with GSM coverage.  
Kit Order Code: MK160KT - £13.95



Most items are available in kit form (KT suffix) or pre-assembled and ready for use (AS prefix).

### 4-Ch DTMF Telephone Relay Switcher

Call your phone number using a DTMF phone from anywhere in the world and remotely turn on/off any of the 4 relays as desired. User settable Security Password, Anti-Tamper, Rings to Answer, Auto Hang-up and Lockout. Includes plastic case. 130 x 110 x 30mm. Power: 12Vdc.  
Kit Order Code: 3140KT - £74.95  
Assembled Order Code: AS3140 - £89.95



### 8-Ch Serial Port Isolated I/O Relay Module

Computer controlled 8 channel relay board. 5A mains rated relay outputs and 4 opto-isolated digital inputs (for monitoring switch states, etc). Useful in a variety of control and sensing applications. Programmed via serial port (use our new Windows interface, terminal emulator or batch files). Serial cable can be up to 35m long. Includes plastic case 130x100x30mm. Power: 12Vdc/500mA.  
Kit Order Code: 3108KT - £64.95  
Assembled Order Code: AS3108 - £79.95



### Infrared RC 12-Channel Relay Board

Control 12 onboard relays with included infrared remote control unit. Toggle or momentary. 15m+ range. 112 x 122mm. Supply: 12Vdc/0.5A  
Kit Order Code: 3142KT - £59.95  
Assembled Order Code: AS3142 - £69.95



### Audio DTMF Decoder and Display

Detect DTMF tones from tape recorders, receivers, two-way radios, etc using the built-in mic or direct from the phone line. Characters are displayed on a 16 character display as they are received and up to 32 numbers can be displayed by scrolling the display. All data written to the LCD is also sent to a serial output for connection to a computer. Supply: 9-12V DC (Order Code PSU445). Main PCB: 55x95mm.  
Kit Order Code: 3153KT - £34.95  
Assembled Order Code: AS3153 - £44.95



### Telephone Call Logger

Stores over 2,500 x 11 digit DTMF numbers with time and date. Records all buttons pressed during a call. No need for any connection to computer during operation but logged data can be downloaded into a PC via a serial port and saved to disk. Includes a plastic case 130x100x30mm. Supply: 9-12V DC (Order Code PSU445).  
Kit Order Code: 3164KT - £54.95  
Assembled Order Code: AS3164 - £69.95





## Hot New Products!

Here are a few of the most recent products added to our range. See website or join our email Newsletter for all the latest news.

### 4-Channel Serial Port Temperature Monitor & Controller Relay Board

4 channel computer serial port temperature monitor and relay controller with four inputs for Dallas DS18S20 or DS18B20 digital thermometer sensors (£3.95 each). Four 5A rated relay channels provide output control. Relays are independent of sensor channels, allowing flexibility to setup the linkage in any way you choose. Commands for reading temperature and relay control sent via the RS232 interface using simple text strings. Control using a simple terminal / comms program (Windows HyperTerminal) or our free Windows application software. Kit Order Code: 3190KT - **£69.95**  
Assembled Order Code: AS3190 - **£84.95**



### 40 Second Message Recorder

Feature packed non-volatile 40 second multi-message sound recorder module using a high quality Winbond sound recorder IC. Stand-alone operation using just six onboard buttons or use onboard SPI interface. Record using built-in microphone or external line in. 8-24 Vdc operation. Just change one resistor for different recording duration/sound quality. sampling frequency 4-12 kHz. Kit Order Code: 3188KT - **£28.95**  
Assembled Order Code: AS3188 - **£36.95**  
120 second version also available




### Bipolar Stepper Motor Chopper Driver

Get better performance from your stepper motors with this dual full bridge motor driver based on SGS Thompson chips L297 & L298. Motor current for each phase set using on-board potentiometer. Rated to handle motor winding currents up to 2 Amps per phase. Operates on 9-36Vdc supply voltage. Provides all basic motor controls including full or half stepping of bipolar steppers and direction control. Allows multiple driver synchronisation. Perfect for desktop CNC applications. Kit Order Code: 3187KT - **£39.95**  
Assembled Order Code: AS3187 - **£49.95**


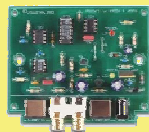
### Video Signal Cleaner

Digitally cleans the video signal and removes unwanted distortion in video signal. In addition it stabilises picture quality and luminance fluctuations. You will also benefit from improved picture quality on LCD monitors or projectors. Kit Order Code: K8036KT - **£32.95**  
Assembled Order Code: VM106 - **£49.95**



Most items are available in kit form (KT suffix) or assembled and ready for use (AS prefix).

## Motor Speed Controllers

Here are just a few of our controller and driver modules for AC, DC, Unipolar/Bipolar stepper motors and servo motors. See website for full details.

### DC Motor Speed Controller (100V/7.5A)



Control the speed of almost any common DC motor rated up to 100V/7.5A. Pulse width modulation output for maximum motor torque at all speeds. Supply: 5-15Vdc. Box supplied. Dimensions (mm): 60Wx100Lx60H. Kit Order Code: 3067KT - **£17.95**  
Assembled Order Code: AS3067 - **£24.95**

### Computer Controlled / Standalone Unipolar Stepper Motor Driver

Drives any 5-35Vdc 5, 6 or 8-lead unipolar stepper motor rated up to 6 Amps. Provides speed and direction control. Operates in stand-alone or PC-controlled mode for CNC use. Connect up to six 3179 driver boards to a single parallel port. Board supply: 9Vdc. PCB: 80x50mm. Kit Order Code: 3179KT - **£15.95**  
Assembled Order Code: AS3179 - **£22.95**



### Computer Controlled Bi-Polar Stepper Motor Driver

Drive any 5-50Vdc, 5 Amp bi-polar stepper motor using externally supplied 5V levels for STEP and DIRECTION control. Opto-isolated inputs make it ideal for CNC applications using a PC running suitable software. Board supply: 8-30Vdc. PCB: 75x85mm. Kit Order Code: 3158KT - **£23.95**  
Assembled Order Code: AS3158 - **£33.95**



### Bidirectional DC Motor Speed Controller



Control the speed of most common DC motors (rated up to 32Vdc/10A) in both the forward and reverse direction. The range of control is from fully OFF to fully ON in both directions. The direction and speed are controlled using a single potentiometer. Screw terminal block for connections. Kit Order Code: 3166v2KT - **£22.95**  
Assembled Order Code: AS3166v2 - **£32.95**

### AC Motor Speed Controller (600W)

Reliable and simple to install project that allows you to adjust the speed of an electric drill or 230V AC single phase induction motor rated up to 600 Watts. Simply turn the potentiometer to adjust the motors RPM. PCB: 48x65mm. Not suitable for use with brushless AC motors. Kit Order Code: 1074KT - **£14.95**  
Assembled Order Code: AS1074 - **£23.95**



See [www.quasarelectronics.com](http://www.quasarelectronics.com) for lots more motor controllers



**QUASAR**  
electronics  
The Electronic Kit Specialists Since 1993

**Credit Card Sales**  
**01279 467 799**

## Electronic Project Labs

Great introduction to the world of electronics. Ideal gift for budding electronics expert!

### 500-in-1 Electronic Project Lab

Top of the range. Complete self-contained electronics course. Takes you from beginner to 'A' Level standard and beyond! Contains all the hardware and manuals to assemble 500 projects. You get 3 comprehensive course books (total 368 pages) - *Hardware Entry Course*, *Hardware Advanced Course* and a microprocessor based *Software Programming Course*. Each book has individual circuit explanations, schematic and connection diagrams. Suitable for age 12+. Order Code EPL500 - **£179.95**  
**Also available:** 30-in-1 **£19.95**, 50-in-1 **£29.95**, 75-in-1 **£39.95** £130-in-1 **£44.95** & 300-in-1 **£69.95** (see website for details)



## Tools & Test Equipment

We stock an extensive range of soldering tools, test equipment, power supplies, inverters & much more - please visit website to see our full range of products.

### Two-Channel USB Pc Oscilloscope

This digital storage oscilloscope uses the power of your PC to visualize electrical signals. Its high sensitive display resolution, down to 0.15mV, combined with a high bandwidth and a sampling frequency of up to 1GHz are giving this unit all the power you need. Order Code: PCSU1000 - **£399.95**



### Personal Scope 10MS/s

The Personal Scope is not a graphical multimeter but a complete portable oscilloscope at the size and the cost of a good multimeter. Its high sensitivity - down to 0.1mV/div - and extended scope functions make this unit ideal for hobby, service, automotive and development purposes. Because of its exceptional value for money, the Personal Scope is well suited for educational use. Order Code: HPS10 - **£189.95** ~~£169.95~~



See website for more super deals!



[www.quasarelectronics.com](http://www.quasarelectronics.com)

Secure Online Ordering Facilities • Full Product Listing, Descriptions & Photos • Kit Documentation & Software Downloads



# EVERYDAY PRACTICAL ELECTRONICS FEATURED KITS

Everyday Practical Electronics Magazine has been publishing a series of popular kits by the acclaimed Silicon Chip Magazine Australia. These projects are 'bullet proof' and already tested down under. All Jaycar kits are supplied with specified board components, quality fibreglass tinned PCBs and have clear English instructions. Watch this space for future featured kits.

July 2010

## 4 CHANNEL VERSATILE MIXER KIT

**KC-5448 £28.75 plus postage & packing**

This is an improved version of our popular guitar mixer kit. The input sensitivity of each of the four channels is adjustable from a few millivolts to over 1 volt, so you plug in a range of input signals from a microphone to a line level signal from a CD player etc. Also features a 3-stage EQ and headphone amplifier circuit for monitoring purposes, making this a very versatile mixer that will operate from 12 volts. Kit includes case, PCB with overlay and all electronic components.

Featured in EPE  
April 2009



## WATER TANK LEVEL METER KIT

**KC-5460 £31.75 plus postage & packing**

This PIC-based unit uses a pressure sensor and displays the tank level via an RGB LED at the press of a button. Add optional wireless remote display panel to monitor up to ten separate tanks (KC-5461) or you can add a wireless remote controlled mains power switch (KC-5462) to control remote water pumps. Kit includes electronic components, case, screen printed PCB and pressure sensor.

Also available:  
Remote display kit KC-5461 £24.75  
UHF remote mains switch  
kit KC-5462 £29.00

Featured in EPE Mar/May 2010




## CDI KIT FOR MOTOR BIKES

**KC-5466 £6.50 plus postage & packing**

Many modern motor bikes use a Capacitor Discharge Ignition (CDI) to improve performance and enhance reliability. However, if the CDI ignition module fails, a replacement can be very expensive. This kit will replace many failed factory units and is suitable for engines that provide a positive capacitor voltage and have a separate trigger coil. Supplied with solder masked PCB and overlay, case and components. Some mounting hardware required.

• PCB: 45 x 64mm

Featured in this issue of EPE

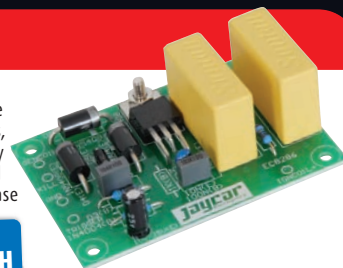

FEATURED  
THIS MONTH

## AV SIGNAL BOOSTER KIT

**KC-5350 £31.95 plus postage & packing**

You may experience some signal loss when using long AV cables. This kit will boost your composite, S-Video and stereo audio signals, preserving them for the highest quality transmission to your home theatre, projector or large screen TV. Kit includes case, PCB, silk-screened punched panels and all electronic components with clear English instructions. Requires 9VAC wall adaptor.

Featured in EPE March 2006



## SPEAKER BASS EXTENDER KIT

**KC-5411 £6.00 plus postage & packing**

Most audiophiles know that loudspeaker enclosures have a natural frequency rolloff which is inherent in their design. Crude bass boost devices that are available simply boost the level of bass anywhere up to +18dB, to offer better bass response. This isn't the best way to do it. The Bass Extender kit boosts the level of the bass to counteract the natural rolloff of the enclosure, producing rich, natural bass. It gives an extra octave of response, and is sure to please even the most avid sound enthusiasts.

• Kit supplied with PCB, and all electronic components

Featured in EPE March 2007



## PIC MICROCONTROLLER SERIAL PROGRAMMER KIT

**KC-5467 £21.75 plus postage & packing**

This very cost effective programmer kit can handle all the dsPIC30F family and almost all of the regular PICs available in a DIP package. It uses freely available software for PCs and is easy to build. Microchip offers free documentation and source code on their website so getting started should be a breeze. Supplied with screen printed PCB, 2 x 40 pin ZIF sockets and all specified components.

Featured in EPE April 2010



## EMERGENCY 12V LIGHTING CONTROLLER KIT

**KC-5456 £20.50 plus postage & packing**

Automatically supplies power for 12V emergency lighting during a blackout. The system is powered with a 7.5Ah SLA battery which is maintained via an external smart charger. Includes manual override and over-discharge protection for the battery. Kit supplied with all electronic components, screen printed PCB, front panel and case. Charger and SLA battery available separately.

Featured in EPE  
November 2009



## 50MHZ FREQUENCY METER KIT

**KC-5369 £16.00 plus postage & packing**

Low cost and invaluable for servicing and diagnostics, this compact autorangeing meter has an 8 digit LCD display and shows frequency in either Hz, kHz or MHz. Kit includes PCB, case with machined and silkscreened lid, pre-programmed PIC and all electronic components with clear instructions.

• Requires 9VDC adaptor (Maplin #GS74R)

Featured in EPE  
September 2006



## AC/DC CURRENT CLAMP METER KIT FOR DMMs

**KC-5368 £8.75 plus postage & packing**

It uses a simple hall effect sensor & iron ring core set up, & connects to your digital multimeter. It will measure AC & DC current & has a calibration dial to allow for any magnetising of the core. Much cheaper than pre-built units.

• Kit supplied with PCB, clamp, case with silk screened front panel & all electronic components.

Featured in EPE June 2006



## SMS CONTROLLER MODULE KIT

**KC-5400 £17.00 plus postage & packing**

Control appliances and receive alert notification from anywhere. It controls up to eight devices by sending plain text messages and simultaneously monitors four digital inputs. It works with old Nokia handsets such as the 5110, 6110, 3210, and 3310, which can be bought inexpensively. Kit supplied with manual, PCB, pre-programmed microcontroller and all electronic components. Requires a common Nokia data cable found in many retail stores.

Featured in EPE March 2007



## SCI-FI SFX KITS

### Mini Theremin Synthesiser MKII Kit

**KC-5426 £43.50 plus postage & packing**

Create unusual sound effects by moving your hand between the antennas! The Theremin MkII improves on its predecessor by allowing adjustments to be made to the tonal quality and features better waveform. Kit includes stand, PCB with overlay, machined case with silkscreen printed lid, loud speaker, pitch and volume antennas & all specified electronic components.

Featured in EPE May/June 2008



### Starship Enterprise Door Sound Emulator Kit

**KC-5423 £11.75 plus postage & packing**

This easy to build kit emulates the unique noise made when the cabin doors on the Starship Enterprise open & close. The sound emulator can be triggered by switch contacts (normally open) which means you can use a reed magnet switch, IR beam or PIR detector to trigger the unit. Kit includes PCB with overlay, case & all electronic components with clear instructions.

• Requires 9-12VDC power  
Featured in EPE June 2008




# AUTOMOTIVE & POWER KITS FOR ELECTRONIC ENTHUSIASTS

## SPEEDO CORRECTOR MKII KIT

### KC-5435 £16.00 plus postage & packing

This kit readjusts the speedometer signal up or down from 0% to 99% of the original signal. This upgraded model enables automatic input setup selection and indicates when the input signal is being received. Kit supplied with PCB with overlay and all electronic components.

Recommended box UB5 use HB-6013 £1.25

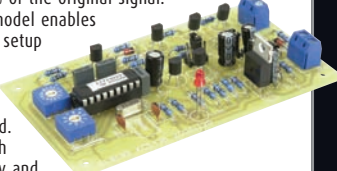

## DIGITAL TACHOMETER KIT

### KC-5290 £19.75 plus postage & packing

Housed neatly in a small jiffy box (83 x 54 x 31mm) to mount nicely on your dashboard, it features 10 LED bargraph with optional dot or bar mode (showing 8-independent rpm thresholds), calibration options for 1-12 cylinder 4-stroke or 1-6 cylinder 2-stroke engines, anti-flickering and automatic night-time display dimming. This kit can also be combined with our rev limiter KC-5265, to perform engine limiting. Kit includes case with silk-screened panel, PCBs, pre-programmed PIC micro, 7-segment displays, red acrylic, hook-up wire and all electronic components.



## 10A 12VDC MOTOR SPEED CONTROLLER KIT

### KC-5225 £7.25 plus postage & packing

Ideal for controlling 12VDC motors in cars such as fuel injection pumps, water/air intercoolers and water injection systems. Use it for headlight dimming or for running 12VDC motors in 24V vehicles. The circuit incorporates a soft start feature to reduce inrush currents, especially on 12V incandescent lamps. Kit includes PCB and all electronic components.



## MIXTURE DISPLAY KIT FOR FUEL INJECTED CARS

### KC-5195 £5.00 plus postage & packing

Also known as an EGO (exhaust, gas, oxygen) monitor, this simple kit allows you to monitor your car's fuel mixtures. Use it as a tuning tool to help in vehicle modification or simply to see the behaviour of the engine control module. LEDs indicate whether mixtures are rich, lean or normal. PCB, LEDs and components supplied. Thousands sold!



## CAR HEADLIGHT REMINDER KIT

### KC-5317 £8.25 plus postage & packing

Features include a modulated alarm, ignition and lights monitoring, optional door switch detection, time-out alarm and a short delay before the alarm sounds. 12VDC kit includes quality solder masked PCB with overlay, case with screen printed lid and all electronic components.



## HIGH PERFORMANCE TIMER KIT

### KC-5379 £12.50 plus postage & packing

A sophisticated timer adaptable for two types of uses.



The first is 'one shot' operation, which can be used to keep electric windows active, or a thermo fan running for a period after ignition is switched off etc. The second is a 'pulse' type operation, which can be used to squirt water spray for 1 second every 9 seconds. The uses are endless, with time adjustable from 0.1 sec to 16.5 mins. Kit supplied with PCB and all electronic components.

## FUEL KITS

### Wideband Fuel Mixture Controller Kit

#### KC-5486 £23.25 plus postage & packing

Partner to the Wideband Sensor Display Kit KC-5485 (below) and intended to be used with a Bosch wideband LSU4.2 oxygen sensor to accurately measure air/fuel ratios over a wide range from rich to lean. It can be used for precise engine tuning and can be a permanent installation in the car or a temporary connection to the exhaust tailpipe. This 12VDC kit comes with PCB and all electronic components including programmed PIC, and case with screen printed lid.

• PCB: 112 x 87mm



### Fuel/Air Mixture Display Kit

#### KC-5485 £17.50 plus postage & packing

Displays your car's air-fuel ratio as you drive. Designed to monitor a wideband oxygen sensor and its associated wideband controller. Alternatively it can be used to monitor a narrowband oxygen sensor or for monitoring other types of engine sensors.

- 12VDC
- Double-sided plated PCB
- Programmed PIC
- Electronic components
- Case with machined lid and screen printed lid



## VOLTAGE MODIFIER KIT

### KC-5490 £23.25 plus postage & packing

Restore correct air/fuel ratios after engine modifications, prevent engine boost cuts; or alter sensor signals for improved drivability. Requires hand controller for programming, RS232 cable and a suitable input signal. Kit includes PCB, case and electronic components.

Recommended with this kit:  
Hand Controller Cat. KC-5386 £19.75  
RS232 Cable Cat. WC-7502 £4.00



## POWER KITS

### 3V to 9V DC-DC Converter Kit

#### KC-5391 £4.75 plus postage & packing

Allows you to use regular Ni-Cd or Ni-MH 1.2V cells, or Alkaline 1.5V cells for 9V applications. Use low cost, high capacity rechargeable cells - imagine the extra capacity you would have using two 9000mAh D cells in replacement of a low capacity 9V cell. Kit supplied with PCB and electronic components.



### DC Relay Switch Kit

#### KC-5434 £5.00 plus postage & packing

An extremely useful and versatile kit that enables you to use a tiny trigger current as low as 400µA at 12V to switch up to 30A at 50VDC. The kit includes PCB with overlay and all electronic components with clear English instructions.



**FREE**  
**JAYCAR 2010**  
**UK CATALOGUE**

[www.jaycarelectronics.co.uk/catalogue](http://www.jaycarelectronics.co.uk/catalogue)

Log in for your free copy

## POST & PACKING CHARGES

Order Value	Cost
£10 - £49.99	£5
£50 - £99.99	£10
£100 - £199.99	£20
£200 - £499.99	£30
£500+	£40

Max weight 12lb (5kg)  
Heavier parcels POA  
Minimum order £10

**Note: Products are despatched from Australia, so local customs duty & taxes may apply.**

- All pricing in Pounds Sterling
- Minimum order £10

Prices valid until 31/07/2010

## HOW TO ORDER

**WEB:** [www.jaycarelectronics.co.uk](http://www.jaycarelectronics.co.uk)  
**PHONE:** 0800 032 7241\*  
**FAX:** +61 2 8832 3118\*  
**EMAIL:** [techstore@jaycarelectronics.co.uk](mailto:techstore@jaycarelectronics.co.uk)  
**POST:** P.O. Box 107, Rydalmere NSW 2116 Australia

\*Australian Eastern Standard Time  
(Monday - Friday 09.00 to 17.30 GMT + 10 hours)  
Expect 10-14 days for air parcel delivery

## KIT OF THE MONTH

### SD/MMC Card Webserver In a Box

#### KC-5489 £26.25 plus postage & packing

Host your own website on a common SD/MMC card with this compact Webserver In a Box (WIB). It connects to the Internet via your modem/router and features inbuilt HTTP server, FTP server, SMT email client, dynamic DNS client, RS232 interface along with four digital outputs and four analogue inputs. Requires a SD memory card, some SMD soldering and a 6-9VDC power adaptor. Kit includes PCB, case and electronic components.



**BEST SELLER**

Order online: [www.jaycarelectronics.co.uk](http://www.jaycarelectronics.co.uk)

**Jaycar**  
Electronics



<b>4000 Series</b>		74HC157	£0.22	74LS368	£0.21	OP495GP	£8.69	<b>Diodes</b>		BC225	£0.15	BU208A	£1.53
4000B	£0.27	74HC158	£0.23	74LS373	£0.43	RC4136	£1.00	1N914	£0.05	2N5060	£0.19	BU237B	£1.40
4001B	£0.16	74HC161	£0.27	74LS374	£0.43	SG3524N	£0.82	1N4001	£0.05	2N5061	£0.19	BU237B	£1.40
4002B	£0.19	74HC162	£0.45	74LS375	£0.43	SG3543A	£6.88	1N4002	£0.05	2N5062	£0.19	BU237B	£1.40
4003B	£0.19	74HC163	£0.45	74LS376	£0.43	SG3543A	£6.88	1N4003	£0.05	2N5063	£0.19	BU237B	£1.40
4009UB	£0.23	74HC164	£0.20	74LS390	£0.34	SSM2141P	£2.21	1N4004	£0.03	2N5064	£0.19	BU237B	£1.40
4010B	£0.23	74HC165	£0.26	74LS393	£0.33	SSM2142P	£6.16	1N4005	£0.04	2N5065	£0.19	BU237B	£1.40
4011B	£0.16	74HC173	£0.38	74LS395	£0.26	SSM2143P	£3.78	1N4006	£0.04	2N5066	£0.19	BU237B	£1.40
4012B	£0.16	74HC174	£0.27	<b>74 Series</b>		TBA1205	£1.04	1N4007	£0.03	2N5067	£0.19	BU237B	£1.40
4013B	£0.18	74HC175	£0.35	7407	£0.40	TBA800	£0.75	1N4008	£0.03	2N5068	£0.19	BU237B	£1.40
4014B	£0.30	74HC193	£0.39	<b>Linear ICs</b>		TBA820M	£0.53	1N4009	£0.03	2N5069	£0.19	BU237B	£1.40
4015B	£0.27	74HC195	£0.32	AD524AD	£23.04	TDA1170S	£4.80	1N4010	£0.03	2N5070	£0.19	BU237B	£1.40
4016B	£0.20	74HC240	£0.32	AD548JN	£2.48	TDA2003V	£1.25	1N4011	£0.08	2N5071	£0.19	BU237B	£1.40
4017B	£0.26	74HC241	£0.37	AD590JH	£5.28	TDA2030AV	£1.24	1N4012	£0.08	2N5072	£0.19	BU237B	£1.40
4018B	£0.25	74HC244	£0.40	AD595AQ	£13.92	TDA2050V	£2.51	1N4013	£0.09	2N5073	£0.19	BU237B	£1.40
4019B	£0.25	74HC245	£0.34	AD620AN	£9.88	TDA2611A	£1.88	1N4014	£0.10	2N5074	£0.19	BU237B	£1.40
4020B	£0.31	74HC251	£0.30	AD625JN	£16.20	TDA2822A	£0.79	1N4015	£0.10	2N5075	£0.19	BU237B	£1.40
4021B	£0.22	74HC253	£0.25	AD635JN	£5.93	TDA2853A	£2.99	1N4016	£0.10	2N5076	£0.19	BU237B	£1.40
4022B	£0.38	74HC257	£0.25	AD648JN	£2.57	TED3718DP	£5.03	1N4017	£0.10	2N5077	£0.19	BU237B	£1.40
4023B	£0.23	74HC259	£0.25	AD711JN	£1.97	TEA5115	£3.11	1N4018	£0.10	2N5078	£0.19	BU237B	£1.40
4024B	£0.22	74HC273	£0.32	AD736JN	£5.80	TL061C	£0.21	1N4019	£0.10	2N5079	£0.19	BU237B	£1.40
4025B	£0.20	74HC299	£0.29	AD797AN	£7.25	TL064CN	£0.29	1N4020	£0.10	2N5080	£0.19	BU237B	£1.40
4026B	£0.67	74HC365	£0.28	AD811CN	£6.00	TL072CN	£0.20	1N4021	£0.10	2N5081	£0.19	BU237B	£1.40
4027B	£0.21	74HC367	£0.38	AD812AN	£6.32	TL081CN	£0.17	1N4022	£0.10	2N5082	£0.19	BU237B	£1.40
4028B	£0.21	74HC368	£0.35	AD820AN	£3.41	TL082CN	£0.32	1N4023	£0.10	2N5083	£0.19	BU237B	£1.40
4029B	£0.17	74HC374	£0.34	AD822AN	£4.27	TL084CN	£0.37	1N4024	£0.10	2N5084	£0.19	BU237B	£1.40
4030B	£0.31	74HC390	£0.37	AD829JN	£6.41	TL7705ACP	£0.82	1N4025	£0.09	2N5085	£0.19	BU237B	£1.40
4035B	£0.24	74HC393	£0.36	AD830AN	£5.44	TL7705ACP	£0.82	1N4026	£0.09	2N5086	£0.19	BU237B	£1.40
4040B	£0.31	74HC393	£0.36	AD847JN	£5.95	TL7705ACP	£0.82	1N4027	£0.09	2N5087	£0.19	BU237B	£1.40
4041B	£0.19	74HC563	£0.56	AD9696KN	£7.73	TL7705ACP	£0.82	1N4028	£0.09	2N5088	£0.19	BU237B	£1.40
4042B	£0.35	74HC574	£0.37	AD9696KN	£7.73	TL7705ACP	£0.82	1N4029	£0.09	2N5089	£0.19	BU237B	£1.40
4043B	£0.42	74HC595	£0.20	AD9696KN	£7.73	TL7705ACP	£0.82	1N4030	£0.09	2N5090	£0.19	BU237B	£1.40
4046B	£0.25	74HC597	£0.22	AD9696KN	£7.73	TL7705ACP	£0.82	1N4031	£0.09	2N5091	£0.19	BU237B	£1.40
4048B	£0.34	74HC688	£0.46	AD9696KN	£7.73	TL7705ACP	£0.82	1N4032	£0.09	2N5092	£0.19	BU237B	£1.40
4049B	£0.29	74HC697	£0.46	AD9696KN	£7.73	TL7705ACP	£0.82	1N4033	£0.09	2N5093	£0.19	BU237B	£1.40
4049UB	£0.17	74HC701	£0.31	AD9696KN	£7.73	TL7705ACP	£0.82	1N4034	£0.09	2N5094	£0.19	BU237B	£1.40
4050B	£0.17	74HC702	£0.31	AD9696KN	£7.73	TL7705ACP	£0.82	1N4035	£0.09	2N5095	£0.19	BU237B	£1.40
4051B	£0.23	74HC703	£0.31	AD9696KN	£7.73	TL7705ACP	£0.82	1N4036	£0.09	2N5096	£0.19	BU237B	£1.40
4052B	£0.32	74HC704	£0.31	AD9696KN	£7.73	TL7705ACP	£0.82	1N4037	£0.09	2N5097	£0.19	BU237B	£1.40
4053B	£0.20	74HC705	£0.31	AD9696KN	£7.73	TL7705ACP	£0.82	1N4038	£0.09	2N5098	£0.19	BU237B	£1.40
4054B	£0.56	74HC705	£0.31	AD9696KN	£7.73	TL7705ACP	£0.82	1N4039	£0.09	2N5099	£0.19	BU237B	£1.40
4055B	£0.34	74HC705	£0.31	AD9696KN	£7.73	TL7705ACP	£0.82	1N4040	£0.09	2N5100	£0.19	BU237B	£1.40
4060B	£0.17	74HC706	£0.31	AD9696KN	£7.73	TL7705ACP	£0.82	1N4041	£0.09	2N5101	£0.19	BU237B	£1.40
4063B	£0.41	74HC707	£0.31	AD9696KN	£7.73	TL7705ACP	£0.82	1N4042	£0.09	2N5102	£0.19	BU237B	£1.40
4066B	£0.22	74HC708	£0.31	AD9696KN	£7.73	TL7705ACP	£0.82	1N4043	£0.09	2N5103	£0.19	BU237B	£1.40
4068B	£0.19	74HC709	£0.31	AD9696KN	£7.73	TL7705ACP	£0.82	1N4044	£0.09	2N5104	£0.19	BU237B	£1.40
4069UB	£0.18	74HC710	£0.31	AD9696KN	£7.73	TL7705ACP	£0.82	1N4045	£0.09	2N5105	£0.19	BU237B	£1.40
4070B	£0.15	74HC711	£0.31	AD9696KN	£7.73	TL7705ACP	£0.82	1N4046	£0.09	2N5106	£0.19	BU237B	£1.40
4071B	£0.20	74HC712	£0.31	AD9696KN	£7.73	TL7705ACP	£0.82	1N4047	£0.09	2N5107	£0.19	BU237B	£1.40
4072B	£0.25	74HC713	£0.31	AD9696KN	£7.73	TL7705ACP	£0.82	1N4048	£0.09	2N5108	£0.19	BU237B	£1.40
4073B	£0.17	74LS00	£0.28	AD9696KN	£7.73	TL7705ACP	£0.82	1N4049	£0.09	2N5109	£0.19	BU237B	£1.40
4075B	£0.17	74LS01	£0.14	AD9696KN	£7.73	TL7705ACP	£0.82	1N4050	£0.09	2N5110	£0.19	BU237B	£1.40
4076B	£0.30	74LS02	£0.15	AD9696KN	£7.73	TL7705ACP	£0.82	1N4051	£0.09	2N5111	£0.19	BU237B	£1.40
4078B	£0.28	74LS03	£0.21	AD9696KN	£7.73	TL7705ACP	£0.82	1N4052	£0.09	2N5112	£0.19	BU237B	£1.40
4079B	£0.30	74LS04	£0.21	AD9696KN	£7.73	TL7705ACP	£0.82	1N4053	£0.09	2N5113	£0.19	BU237B	£1.40
4081B	£0.13	74LS05	£0.14	AD9696KN	£7.73	TL7705ACP	£0.82	1N4054	£0.09	2N5114	£0.19	BU237B	£1.40
4082B	£0.21	74LS08	£0.19	AD9696KN	£7.73	TL7705ACP	£0.82	1N4055	£0.09	2N5115	£0.19	BU237B	£1.40
4085B	£0.28	74LS09	£0.15	AD9696KN	£7.73	TL7705ACP	£0.82	1N4056	£0.09	2N5116	£0.19	BU237B	£1.40
4086B	£0.33	74LS10	£0.27	AD9696KN	£7.73	TL7705ACP	£0.82	1N4057	£0.09	2N5117	£0.19	BU237B	£1.40
4093B	£0.16	74LS11	£0.17	AD9696KN	£7.73	TL7705ACP	£0.82	1N4058	£0.09	2N5118	£0.19	BU237B	£1.40
4094B	£0.29	74LS12	£0.25	AD9696KN	£7.73	TL7705ACP	£0.82	1N4059	£0.09	2N5119	£0.19	BU237B	£1.40
4098B	£0.40	74LS14	£0.36	AD9696KN	£7.73	TL7705ACP	£0.82	1N4060	£0.09	2N5120	£0.19	BU237B	£1.40
4099B	£0.35	74LS15	£0.24	AD9696KN	£7.73	TL7705ACP	£0.82	1N4061	£0.09	2N5121	£0.19	BU237B	£1.40
4502B	£0.32	74LS20	£0.27	AD9696KN	£7.73	TL7705ACP	£0.82	1N4062	£0.09	2N5122	£0.19	BU237B	£1.40
4503B	£0.40	74LS21	£0.20	AD9696KN	£7.73	TL7705ACP	£0.82	1N4063	£0.09	2N5123	£0.19	BU237B	£1.40
4508B	£1.40	74LS26	£0.25	AD9696KN	£7.73	TL7705ACP	£0.82	1N4064	£0.09	2N5124	£0.19	BU237B	£1.40
4510B	£0.45	74LS27	£0.25	AD9696KN	£7.73	TL7705ACP	£0.82	1N4065	£0.09	2N5125	£0.19	BU237B	£1.40
4511B	£0.30	74LS32	£0.23	AD9696KN	£7.73	TL7705ACP	£0.82	1N4066	£0.09	2N5126	£0.19	BU237B	£1.40
4512B	£0.30	74LS37	£0.23	AD9696KN	£7.73	TL7705ACP	£0.82	1N4067	£0.09	2N5127	£0.19	BU237B	£1.40
4515B	£0.39	74LS38	£0.23	AD9696KN	£7.73	TL7705ACP	£0.82	1N4068	£0.09	2N5128	£0.19	BU237B	£1.40
4516B	£0.44	74LS38	£0.18	AD9696KN	£7.73	TL7705ACP	£0.82	1N4069	£0.09	2N5129	£0.19	BU237B	£1.40
4518B	£0.42	74LS40	£0.14	AD9696KN	£7.73	TL7705ACP	£0.82	1N4070	£0.09	2N5130	£0.19	BU237B	£1.40
4520B	£0.34	74LS51	£0.24	AD9696KN	£7.73	TL7705ACP	£0.82	1N4071	£0.09	2N5131	£0.19	BU237B	£1.40
4521B	£0.68	74LS83	£0.38	AD9696KN	£7.73	TL7705ACP	£0.82	1N4072	£0.09	2N5132	£0.19	BU237B	£1.40
4526B	£0.40	74LS85	£0.48	AD9696KN	£7.73	TL7705ACP	£0.82	1N4073	£0.09	2N5133	£0.19	BU237B	£1.40
4527B	£0.40	74LS86	£0.25	AD9696KN	£7.73	TL7705ACP	£0.82	1N4074	£0.09	2N5134	£0.19	BU237B	£1.40
4529B	£0.44	74LS92	£0.45	AD9696KN	£7.73	TL7705ACP	£0.82	1N4075	£0.09	2N5135	£0.19	BU237B	£1.40
4532B	£0.24	74LS93	£0.44	AD9696KN	£7.73	TL7705ACP	£0.82	1N4076	£0.09	2N5136	£0.19	BU237B	£1.40
4536B	£1.00	74LS107	£0.30	AD9696KN	£7.73	TL7705ACP	£0.82	1N4077	£0.09	2N5137	£0.19	BU237B	£1.40
4538B	£0.26	74LS109	£0.21	AD9696KN	£7.73	TL7705ACP	£0.82	1N4078	£0.09	2N5138	£0.19	BU237B	£1.40
4541B	£0.33	74LS112	£0.24	AD9696KN	£7.73	TL7705ACP	£0.82	1N4079	£0.09	2N5139	£0.19	BU237B	£1.40
4555B	£0.32	74LS113	£0.23	AD9696KN	£7.73	TL7705ACP	£0.82	1N4080	£0.09	2N5140	£0.19	BU237B	



## Editorial Offices:

EVERYDAY PRACTICAL ELECTRONICS EDITORIAL  
Wimborne Publishing Ltd., 113 Lynwood Drive, Merley,  
Wimborne, Dorset, BH21 1UU

Phone: (01202) 873872. Fax: (01202) 874562.

Email: enquiries@epemag.wimborne.co.uk

Website: www.epemag.com

See notes on **Readers' Technical Enquiries** below – we regret technical enquiries cannot be answered over the telephone.

## Advertisement Offices:

Everyday Practical Electronics Advertisements  
113 Lynwood Drive, Merley, Wimborne, Dorset, BH21 1UU  
Phone: 01202 873872 Fax: 01202 874562

Email: stewart.earn@wimborne.co.uk

## Addressing the future

Just as we are getting used to using the Internet for everything from news and shopping to esoteric articles on alien abduction conspiracies, it seems we are about to run out of addresses. It's not that people can't dream up new 'www.thisismyuniqueaddress.com' destinations; no, the problem lies in the unsustainable rate at which we are devouring the limited amount of 'number' addresses that lie behind the Internet's basic structure.

All devices connected to the public Internet are given a unique number known as an Internet Protocol (IP) address. These consist of four numbers (in the range 0-255) separated by full stops, and which look like 127.0.0.1.

The 127.0.0.1-style system, known as IPv4, can supply around four billion addresses, which sounds a lot until you consider the huge and growing number of home and office computers, networks, mobile phones and all the other digital systems that need to be uniquely addressed. ISPs have delayed the address drought with techniques such as dynamic addressing, but the end is nigh for IPv4, with some commentators speculating that September next year will see the system serving up the last set of IPv4 addresses.

Fortunately, there is a plan B, called IPv6 (IPv5 was a dead end it seems). IPv6 will enable a jaw-dropping 340 trillion trillion trillion addresses. The good news is that most computer operating system suppliers have made their software IPv6 compliant (since XP for MS Windows and 10.3/Panther for Mac OSX aficionados). The bad news is that not all hardware is compliant, with devices such as Skype phones or printers listed as potential trouble spots. Big system changes are never problem free, so now might be a good time to check if your system is going to be affected.

*M. Min*

## AVAILABILITY

Copies of EPE are available on subscription anywhere in the world (see opposite) and from all UK newsagents (distributed by SEYMOUR). EPE can also be purchased from retail magazine outlets around the world. An Internet online version can be purchased and downloaded for just \$18.99US (approx £13) per year, available from [www.epemag.com](http://www.epemag.com)

## SUBSCRIPTIONS

Subscriptions for delivery direct to any address in the UK: 6 months £19.95, 12 months £37.90, two years £70.50; Overseas: 6 months £23.00 standard air service or £32.00 express airmail, 12 months £44.00 standard air service or £62.00 express airmail, 24 months £83.00 standard air service or £119.00 express airmail.

Online subscriptions, for downloading the magazine via the Internet, \$18.99US (approx £13) for one year available from [www.epemag.com](http://www.epemag.com).

Cheques or bank drafts (in £ sterling only) payable to Everyday Practical Electronics and sent to EPE Subs. Dept., Wimborne Publishing Ltd. 113 Lynwood Drive, Merley, Wimborne, Dorset BH21 1UU. Tel: 01202 873872. Fax: 01202 874562. Email: subs@epemag.wimborne.co.uk. Also via the Web at: [www.epemag.com](http://www.epemag.com). Subscriptions start with the next available issue. We accept MasterCard, Maestro or Visa. (For past issues see the Back Issues page.)

## BINDERS

Binders to hold one volume (12 issues) are available from the above address. These are finished in blue PVC, printed with the magazine logo in gold on the spine. Price £7.95 plus £3.50 p&p (for overseas readers the postage is £6.00 to everywhere except Australia and Papua New Guinea which cost £10.50). Normally sent within seven days, but please allow 28 days for delivery – more for overseas.

Payment in £ sterling only please. Visa, Maestro and MasterCard accepted. Send, fax or phone your card number, card expiry date, valid from date and card security code (the last 3 digits on or just under the signature strip), with your name, address etc. Or order on our secure server via our UK website. **Overseas customers** – your credit card will be charged by the card provider in your local currency at the existing exchange rate.

## VOL. 39 No. 7 JULY 2010

Editor: MATT PULZER

Consulting Editor: DAVID BARRINGTON

Subscriptions: MARILYN GOLDBERG

General Manager: FAY KEARN

Editorial/Admin: (01202) 873872

Advertising and Business Manager:

STEWART KEARN (01202) 873872

On-line Editor: ALAN WINSTANLEY

EPE Online (Internet version) Editors:

CLIVE (Max) MAXFIELD and ALVIN BROWN

Publisher: MIKE KENWARD

## READERS' TECHNICAL ENQUIRIES

Email: techdept@epemag.wimborne.co.uk

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years' old. Letters requiring a personal reply must be accompanied by a stamped self-addressed envelope or a self-addressed envelope and international reply coupons. We are not able to answer technical queries on the phone.

## PROJECTS AND CIRCUITS

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it.

A number of projects and circuits published in EPE employ voltages that can be lethal. You should not build, test, modify or renovate any item of mains-powered equipment unless you fully understand the safety aspects involved and you use an RCD adaptor.

## COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers.

We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

## ADVERTISEMENTS

Although the proprietors and staff of EVERYDAY PRACTICAL ELECTRONICS take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are bona fide, the magazine and its publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or in inserts. The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture.

## TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT

We advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the UK. Readers should check the law before buying any transmitting or telephone equipment, as a fine, confiscation of equipment and/or imprisonment can result from illegal use or ownership. The laws vary from country to country; readers should check local laws.





# NEWS

A roundup of the latest Everyday  
News from the world of  
electronics



## The dock is dead, long live wireless! By Barry Fox

According to Joseph Liow, VP Personal Digital Entertainment Products at Californian company Creative Labs, 'Docking speakers are dead. Say goodbye to them. Wireless speakers are in.'

Creative is hoping to redefine wireless connection with a two-pronged strategy; simplify Bluetooth pairing and use a different audio coding system to improve sound quality and reduce latency, the delay usually caused by Bluetooth coding and decoding.

Conventional Bluetooth wireless links, as now standard with portable music players and cellphones, can be tricky to set up. The user must set the devices to search for each other, then enter a pass code to authorise temporary connection and push keys to confirm permanent connection. Different devices may use different codes (such as 0000, 1234 or 12345), which adds to the

difficulty; sometimes the codes must be entered very rapidly to work; and some devices just stubbornly refuse to pair.

The mandatory standard for transmitting stereo by Bluetooth is the A2DP codec (Advanced Audio Distribution Profile) which has limited audio quality and delays the sound, which spoils lip sync for TV and video sound. Creative is using the apt-x coding system, developed around 1990 by Belfast-based company apt-x for professional use, and now permitted as an optional standard for Bluetooth. Audio is transparently delivered over the Bluetooth link, whether it is stored uncompressed or in a compression format (MP3, AAC, FLAC). Low latency means the signal is not noticeably delayed.

Creative is now launching a range of wireless speaker kits worldwide, which use a Bluetooth transmitter dongle that plugs

into an iPod (except the Shuffle), iPhone or iPad, or any laptop or netbook USB socket that supports Bluetooth A2DP. The dongle then transmits an apt-x stream at 768kbps to a matching receiver in the speaker. The source player controls the speaker volume.

'It's super easy and super hassle-free' said Creative's Marcom Director Mac Aw Kum Weng, before proving the point at a London demonstration by plugging a dongle into a new iPad and getting near instantaneous connection to one of Creative's new speakers.

Creative is launching four speaker systems between now and July, ranging in price from around £50 to £250. Dongles cost £35. The speakers can also be used with portables that do not have a standard iPod 30-pin socket or USB port. But the connection is then in ordinary Bluetooth A2DP mode, with conventional pairing.

## New technology used to unearth crucial information about historic photographs

A wealth of vital information about the early days of photography could be unearthed by a computer program which mimics human decision-making.

De Montfort University Leicester (DMU) has amassed a collection of hundreds of exhibition catalogues containing invaluable information about individual photographs, but the images themselves are missing as the catalogues were printed before the technology existed to reproduce pictures alongside the descriptions.

DMU's Professor Stephen Brown and Professor Robert John are investigating a form of computational intelligence known as fuzzy logic to see if it is possible to match these catalogue entries with photographs in online collections owned by museums.

Professor Brown, of the Faculty of Art and Design, said: 'Many of the photographs in question appear to have survived and are increasingly accessible online through museum and gallery websites. However, precise associations between particular exhibits and images are not always clear.'

Software using fuzzy logic is able to suggest possible connections based on vague

information. It mimics the human approach to problem solving, but arrives at a decision much more quickly than people do.

Uniting the catalogue records with their original photographs would provide researchers with an important primary resource.

Professor Stephen Brown said: 'Photographic history research is important in a range of areas of study, including social, political, economical, scientific and architectural studies.'

'For example, Sir Benjamin Stone, who was MP for Birmingham, was a keen photographer and collector. He was able to photograph many leading scientists, politicians and dignitaries and significant historical and royal occasions – such as Queen Victoria's funeral.'

Professor Robert John, Head of the Centre for Computational Intelligence and a world-leading expert in fuzzy logic, said: 'Using fuzzy logic will allow photographs to be analysed and compared with the catalogue information very quickly.'

'The benefits of this type of technology are that it can make decisions much more quickly than humans and it is not restricted to a simple 'match'/'no match' answer.'

In straightforward cases, photographs and catalogue information could be matched by name, title and other details, however, the majority of cases are more complicated.

Professor Brown added: 'Some of the records in the catalogues are rather vague. For instance, you might have the name, but the only address given is 'London'. If a photograph is then found with the same name, but the photographer's address is given as 'Blackheath' then is that the same person? It could well be, but further examination is needed.'

'We could get a group of photographic experts to examine the images and the catalogue entries in order to match them up, but it would take years and be prohibitively expensive.'

Researchers will first carry out an exploratory study to investigate the potential of using fuzzy logic to match images with the descriptions in the catalogues.

If it proves to be a success, researchers hope it will be extended to a full project which will see online photo collections from museums and galleries around the world scanned for possible matches.

DMU has two online collections of catalogue records from photographic exhibitions:

- Photographic Exhibitions in Britain 1839 to 1865 – see <http://peib.dmu.ac.uk>
- Exhibitions of the Royal Photographic Society 1870 to 1915 – see <http://erps.dmu.ac.uk>

## Could you be an unusual suspect?

Following on from last month's item about file sharing, the consumer magazine *Which?* has issued advice on insecure home networks.

'Make sure you secure the wireless network on your internet connection', says *Which? Computing*, 'or you could end up as one of the 'unusual suspects' – people who have been wrongly accused of illegal file sharing'.

Thousands of letters have been sent by law firms to people who, the lawyers claim, have illegally uploaded their clients' copyrighted material onto the internet. These include 80-year-olds accused of sharing techno music and young mums accused of uploading gay pornography.

*Which?* has been highly critical of law firms who employ this practice and is campaigning so that the volume litigation approach to file sharing is stopped. The consumer champion believes that legal action should not be used as a first response, but reserved for the most serious offenders.

In the meantime, an estimated 7.8 million UK households have unsecured wireless networks. Anyone with a WiFi enabled device could piggyback onto this connection without the account holder's knowledge. Any illegal activity could see the finger of blame pointed squarely at the owner of the wireless network.

*Which? Computing* thinks it's a good idea that internet users secure their connection, even though they are not obliged to, and has published advice on how to achieve this.

Peter Vicary-Smith, chief executive, *Which?*, says:

'*Which?* continues to battle law firms that threaten innocent consumers, but people also need to take steps to protect themselves. We urge anyone with a wireless network to secure it immediately. If they don't, they could end up in the awful position of being accused of a crime they haven't committed and, in some cases, wouldn't even know how to commit.'

## Samsung's newest baby



Samsung Electronics has announced the launch of the world's smallest monochrome laser printer. The ML-1665 fits easily into a small business or home office environment and its environmentally-friendly features make this compact printer perfect for environmentally aware students, home office and small office users.

At just 341 x 224 x 184mm (13.4in x 8.8in x 7.2in) it may be tiny, but it packs a punch, with up to 1200 x 600dpi effective output and up to 16ppm in A4.

## Car hacking – a real threat



Yes, you read that correctly, 'car hacking', not 'car jacking'. A report, *Experimental Security Analysis of a Modern Automobile*, from the The Center for Automotive Embedded Systems Security (a collaboration between researchers at the University of California San Diego and the University of Washington) has expressed concern about the cyber security of modern cars.

The report states, 'Modern automobiles are no longer mere mechanical devices; they are pervasively monitored and controlled by dozens of digital computers coordinated via internal vehicular networks. While this transformation has driven major advancements in efficiency and safety, it has also introduced a range of new potential risks.'

The authors continue, '... we experimentally evaluated these issues on a modern automobile and demonstrated the fragility of the underlying system structure. We demonstrated that an attacker who is able to infiltrate virtually any electronic control unit

(ECU) can leverage this ability to completely circumvent a broad array of safety-critical systems. Over a range of experiments, both in the lab and in road tests, we demonstrated the ability to adversarially control a wide range of automotive functions and completely ignore driver input – including disabling the brakes, selectively braking individual wheels on demand, stopping the engine, and so on.

'We found that it is possible to bypass rudimentary network security protections within the car, such as maliciously bridging between our car's two internal subnets.' The authors also highlighted 'composite attacks that leverage individual weaknesses, including an attack that embeds malicious code in a car's telematics unit and that will completely erase any evidence of its presence after a crash.'

Fortunately, the report's authors give advice on 'addressing these vulnerabilities while considering the existing automotive ecosystem.'

## HP builds a 'memristor'

Researchers at HP Labs have solved a decades-old mystery by proving the existence of a fourth basic element in integrated circuits that could make it possible to develop computers that turn on and off like an electric light.

The memristor – short for memory resistor – could make it possible to develop far more energy-efficient computing systems with memories that retain information even after the power is off, so there's no wait for the system to boot up after turning the computer on. It may even be possible to create systems with some of the pattern-matching abilities of the human brain.

Leon Chua, who first described and named the memristor, argued that it should be included with the resistor, capacitor and inductor as the fourth fundamental circuit element, since it has properties that cannot be duplicated by any combination of the other three.

## Nature by Numbers



True enough, this is not about electronics, but I am quite certain that anyone who is interested in how the world works – and that must mean *EPE* readers – will be captivated by this short film on YouTube.

*Nature by Numbers* examines the occurrence of the Fibonacci sequence and Golden Ratio as fundamental mathematical building blocks in nature. Beautifully crafted and free to view, this lovely little film is available at: [www.youtube.com/watch?v=kkGeOWYOFoA](http://www.youtube.com/watch?v=kkGeOWYOFoA). Well worth four minutes of your time.



Reduce the possibility of a drowning in your swimming pool – if someone falls in, an excruciatingly loud siren sounds.

Build this

# SWIMMING POOL ALARM

by JOHN CLARKE

**S**WIMMING POOLS are dangerous places, especially for toddlers – as the table above right chillingly shows. And the pool in your own backyard is certainly not exempt; in fact, statistics show that's where more than half of all toddler drownings occur.

Even while taking the photographs for this article, with mother millimetres out of shot and grandfather (Ross) in front taking the picture, 14-month-old Keira (who cannot swim) needed no prompting to attempt to get in the

pool – not once, but again and again.

While swimming pools these days must be fenced off, there is always the possibility that a toddler will find a way in. That can be as simple as a gate not latching properly or a determined youngster climbing the fence.

So while fences may appear to make a pool secure, they are never foolproof. A secondary defence, one that warns if someone falls into the pool, can literally be the difference between life and death.

A way to add secondary safety is with a pool alarm. The type of pool alarm

described here monitors the amount of pool water movement and sounds an alarm when this exceeds a preset level.

Of course, wind can also create movement in the pool water – after all, that's what makes waves in the ocean. The last thing you want is false alarms – remember the boy who cried 'wolf'?

The Pool Alarm can be set to a level which ignores typical wind movement but screams its head off when that level is exceeded – ie, someone falls in.





### Here's why your pool needs this swimming pool alarm – some sobering facts about toddler (0-5yrs) drownings\*:

- 41% occur in swimming pools (virtually all in backyard pools)
- 60% occur in the toddler's own home
- 70% occur in metropolitan areas
- 40% occur during school hours (38% 3-6pm and 20% 6-9pm)
- 66% are boys
- 60% are either one or two years old



\* From NSW Water Safety Task Force Report, 2002

### FEATURES....

- Monitors wave height caused by any disturbance in the pool
- Adjustable quiescent and alarm wave levels
- Adjustable alarm period
- Pushbutton switch for Hold/Monitor modes
  - Hold mode gives visual but silent alarm (for testing and attended pool use)
  - Monitor mode for visual and audible alarm (for unoccupied pool use)
- Automatic return to Monitor mode after pool water settles
- Adjustable return to Monitor period
- Optional Set-to-Hold mode with pool turbulence preventing false alarms
- Indications of Hold, Status and Alarm conditions
- Weatherproof housing
- Can drive two alarm sirens
- Plugpack-powered
- Suits all pools where the top water level is below the pool edge



## Constructional Project

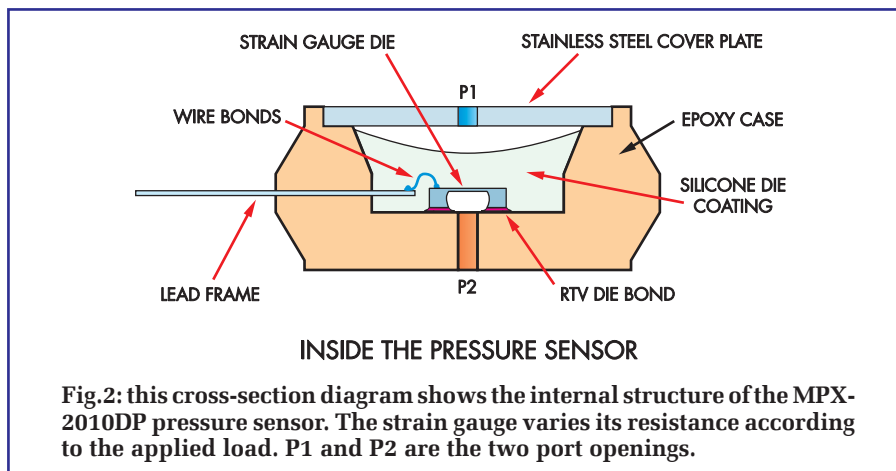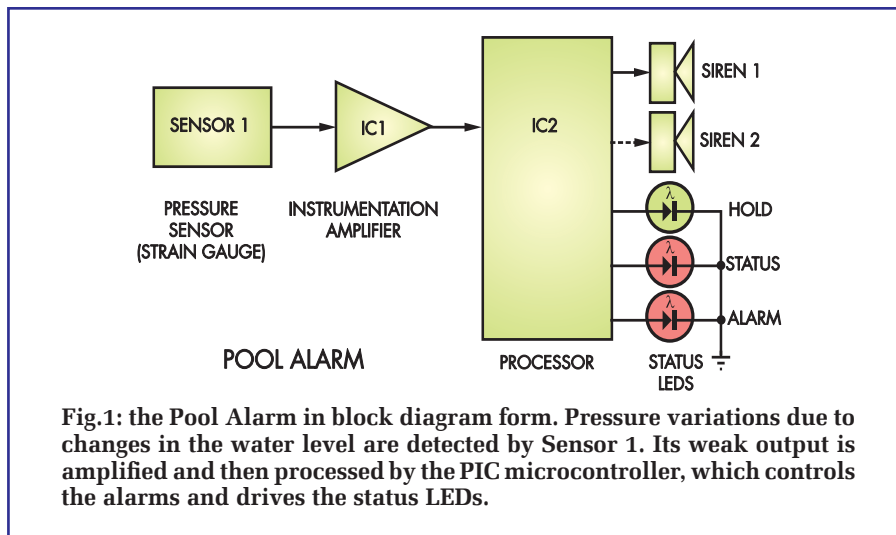

### How it works

OK, let's see how it works. Fig.1 shows the block diagram of the Pool Alarm. It uses a pressure sensor to detect sudden increases in water depth, as happens when an object falls into the pool creating waves.

The unit is built in two sections, each in a weatherproof box. One houses the sensor, while a second, which we have dubbed the Pool Alarm box, houses the PIC-controlled alarm circuit. The two are connected via a 4-way cable.

While our photo shows the alarm box on the side of the pool, this would not be a typical installation. Rather, the Pool Alarm box would normally be located close to the filter box (where mains power is available) or more likely in the house, if the pool is reasonably close. The cable can be run underground across to the pool sensor box.

Inside the sensor box is a pressure sensor. This measures the water pressure variations in the pool due to waves, and sets off an alarm if these variations

reach a preset level. The sensor box has a thin tube emerging from it. The box is placed so that the probe tip is about 60mm to 90mm under water. This sensor box can be secured to a pool ladder or fixed to the side of the pool, as we have shown in our photos.

The pool alarm is plugpack-powered, so it needs to be located near to the mains. Complete safety from the mains power is provided first by the isolation given by the plugpack and second, by the fact that there is no electrical contact with the water itself.

### Additional features

Our Pool Alarm has several features worth noting. Most prominent on the main alarm box is a weatherproof pushbutton 'Hold' switch. This is used to set the operating mode of the alarm. When powered up, the alarm is initially set to its normal monitor mode, where it checks for pool wave movement. It takes about 10 seconds after power up to begin monitoring, and during this

time, the green 'Hold' LED remains lit. After the 10 seconds, the LED flashes briefly every 1.5 seconds, indicating that the alarm is in the monitor mode.

If the alarm senses that the pool wave movement is sufficient, it will sound the alarm. The alarm period can be varied from between zero and five minutes, with typical settings around the 30s to 3-minute range. During the alarm period, an Alarm LED flashes on and off at five times per second.

The alarm siren can be stopped at any time by pressing the Hold switch. This will also stop the Alarm LED flashing. The Hold LED will also stop flashing, but unlike the Alarm LED, it will remain constantly on. The Pool Alarm is now in the Hold mode, where the alarm will not sound.

However, the Alarm LED will flash whenever wave movement is above the alarm threshold. The hold mode is used when the pool is in use.

### Wave movement

The degree of wave movement required to set off the alarm can be calibrated to suit your pool. This is done by dropping a weighted bucket into the pool (simulating a small child falling into the water) and pressing the alarm level switch (on the PC board). The Pool Alarm will monitor the wave movement over a 10s period, and set up the level required for the alarm. During this calibration period, a 'Status' LED will be lit.

A second quiescent level can also be calibrated into the Pool Alarm. This level is the wave movement within the pool when no-one is in it, but with a light breeze blowing and perhaps the filter running (normal filter running should not trigger the alarm).

In practice, the level is calibrated under these conditions (ie, when a reasonable wind is blowing) by pressing the Quiescent Level calibration switch. The alarm then monitors wave movement for 10 seconds and stores the level. During this calibration period, the Status LED is lit.

Quiescent level calibration allows the Pool Alarm to provide extra features. First, it allows the mode to return from the Hold to the monitor mode automatically. So when the pool is being used, the Hold switch is pressed to set the Pool Alarm to the Hold mode so that the alarm will not sound. However, during this time, the alarm continues to monitor the wave movement. Typically,



Here are the three main elements of the Pool Alarm. At left, actually shown upside-down, is the sensor with the open-ended tube emerging from a cable gland. Centre is the alarm proper, housed in a waterproof box so it can be mounted outside near the pool if you wish. At right is a commercial strobe/siren, which is triggered when a large enough wave occurs in the pool, ie, when someone falls in!

during pool use, the wave movement will continue to be over the quiescent level and the alarm will remain in the Hold mode.

When the pool is not in use, wave movement within the pool will settle to below the quiescent level. In this case, the alarm will change from Hold mode to Monitor mode, after a preset period of 'no pool' activity. The period of inactivity can be adjusted to allow for the way the pool is used.

If the pool is often vacant for a short time before it is used again, the period can be made sufficiently long to prevent the return to Monitor happening in that time period. The adjustment range is from 1.25 to 75 minutes. One setting prevents the monitor return function.

The change from Hold to Monitor and from Monitor to Hold can also be toggled with the Hold pushbutton switch. The Hold LED then flashes for Monitor and is continuously lit for the Hold mode.

During the monitoring mode, windy conditions may cause wave movement that could exceed the quiescent level but may be below the alarm level. The Pool Alarm has an option that can return it to the Hold mode if

the quiescent level is exceeded for 30 seconds without the alarm level being exceeded. This feature is included to prevent false alarms from the siren in windy weather. The Pool Alarm will then return to the monitoring mode after the wave movement has reduced to below the quiescent level.

Should the alarm sound and time out before the Hold switch is pressed, the alarm will return to Hold after the alarm period expires. The 'return to hold' option can be enabled or disabled with a jumper pin selection.

Just which option you select depends on your pool and whether it is subject to windy conditions. Protected pools may not need the 'return-to-hold' feature. This is a compromise between preventing false alarms and providing continuous pool protection.

### Pressure sensor

An air-pressure sensor, the MPX-2010DP manufactured by Freescale Semiconductor, is used to measure wave movement. Its internal arrangement is shown in Fig.2. The sensor comprises a strain gauge that provides a resistance variation with applied load. In this case, the load is the air pressure exerted on the

gauge due to a tube inserted into the pool.

The sensor is called a differential type because it measures the difference in pressure between one port and the other. For our application, we use Port 1, which has a silicone gel protective layer to prevent moisture affecting the strain gauge element. Port 2 is left disconnected and is vented to the inside of the enclosure.

By the way, this is the same pressure sensor as used in the *PIC-Based Water Tank Level Meter*, described in the last three issues.


### Circuit description

The full circuit of the Pool Alarm is shown in Fig.2, and comprises the pressure sensor, an instrumentation amplifier and a PIC microcontroller, plus associated switches, LEDs and other components.

Sensor 1 has differential outputs at pins 2 and 4. With the same pressure at both ports, pins 2 and 4 are nominally at the same voltage; ie, 2.5V. If the pressure at port 1 increases compared to port 2, pin 2 rises and pin 4 falls. The change in voltage is quite small – around 1mV for a 1kPa pressure difference. However, the actual voltage change with typical wave movement is only around 200µV,



## Constructional Project

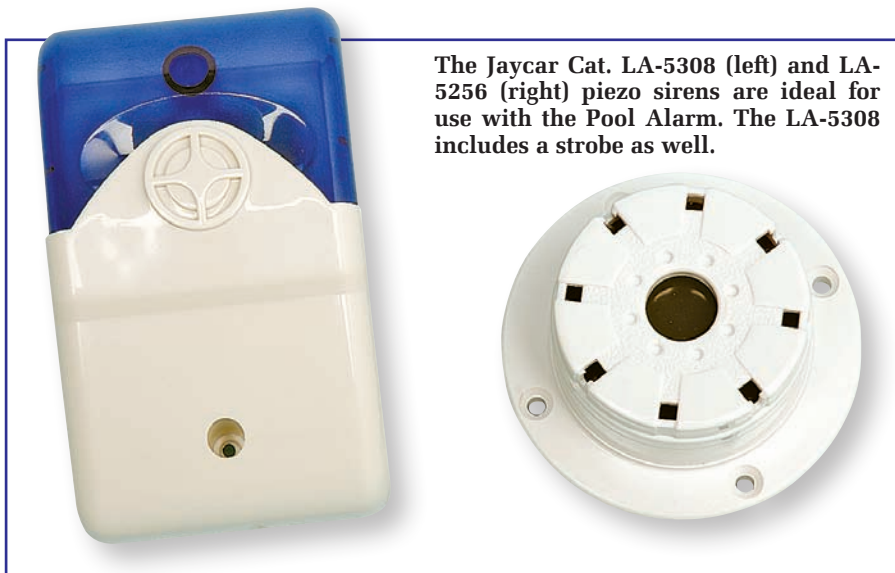

The Jaycar Cat. LA-5308 (left) and LA-5256 (right) piezo sirens are ideal for use with the Pool Alarm. The LA-5308 includes a strobe as well.

so we need to amplify this signal using instrumentation amplifier IC1.

Since we are concerned with wave movements (ie, pressure variations) rather than the absolute pressure levels, the output from the sensor is AC-coupled via  $1\mu\text{F}$  non-polarised capacitors to op amps IC1a and IC1b. The non-inverting inputs of IC1a and IC1b (pins 3 and 5 respectively) are biased via  $470\text{k}\Omega$  resistors to a  $+2.5\text{V}$  reference, derived using two  $2.2\text{k}\Omega$  resistors and a  $100\mu\text{F}$  capacitor.

IC1a and IC1b are set up as non-inverting amplifiers with  $39\text{k}\Omega$  feedback resistors and a single  $10\Omega$  resistor between their inverting inputs. A  $470\text{pF}$  capacitor across the  $39\text{k}\Omega$  resistors rolls off signals above about  $8.7\text{kHz}$ , and this prevents possible oscillation. The gains of IC1a and IC1b are each  $1 + 39\text{k}\Omega/10\Omega$ , or close enough to 3900.

The outputs of IC1a and IC1b are summed in differential amplifier IC1c, which effectively adds the two outputs together. IC1c's gain is  $2 \times 27\text{k}\Omega/22\text{k}\Omega$ , or 2.45 (for the two outputs), so the overall gain is  $3900 \times 2.45$  or 9555.

### Rain filtering

IC1c's output is filtered using a  $2.2\text{k}\Omega$  resistor and a  $10\mu\text{F}$  capacitor to remove high-frequency signals above  $7.2\text{Hz}$ . This prevents alarm triggering due to the detection of rain falling on the pool. IC1c also shifts the DC level of the output signal. This is done by feeding it with an offset voltage from IC1d, via the  $27\text{k}\Omega$  resistor from pin 14.

IC1d obtains its reference voltage from a pulse width modulated (PWM) signal from PIC micro IC2. This signal swings from  $0\text{V}$  to  $5\text{V}$  at a frequency of

$490\text{Hz}$ , and has a duty cycle of about 50%. The PWM signal is filtered using a  $220\text{k}\Omega$  resistor and a  $10\mu\text{F}$  capacitor, and is fed to pin 12 of IC1d.

The PWM signal is adjusted automatically during calibration so that IC1c's output is at  $2.5\text{V}$  when there is no signal from Sensor 1.

### Microcontroller functions

The PIC16F88-I/P microcontroller (IC2) processes the signal from IC1c and drives the alarm and the Hold, Status and Alarm LEDs. IC2 also monitors inputs at RB1, RB2 and RB3 for the switches, the linking options at RA2, the RB4 to RB7 inputs for BCD1 and the voltage at the wiper of trimpot VR1.

Output RA7 drives the flashing Alarm LED, while output RA6 drives transistors Q1 and Q2, which are the siren drivers.

Trimpot VR1 is monitored by the AN4 input and its wiper voltage is converted to a digital value from 0 to 255 for its  $0\text{V}$  to  $5\text{V}$  range, to give a timeout period in minutes. This value is placed in a counter that is decremented every  $1.18\text{s}$  until it reaches zero and the alarm goes off.

Hold switch S1 connects to the RB3 input, which is normally held high ( $+5\text{V}$ ) via an internal pull-up resistor. When S1 closes, IC2 responds by altering the mode from Hold to Monitor, or from Monitor to Hold. Output RA1 drives the Hold LED via a  $1\text{k}\Omega$  resistor.

Output RA0 drives Status LED 2 via a  $1\text{k}\Omega$  resistor. LED2 lights during the quiescent set and Alarm set procedures. If LED2 is flashing, it indicates levels that are over the quiescent setting.

Switches S2 (Quiescent Set) and S3 (Alarm Set) are monitored by the RB1

and RB2 inputs. Pressing S2 or S3 starts the program in IC2. This monitors the AN3 input and calculates the voltage range encountered for a period of  $10\text{s}$ .

It does this by monitoring the AN3 input every  $100\text{ms}$  and storing the level in memory. After sampling for  $10\text{s}$ , it finds the minimum and maximum values and subtracts the minimum from the maximum to derive the span range. This value is then multiplied by 95% for the Alarm level, and 105% for the Quiescent level. The lower alarm level provides for a small amount of leeway in pool movement to sound the alarm.

The higher quiescent setting of 105% is so that the quiescent level for the pool will normally be less than this. The resulting values are then used to check for quiescent or alarm levels at the AN3 input.

Whether or not to return to Hold from monitoring is selected with the linking at input RA2. RA2 is pulled high with the link in LK2 position and low with the link in LK1.

Rotary switch BCD1 selects the monitor return period. When BCD1 is in position 0, all the switches are open and the RB4 to RB7 inputs are pulled high via internal pull-up resistors. This setting is for a 'no-return to monitoring' from hold. Other settings of the BCD switch will pull at least one of the RB4-RB7 lines to ground via its common pin, and select a time period as shown in Table 3.

### PWM signal

As already noted, the CCP1 output at IC2 pin 6 produces the PWM signal. It is initially preset so that the output of IC1c is nominally at  $+2.5\text{V}$ . However, because of manufacturing tolerances in IC1, the output could vary and so there is a set-up procedure (to set the output to  $2.5\text{V}$ ).

Pressing switch S2 before power is applied to the circuit runs this procedure. The program within IC2 then adjusts the PWM percentage so that the reading at port AN3 is at  $+2.5\text{V}$ . This process takes about  $60\text{s}$ . The new PWM value is then stored and used every time the pool alarm is powered up.

IC2 operates at  $500\text{kHz}$  using an internal oscillator, and is run from a  $5\text{V}$  supply derived from regulator REG1.

### Software

The software files are available via the *EPE Library* site, accessed via [www.epemag.com](http://www.epemag.com). Pre-programmed PICs will also be available from Magenta


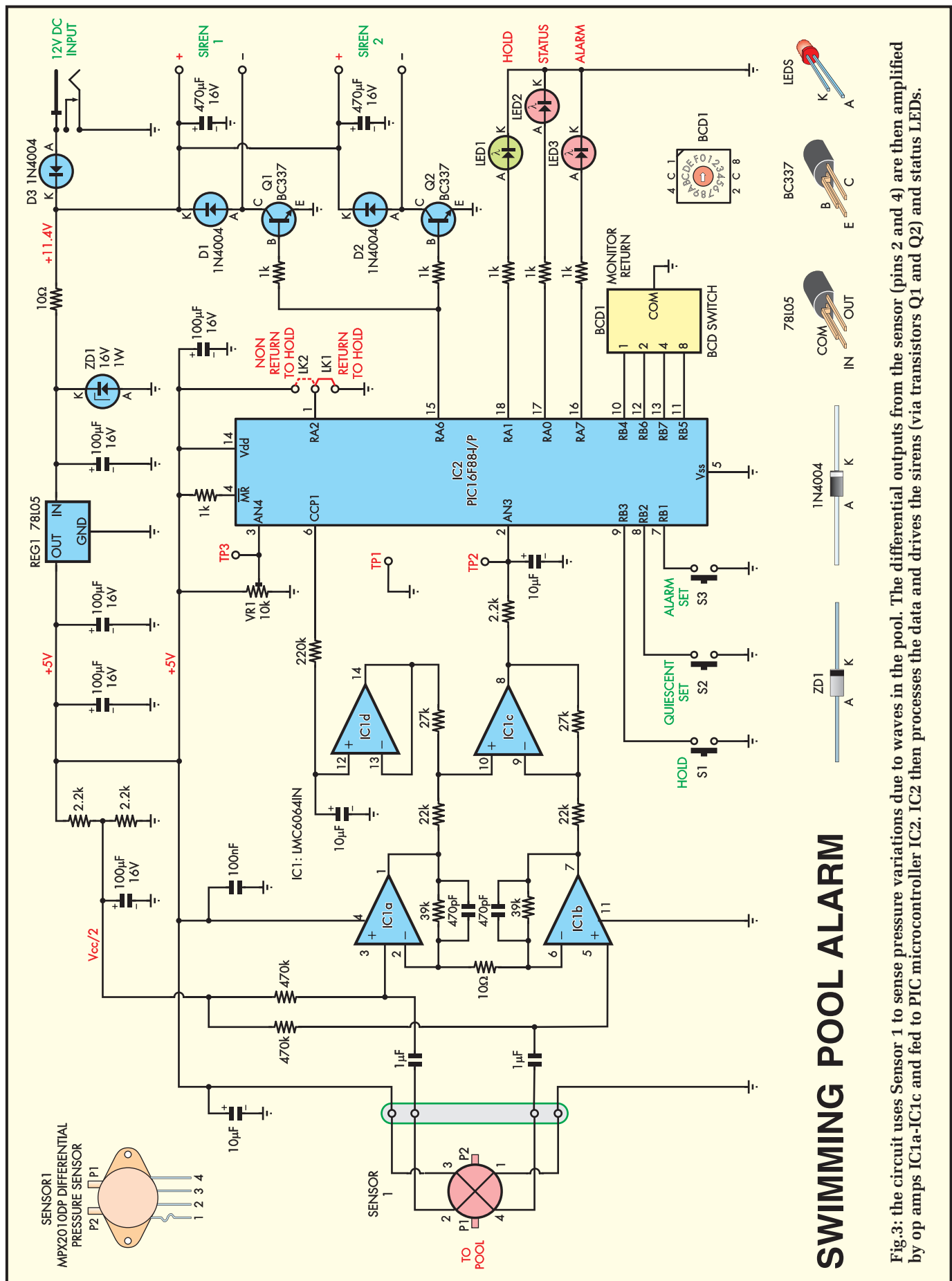


Fig.3: the circuit uses Sensor 1 to sense pressure variations due to waves in the pool. The differential outputs from the sensor (pins 2 and 4) are then amplified by op amps IC1a-IC1c and fed to PIC microcontroller IC2. IC2 then processes the data and drives the sirens (via transistors Q1 and Q2) and status LEDs.

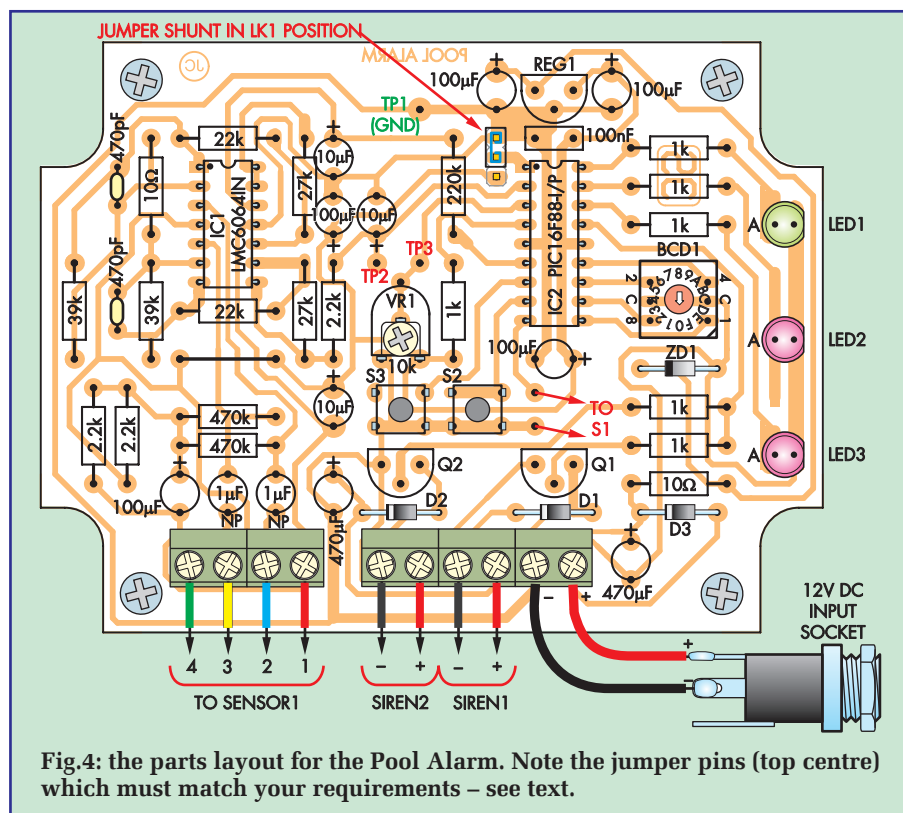

## Constructional Project



and the BCD switch (BCD1). **The correct orientation for BCD1 is with the dot to the lower right – see Fig.4.**

Switches S2 and S3 can be inserted next. These will only fit easily on the PC board with the correct orientation. Last, the screw terminals can be inserted. Note that the 6-way terminals are made up of three 2-way terminals that are interconnected using the moulded dovetails that attach the pieces together. The 4-way terminals are made using two 2-way terminals.

### Pool alarm box

Work can now be started on the main Pool Alarm box. First, drill a hole in the lid for S1, plus holes in the box for the cable glands for the sensor and siren wiring. You will also need a hole for the DC input socket.

That done, place the PC board in the box and secure it with four M3 × 6mm screws. You can now attach the panel label (see full-size artwork below Parts List) to the lid, install switch S1 and insert the neoprene seal that is pressed into the lid surround.

Next, wire up the DC socket to the screw terminals and wire switch S1 to the two terminals on the PC board. That done, connect a 12V DC plugpack to the DC socket and apply power. Check that there is +5V between pins 11 and 4 on IC1 and at pins 5 and 14 on IC2's socket. If the voltage is within the range of +4.75V to +5.25V, then power can be disconnected and IC2 installed in its socket.

Apply power again and measure the voltage between TP1 (GND) and TP2. **This should be about 2.5V, but if this differs by 0.25V, you will need to run the set-up to adjust TP2 to sit at 2.5V.** This needs to be done at a later stage when the pressure Sensor is connected.

### Sensor box assembly

The full assembly details for the Sensor box are shown in Fig.5.

First, a baseplate is made up using sheet aluminium measuring 31 × 26mm.

Electronics – see their advert in this issue for contact details.

### Construction

The Pool Alarm is built on a PC board, code 762, measuring 102mm × 77mm. This board is available from the *EPE PCB Service*.

The board is housed in an IP65 sealed polycarbonate enclosure with a clear lid (115mm × 90mm × 55mm). Similarly, the pressure sensor is housed in an IP65 sealed ABS case measuring 64mm × 58mm × 35mm.

The wiring details for the PC board are shown in Fig.4. Start the assembly by checking the PC board for any defects, such as shorted tracks and breaks in the copper. You should also check the hole sizes. The holes for the corner mounting screws need to be 3mm in diameter, while the holes for the screw

terminals need to be 1.2mm. Check also that the PC board will fit into the box.

Install the single wire link and the resistors first. Use the resistor colour code table as a guide to finding each value. Better still, use a digital multimeter (DMM) to check each resistor before installing it. That done, install the PC stakes for test points TP1 to TP3 and for the connections to S1, then fit the 3-way header for links LK1 and LK2.

Next, install diodes D1 to D3 and Zener diode ZD1. IC1 can now be mounted, but just insert and solder in the socket for IC2 at this stage. Both the IC and socket must be oriented correctly.

The capacitors can go in next. Note that the electrolytic types must be oriented with the correct polarity, as shown. Now install transistors Q1, Q2 and regulator REG1, taking care not to mix them up, then install trimpot VR1

**Table 1: Resistor Colour Codes**

	No.	Value	4-Band Code (1%)	5-Band Code (1%)
□	2	470kΩ	yellow violet yellow brown	yellow violet black orange brown
□	1	220kΩ	red red yellow brown	red red black orange brown
□	2	39kΩ	orange white orange brown	orange white black red brown
□	2	27kΩ	red violet orange brown	red violet black red brown
□	2	22kΩ	red red orange brown	red red black red brown
□	3	2.2kΩ	red red red brown	red red black brown brown
□	6	1kΩ	brown black red brown	brown black black brown brown
□	2	10Ω	brown black black brown	brown black black gold brown

This is then fitted with two M3 × 20mm screws and M3 nuts for the sensor, and attached to two central mounting posts in the box using M3 × 6mm screws.

That done, the sensor can be slipped onto its mounting screws (notched pin to the left) and secured using two more M3 nuts. Note that the sensor is oriented so that port 1 is the one that is connected to the tubing.

The wiring can now be connected to the four sensor pins, with the cable exiting through the adjacent end of the box via a cable gland. Take care with this wiring and make a note of the wire colour used to make each connection.

If you are using flat 4-way cable, it will not form a watertight seal within the gland. Applying a small amount of silicone sealant around the wire where it passes through the gland can provide this waterproofing.

The Port 1 connection to the sensor consists of a 3mm PVC tube that's covered with a 145mm length of metal tubing. This assembly is passed through the cable gland and clamped in place.


The metal tube maintains an even temperature inside the vinyl tube, keeping it at the same temperature as the pool water. The metal tube also keeps the vinyl tubing straight and holds it in place at a fixed depth in the water.

**If you need to run the TP2 set-up, this can be done now. With power off, temporarily connect the sensor to the alarm PC board terminals, taking care that everything is correct. Now press switch S2 and reapply power.** The Status LED should light and the TP2 voltage will be seen to vary and finally settle at about 2.5V after 60 seconds.

The sensor box can now be mounted at the pool, with the probe tip immersed by about 60mm to 90mm. The box can be attached to the side of the pool using brackets to the ladder or secured to the side of the pool using an underwater-curing epoxy such as Bostik Titan Bond Plus.

Note that when using the box mounting holes, it has two mounting screw points that are effectively located outside of the box enclosure, but which are accessed with the lid off.

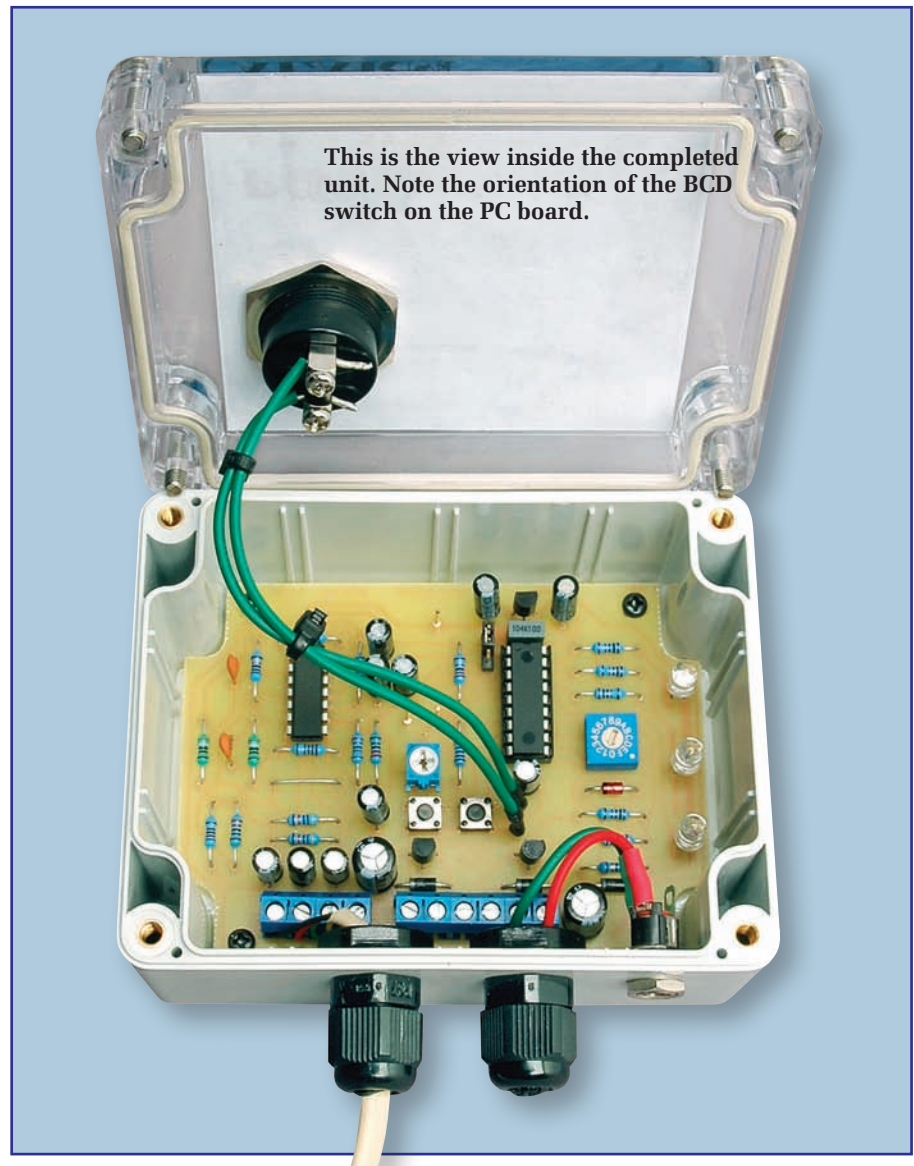The sensor box must be located so that it does not receive the force of the filter pump outlet. In addition, the filter outlet nozzle should be adjusted so that it does not cause turbulence at the top of the water.



The wiring between the sensor box and Pool Alarm needs to be protected from damage by using conduit in areas where it is exposed. This conduit can be placed underground.

You can use one or two sirens with the alarm. These can be located in different parts of your property to provide full sound coverage. It is best to have these disconnected until the Pool Alarm is calibrated.

### Calibration

The calibration is carried out by using on-board switches S2 and S3 to set the water movement levels that correspond to your pool.

For the alarm level, you need to simulate pool water movement when a small child falls into the water. To do this, fill a 10 to 12-litre bucket with water, about one-third full, and drop


the bucket from about 30mm above the pool water into the pool. Press S3 (Alarm Set) to record the movement. The Status LED will light during this procedure.

Note that the calibration may not be successful if the wave from the bucket does not reach the sensor during the 10s calibration period. If it doesn't calibrate, try again (after the pool water has settled) and wait until the wave caused by the bucket has almost reached the sensor before pressing S3. You will need to try this at different points around the pool.

### Quiescent alarm calibration

Quiescent alarm calibration should be done with the filter pump operating and with a typical breeze blowing across the pool. Press S2 (the Quiescent Set switch) during these events to record the water movement levels. The Status LED will



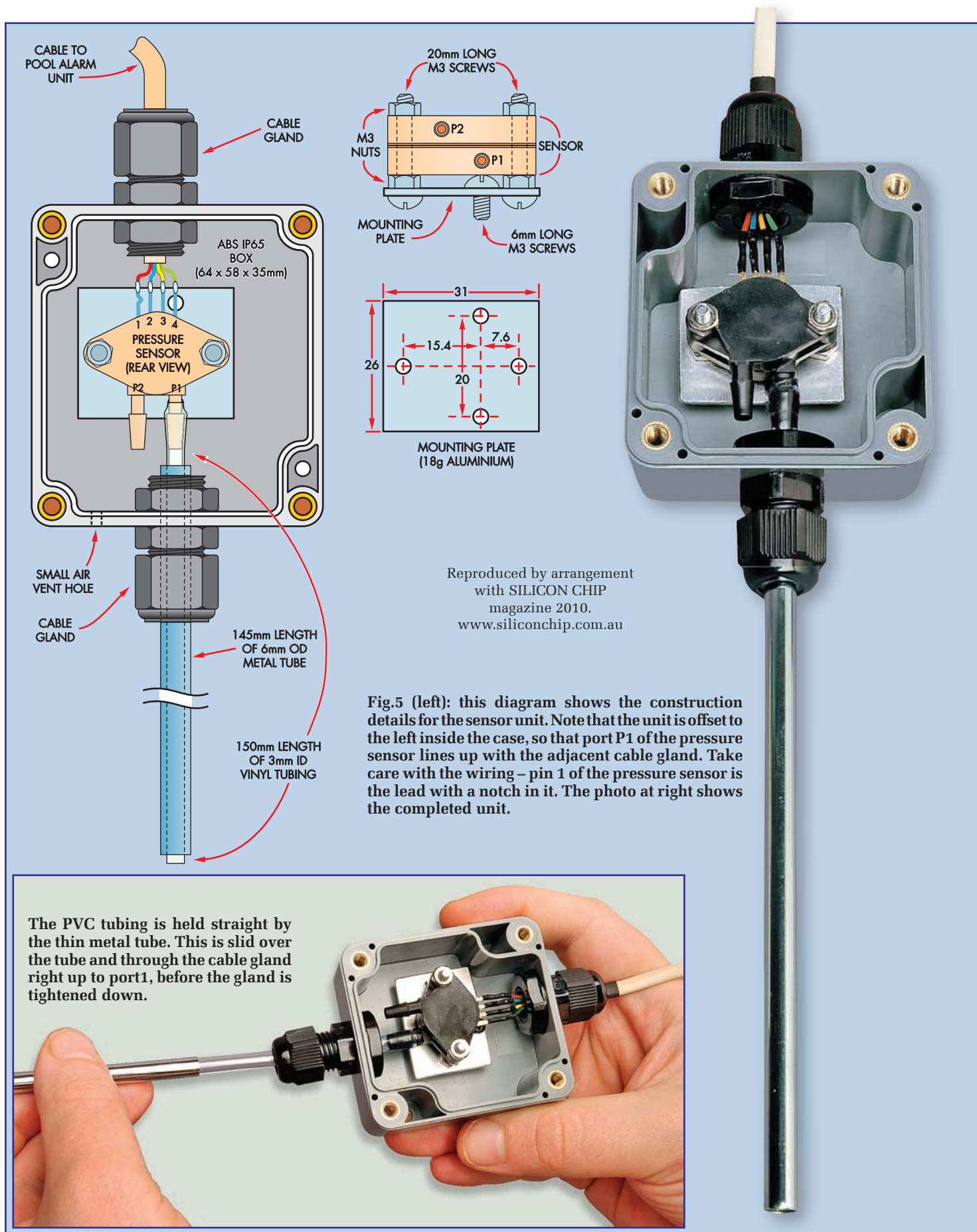

**Table 2: Setting The Alarm Period**

VR1 Setting (measured between TP1 and TP3)	Alarm Period
0.5V	30 seconds
1.0V	1 minute
1.5V	1.5 minutes
2.0V	2 minutes
2.5V	2.5 minutes
3.0V	3 minutes
3.5V	3.5 minutes
4.0V	4 minutes
5.0V	5 minutes

**Table 3: Monitor Return Settings**

BCD Setting	Return Period
0	No return
1	1.25 minute
2	2 minutes
3	3 minutes
4	4 minutes
5	5 minutes
6	6 minutes
7	7 minutes
8	8 minutes
9	9 minutes
A	10 minutes
B	20 minutes
C	30 minutes
D	45 minutes
E	60 minutes
F	75 minutes

light during this time and extinguish after 10 seconds.

Note that this quiescent level must be less than the alarm level in order for the 'return to monitor' function and for the 'set to hold' feature to work.

Now set the alarm period using VR1, noting that the voltage at TP3 will show the timeout. A 1V setting gives a one-minute alarm, while 2V gives two minutes and a 5V setting provides a five-minute alarm – see Table 2.

Next, select whether you want the 'return to hold' feature with LK1 or LK2 and set BCD1 for the required return to

## Parts List – Pool Alarm

- 1 PC board, code 762, available from the *EPE PCB Service*, size 102mm × 77mm
- 1 IP65 sealed polycarbonate enclosure with clear lid, size 115mm × 90mm × 55mm (Jaycar HB-6246 or equivalent)
- 1 IP65 sealed ABS case, 64mm × 58mm × 35mm
- 1 sheet 18g of aluminium, size 26mm × 31mm
- 1 12V 400mA DC adaptor
- 1 piezo siren (Jaycar Cat. LA5308 or LA5256)
- 1 piezo siren as above (optional)
- 1 MPX2010DP Freescale Semiconductor pressure sensor (Jaycar ZD-1904 or equivalent) (Sensor1)
- 1 SPST waterproof momentary switch (Jaycar SP-0732 or equivalent) (S1)
- 2 SPST micro tactile switches (Jaycar SP-0600 or equivalent) (S2, S3)
- 1 BCD DIL rotary switch (0-F) (Jaycar SR-1220 or equivalent) (BCD1)
- 5 2-way PC-mount screw terminals with 5mm or 5.08mm spacing
- 1 2.5mm DC panel socket
- 4 3-6.5mm diameter IP68 waterproof cable glands
- 1 2-way pin header, 2.54mm spacing
- 1 18-pin DIL IC socket
- 2 M3 × 20mm screws
- 6 M3 × 6mm screws
- 4 M3 nuts

- 3 PC stakes
- 1 150mm length of medium duty hookup wire
- 1 30mm length of 0.8mm tinned copper wire
- 1 length of 2-pair (4-wire) telephone sheathed cable or 4-core alarm cable (to suit)
- 2 100mm cable ties
- 1 150mm length of 3mm ID (5mm OD) vinyl tube
- 1 145mm length of 5mm ID (6mm OD) metal tubing

### Semiconductors

- 1 LMC6064IN quad op amp (IC1)
- 1 PIC16F88-I/P preprogrammed microcontroller (IC2)
- 2 BC337 NPN transistors (Q1, Q2)
- 3 1N4004 1A diodes (D1-D3)
- 1 16V 1W Zener diode (ZD1)
- 1 5mm green LED (LED1)
- 2 5mm red LED (LED2, LED3)

### Capacitors


- 2 470µF 16V PC radial elect.
- 5 100µF 16V PC radial elect.
- 3 10µF 16V PC radial elect.
- 2 1µF NP radial elect.
- 1 100nF MKT polyester
- 2 470pF ceramic

### Resistors (0.25W 1% metal film)

- 2 470kΩ
- 1 220kΩ
- 2 39kΩ
- 2 27kΩ
- 2 22kΩ
- 3 2.2kΩ
- 6 1kΩ
- 2 10Ω
- 1 10kΩ horizontal trimpot (VR1)

monitor period – see Table 3. If 'return to monitor' is used (for settings other than 0), then select the setting that best suits your pool use.

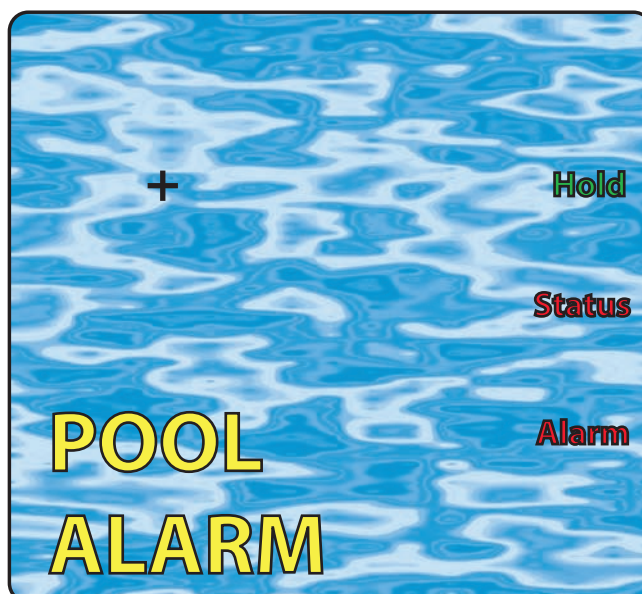If you tend to vacate the pool area after swimming, then the 'return to monitor period' can be set to a short period. If you tend to swim and then sunbake, then a longer period may be necessary to prevent the pool alarm sounding when you return for a swim. **EPE**





# What's That?

**If you're a diabetic, it might just be a complete medical lab in a package smaller than most mobile phones. Medical electronics can now also diagnose early onset of conditions like glaucoma, while an 'electrowetting' technique can create liquid optical lenses. Mark Nelson focuses on these mini miracles.**

It's a cruel irony of the communications overload of today's information era that diabetes remains a closed book to so many people. According to the charity Diabetes UK, up to half a million people in the UK have diabetes but do not realise they have it. Nor are they aware that if untreated, it can be fatal. Treatment often involves regular monitoring of blood glucose levels and with today's overburdened healthcare resources, self-diagnosis is the most cost-effective solution.

## A lab in the palm of your hand

Keeping an accurate watch on your blood sugar levels is an integral part of successful diabetes management and personal blood glucose meters are a vital means of simplifying diabetes treatment. There are well over a dozen models available in the UK, each is battery operated and significantly smaller than a mobile phone handset (about the same size as a pocket pedometer).

Generally, they work by lancing (pricking) your finger (almost) painlessly to extract a minute drop of blood for analysis, and can take as little as five seconds to provide accurate blood sugar level results. A typical modern device can store 500 readings to show the user a 7, 14 or 30-day average, with an alarm buzzer to remind him or her when it's time to perform another test. An infrared port located at the top of the device allows the meter to communicate with a home PC.

The amazingly low (subsidised) cost of these vitally necessary devices belies the highly sophisticated electronics 'under the hood'. Many of them employ a so-called amperometric electrochemical reaction to read the glucose level in the blood. Expressed simply, measuring an electric current passed through a liquid between two electrodes indicates the concentration of the glucose present. In fact, a similar process is used in chocolate factories to control the different sugars to ensure batch reproducibility and maintain the flavour profile that consumers demand from a particular brand.

A popular semiconductor for glucose measurement in blood glucose meters is the Texas Instruments 7001201, which reads the current flowing through the blood sample and provides the result to a MSP430U334 custom microcontroller (also from Texas), which handles the calculation and storage of results, controlling the LCD readout and the infrared port.

## A boon but...

For many sufferers, these blood glucose meters are an absolute boon, but some

observers are not satisfied. They say that these devices are viewed by manufacturers as revenue generation devices, not as devices for real blood glucose control. Also, that little is done to make this technology improve health and healthcare outcomes.

It's certainly true that the meters are almost given away (so that industry can make the real profit on the special test strips used), but also that the information given by the meters is presented so ineffectively that few consumers or health providers actually use it. Users cannot relate the readings to the things affecting them: food, exercise, insulin injections or medications. No attempt is made to reveal patterns which can be used to change therapy and improve people's blood sugars.

These readings could be made more meaningful by enabling the portable meters to communicate with a sophisticated computer network, which could analyse each user's results and advise them what next to do. A step in this direction is the European Commission's current funding of £6.2 million for a portable personalised blood glucose prediction tool called DIAdvisor.

This joint industry and academic scheme is halfway through its four-year term. Analysis of physiological inputs from non-intrusive body-worn wireless monitors will provide information and trend data directly to healthcare providers, to enable further therapy improvements and reduce the cost of treatment. Will this hugely expensive development provide value for money, or solve most sufferers' problems? only time will tell.

## Have you got it?

I know you buy *EPE* to read about practical electronics, not medical matters, but I'd be failing if I didn't explain why the care of diabetes patients was such a big deal. Diabetes is an 'invisible' illness, without any outward signs of its highly unwelcome outcomes. There are currently over 2.6 million people confirmed with diabetes in the UK and up to half a million more who are undiagnosed (I was one of the totally unaware ones).

If you suffer an unquenchable thirst, frequent toilet trips, occasional blurred vision and wobbles or permanent tiredness, do see a doctor as these are the classic signs of diabetes. Diabetes is not curable, but it's treatable, and 90 per cent of sufferers can control it by being careful with their diet, taking tablets or a combination of both. Ignoring the symptoms will have very unpleasant consequences. Now back to electronics.

## Taking the strain

Glaucoma is a disease in which the optic nerve is damaged, leading to progressive, irreversible loss of vision. The second most common cause of blindness around the world, its symptoms can include the patchy loss of peripheral vision, reduced clarity of colours and halos around lights, all of which require examination by an eye specialist.

Because the condition is usually associated with increased pressure of the fluid in the eye, an electronic pressure gauge would be an ideal diagnostic tool, which is what prompted the Swiss company Sensimed to develop Triggerfish, an ingenious 'smart' contact lens that incorporates a minute embedded strain gauge for monitoring the contours of the eye. The lens itself does not interfere with normal vision and can remain on the eye while the user is asleep.

Whereas normal contact lenses are worn daily, Triggerfish is used only for a period of 24 hours (typically). This is because it's used not for correcting sight, but as a diagnostic tool, providing valuable disease management data that is not currently obtainable using conventional ophthalmic equipment.

Another difference from normal contact lenses is that whereas they are self-contained units, Triggerfish is a multi-part device. The contact lens part incorporates a telemetric sensor that 'talks' to a ring-patch worn around the eye that in turn is attached to a recording device similar to a small pocket dictation machine.

Currently, Triggerfish is used only in a few, selected and closely controlled medical centres in Europe, but both Sensimed and ST Microelectronics (the company that developed the combined strain gauge and radio antenna) are looking to create a version that can be mass-produced for widespread use all over the world.

## Liquid lens

An equally ingenious optical device is the liquid lens that Varioptic has developed in France. Unlike 'solid' conventional lenses made of glass or plastic, the liquid lens is essentially fluid, being a droplet of oil inside a thin glass cell.

A clever 'electrowetting' technology alters the surface tension of the liquid, leading to a change of the focal length of the lens. With no moving parts the lens consumes only flea power (less than 50mW) and with suitable electronics gives auto-focussing and image stabilisation. This, says the company, will bring the full digital camera experience to mobile phone users.

THE ORIGINAL SINCE 1994  
**PCB-POOL**<sup>®</sup>  
 Beta LAYOUT

Specialising in Prototype PCBs

**NEW!** Free Laser Stencil  
 with all Prototype  
 PCB orders

**NEW!** 1 WD prototype  
 service

**NEW!** Chemical Tin Finish  
 (no extra cost)

Free  
 Phone  
 UK 0800 389 8560

@ Simply send your layout files  
 and order ONLINE  
 PCB-POOL.COM • sales@pcb-pool.com

Beta  
 LAYOUT

## SHERWOOD ELECTRONICS

Buy 10 x £1 Special Packs and choose another one FREE

SP1	15 x 5mm Red Leds	SP133	20 x 1N4004 diodes
SP2	12 x 5mm Green Leds	SP134	15 x 1N4007 diodes
SP3	12 x 5mm Yellow Leds	SP135	5 x Miniature slide switches
SP5	25 x 5mm 1 part Led clips	SP136	3 x BFY50 transistors
SP6	15 x 3mm Red Leds	SP137	4 x W005 1.5A bridge rectifiers
SP7	12 x 3mm Green Leds	SP138	20 x 2.2/63V radial elect caps
SP8	10 x 3mm Yellow Leds	SP142	2 x Cmos 4017
SP9	25 x 3mm 1 part Led clips	SP143	5 Pairs min. croc.clips (Red+Blk)
SP10	100 x 1N4148 diodes	SP144	5 Pairs min. croc.clips (assorted colours)
SP11	30 x 1N4001 diodes	SP146	10 x 2N3704 transistors
SP12	30 x 1N4002 diodes	SP147	5 x Stripboard 9 strips x 25 holes
SP18	20 x BC182B transistors	SP151	4 x 8mm Red Leds
SP20	20 x BC184B transistors	SP152	4 x 8mm Green Leds
SP23	20 x BC549B transistors	SP153	4 x 8mm Yellow Leds
SP24	4 x Cmos 4001	SP154	15 x BC548B transistors
SP25	4 x 555 timers	SP156	3 x Stripboard 14 strips x 27 holes
SP26	4 x 741 Op-amps	SP160	10 x 2N3904 transistors
SP28	4 x Cmos 4011	SP161	10 x 2N3906 transistors
SP29	4 x Cmos 4013	SP164	2 x C106D thyristors
SP33	4 x Cmos 4081	SP165	2 x LF351 Op-amps
SP34	20 x 1N914 diodes	SP166	20 x 1N4003 diodes
SP36	25 x 10/25V radial elect caps	SP167	5 x BC107 transistors
SP37	12 x 100/35V radial elect caps	SP168	5 x BC108 transistors
SP38	15 x 47/25V radial elect caps	SP172	4 x Standard slide switches
SP39	10 x 47/16V radial elect caps	SP173	10 x 220/25V radial elect caps
SP40	15 x BC237 transistors	SP174	20 x 22/25V radial elect caps
SP41	20 x Mixed transistors	SP175	20 x 1/63V radial elect caps
SP42	200 x Mixed 0.25W CF resistors	SP177	10 x 1A 20mm quick blow fuses
SP47	5 x Min. PB switches	SP178	10 x 2A 20mm quick blow fuses
SP49	4 x 4 metres stranded core wire	SP181	5 x Phono plugs - assorted colours
SP102	20 x 8 pin DIL sockets	SP182	20 x 4.7/63V radial elect caps
SP103	15 x 14 pin DIL sockets	SP183	20 x BC547B transistors
SP104	15 x 16 pin DIL sockets	SP186	8 x 1M horizontal trim pots
SP109	15 x BC557B transistors	SP189	4 x 4 metres solid core wire
SP112	4 x Cmos 4093	SP192	3 x Cmos 4066
SP115	3 x 10mm Red Leds	SP195	3 x 10mm Yellow Leds
SP116	3 x 10mm Green Leds	SP197	6 x 20 pin DIL sockets
SP118	2 x Cmos 4047	SP198	5 x 24 pin DIL sockets
SP124	20 x Assorted ceramic disc caps	SP199	4 x 2.5mm mono jack plugs
SP130	100 x Mixed 0.5W CF resistors	SP200	4 x 2.5mm mono jack sockets
SP131	2 x TL071 Op-amps		

### RESISTOR PACKS - C.Film

RP3	5 each value - total 365 - 0.25W	£3.45
RP7	10 each value - total 730 - 0.25W	£4.75
RP10	1000 popular values - 0.25W	£6.70
RP4	5 each value - total 305 - 0.5W	£4.30
RP8	10 each value - total 610 - 0.5W	£6.95
RP11	1000 popular values - 0.5W	£9.15

Catalogue available £1 inc. P&P or  
**FREE** with first order.

P&P £2.25 per order. NO VAT  
 Cheques and Postal Orders to:  
**SHERWOOD ELECTRONICS,**  
**10 NEWSTEAD STREET,**  
**MANSFIELD, NOTTS. NG19 6JJ**

# MAGENTA

## ELECTRONICS LTD

### MICROSTEPPER Stepping Motor Driver

May 09 EPE. 1/2 1/4 1/8 and 1/16  
 microstep driver for standard 4 phase  
 unipolar motors. Up to 46V at 3A.

Adjustable current with efficient  
 PWM control. Opto isolated in-  
 puts and outputs for computer  
 (LPT)# or logic level control.  
 SLA7062M driver chip contains  
 all sequencer logic - Only needs  
 Step and Direction inputs.  
 Kit includes PTH circuit board  
 Chip, and **all** components.

**KIT 920**  
**£18.76**

Special Offer - Kit 920 + MD23  
 200 Step motor £31.91

# Connection details and (Slow  
 speed) demo PC software: free  
 download from website.

### 20W Stereo Amp.

Low distortion 11W/channel  
 Stereo/20W Mono. True (rms) Real  
 Power. High Slew Rate/bandwidth  
 & low noise. Ideal MP3 booster.  
 Short Circuit & Overtemp. Protect-  
 ed. STA7360 chip. Needs 8 to 18V  
 supply. EPE Project May2005.

**KIT 914**  
**£11.90**

Includes  
 all parts &  
 heatsink  
 for stereo  
 & mono

All Prices Include VAT, Add £3.00 P&P per order, or £7.99 for next  
 day. Chqs. P.O. & most major cards accepted. Mail Order Only.

135 Hunter Street Burton on Trent Staffs DE14 2ST  
 Tel: 01283 565435 Fax: 01283 546932  
 www.magenta2000.co.uk sales@magenta2000.co.uk

## CRICKLEWOOD ELECTRONICS

Established 1981

Frustrated with your supplier?  
 Visit our component packed  
 website for a vast range of  
 parts - old and new,  
 many unavailable elsewhere!  
 www.cricklewoodelectronics.com

**1000's OF PRICES REDUCED!**

Alternatively phone us on  
 020 8452 0161 with your  
 requirements.

Visit our Shop, Call or Buy online at:  
**www.cricklewoodelectronics.com**  
**020 8452 0161**

Visit our shop at:  
 40-42 Cricklewood Broadway  
 London NW2 3ET



# DSP Musicolour: calibrating and operating



Part 3:  
By MAURO GRASSI

*In last month's article, we detailed the construction of the DSP Musicolour. In this month's article, we guide you through the final testing of the DSP Musicolour and give troubleshooting tips. We also explain the operation of the firmware in more detail as well as discussing possible accessories.*

**W**hile the circuit of the *DSP Musicolour* (published in *EPE* in May 2010) may at first seem complicated, it is relatively simple when you consider all the features that we have been able to pack into this powerhouse. Check out the list opposite. We think you'll agree!


We assume that you have read the first and second parts of the article in the previous two issues of *EPE*. If you have followed the construction in last month's issue, you should have a fully assembled DSP Musicolour in its case, and you should have tested the supply rails at test points TP0 and TP1. These should have measured close to their correct values of +5V and +10V respectively.

If they do not measure close to these values, you should refer to the troubleshooting section below for further hints, although we did mention some extra checks to perform in last month's issue, to which you should refer first.

In last month's article, we mentioned that link LK4 is optional and is normally omitted. When LK4 is omitted, the DSP Musicolour has three independent audio inputs that can be used to modulate the output channels. These are the Microphone input, the Left Audio channel and the Right Audio Channel.

The Left and Right Audio channels from the speaker terminals on the back panel are attenuated by the Left and Right potentiometers on the front panel. The Microphone line input is a mix of the on-board electret microphone signal and any external microphone connected to the 6.5mm jack on the back panel.

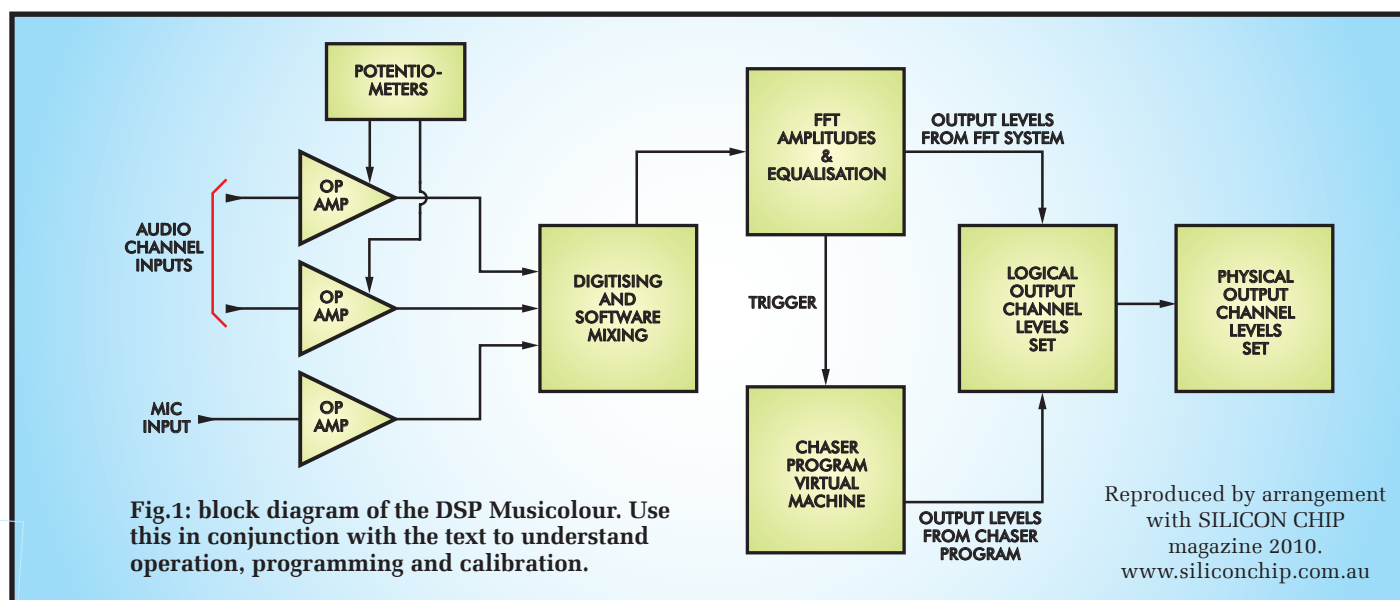When LK4 is installed, however, the Left and Right Audio channels from the back panel are mixed in hardware before being digitised by the microcontroller. In this case, either the Left or Right potentiometer can be used to attenuate the input signal before it is digitised (and you should not install both potentiometers).



In other words, when LK4 is installed you lose one independent audio channel, but you need only one potentiometer on the front panel. Link LK4, therefore, controls whether the DSP Musicolour Left and Right audio channels are mixed in hardware or software (dual mono or joint stereo). The most common option is to omit LK4 and to disable hardware mixing.

With regards to jumper links LK5 and LK6, we mentioned in the first part of the article that the default is to have LK5 installed and LK6 omitted. In fact, the firmware will ignore the state of links LK5 and LK6 – it does not matter if they are installed or not.

## Power up

First, make sure that the plastic case has been screwed shut. When you first apply power, you should see the start up screen scroll past on the dot matrix LED display.

The DSP Musicolour will go through a number of tests and then go to its default state. If it does not, you should switch off mains power immediately and go to the troubleshooting section below.

## Boot-up sequence

When the DSP Musicolour first boots up, it goes through a number of internal checks before commencing operation. The following occurs on boot up (in chronological order):

1. The firmware displays the start up screen and its version number (this can be disabled for a quicker boot by changing the start up settings in the SYSTEM>Startup submenu).
2. The firmware measures the frequency of the mains supply. If the measured value is within tolerance, the firmware accepts the measured value and assigns its internal settings for either 50Hz or 60Hz operation (the firmware chooses the value closest to the measured frequency).

If the measured value is not within tolerance, the firmware will display a warning indicating that no mains was detected and will default to 60Hz operation. In normal mains-powered operation, this warning should never be seen. If it is, it indicates a problem with the Musicolour's zero crossing detection system.

The fallback value of 60Hz was chosen because it is the safer value for the purpose of controlling the triacs in the output stages.

## DSP MUSICOLOUR FEATURES

1. Selectable 8-band equaliser
2. Auto detection of mains frequency (50Hz or 60Hz)
3. Selectable phase-controlled or zero voltage-switched output channels (8-bit resolution)
4. For each logical output channel:
  - (a) Selectable gain
  - (b) Selectable audio passband: arbitrary minimum and maximum frequencies
  - (c) Selectable acquisition mode: peak or average
  - (d) Selectable quiescent level (filament preheat)
  - (e) Selectable ZV (zero voltage) mode, Strobe mode, Direct mode or Continuous mode
5. Selectable logical channel for each physical output channel
6. Chaser modes implemented as a virtual machine
7. Trigger channel with:
  - (a) Selectable audio passband
  - (b) Selectable trigger threshold
8. Firmware support for RC5 remote control (requires additional PC board; to be described next month)
9. Firmware support for high speed UART (requires additional PC board)
10. Selectable balance
11. Selectable display frequency, brightness and screen saver time-out period
12. Selectable sampling frequency, from 16kHz to 50kHz simultaneous on all channels
13. Real time 7-bit FFT using double buffering
14. Persistent software settings and multiple non-volatile user memories
15. Self-calibration and diagnostics
16. Automatic and manual tuning of the internal fast RC oscillator for increased accuracy
17. Adaptive potentiometer controls
18. Silence detection and triggering
19. Input op amp stage clipping detection



3. If you are running from a 50Hz supply, and somehow the frequency is not properly detected and defaults to 60Hz, the shorter mains period will at worst mean that less power is delivered to the output loads. Therefore, even if your mains supply is 50Hz and the detection fails, at least the outputs will not flicker. Flickering can occur when the triacs are switched on beyond the next zero crossing of the mains waveform and should not occur in normal operation.

Another fail-safe feature is that in the rare event that no good mains frequency is detected, the firmware will disable all output channels (the rest of the firmware will function normally, however).

4. The firmware will load any persistent settings from the last active session and initialise all internal peripherals, including enabling all interrupts in the correct sequence.
5. The firmware will detect and enable any connected accessories. It is possible to add a small infrared remote control PC board to the main board to allow the DSP Musicolour to be operated by a standard RC5 remote control.

Also, the firmware implements an RTSP (Run Time Self Programming) server in a secure part of program memory (it also switches the interrupt vectors to an alternative location), which can be used with a UART. The DSP Musicolour is highly customisable, but for most applications, you will not need to change any settings, as the preloaded defaults should be adequate.

6. The firmware will jump to the main loop (described below).

## Automatic calibration

Although the DSP Musicolour will adjust its settings according to the detected mains frequency, all its calculations assume a fixed system clock.

The system clock is derived from the microcontroller's (dsPIC30F4011) internal fast RC oscillator (nominally 7.37MHz) and a 16× PLL multiplication stage is used to achieve around 30MIPs operation (4 clocks per instruction).

Since this oscillator's frequency tolerance can be relatively high, due to internal manufacturing variations, it may be necessary, if you are experiencing unusual effects like flickering lights on the output channels, to calibrate the frequency as close to 7.37MHz as possible. This is a good thing to do – just in case.

The dsPIC30F4011 has an internal non-volatile calibration setting to achieve this, meaning the internal fast RC oscillator can be tuned to bring it as close as possible to its intended frequency. The firmware assumes that the mains line frequency is very close to its theoretical value of either 50Hz (if you are in Australia, Europe and most other parts of the world) or 60Hz (if you are in America, Japan and a few other places).

Since the mains frequency can be measured by the firmware against the system clock, the firmware can then calculate the error in the internal fast RC oscillator and automatically adjust it to minimise the error.

This is what the firmware does in its automatic calibration. It will run once when you first power up, but if you need to, you can also do it manually.

To do this, go to the ADVANCED>Calibration submenu. If you wish to see how far from the ideal the microcontroller is operating, go to the INFORMATION>Error menu, and the current percentage error in the measured mains frequency will be displayed.

## The main loop

After boot up, the firmware spends most of its time in the main loop, where the Musicolour is either in Automatic mode (AUTO LED is lit) or User Mode (USER LED is lit). Either way, the AUTO LED or the USER LED will flash if no input signal is detected.

The SET LED will also flash if there is clipping (overload) in the op amp stages of either the Left or Right audio input channels.

While clipping is very undesirable in an audio amplifier, greatly affecting the sound quality, its effect may actually help in getting a good display from the DSP Musicolour. So the detection of clipping is merely an indication that you may want to turn down the Left and Right potentiometers.

While in the main loop, you may enter the menu system by pressing the SET button. The display is refreshed according to the currently selected display. The selected display can be scrolled to the next available display using the AUTO button when already in Automatic Mode, and the USER button when already in User Mode.

Some of the implemented main loop displays are shown in Table 1. Note that they do not affect the internal operation of the DSP Musicolour; they only affect what the display shows.

In the main loop in Automatic Mode, the CH1 to CH4 LEDs will light according to the logical output channel levels. The main difference between Automatic mode and User Mode is that in Automatic mode the Musicolour uses its current settings for all functions, whereas in User Mode, one of four previously stored settings profiles is used instead.

Thus, User Mode can be used to quickly run the Musicolour in a previously set configuration. In User Mode, the CH1 to CH4 LEDs will indicate one of the four preset profiles currently active. You may press the CH1-CH4 buttons to change the preset on the fly while in User Mode.

The main loop running in Automatic or User Mode consists of the following sequence, as shown in Fig.1.

**Table 1: The display modes in the main loop**

Spectrum Fine	The spectrum is displayed on the display from lowest to highest frequency (left to right).
Spectrum Centered	The spectrum is displayed in centred mode.
Logical Channel Displayed Single	The output levels of each channel are displayed. The top horizontal bar indicates the first logical channel's level. The third horizontal bar from the top indicates the second logical channel's level.
Logical Channel Display	Similarly, the fifth and seventh horizontal bars from the top indicate the third and fourth logical channels' levels respectively.
Averaging	Same as above, except every horizontal bar in between the output channel bars is the average of the previous and next bars.
RMS display	Displays the RMS level of the input signal as an analogue meter.

## Logical and physical channels

We should first mention that the firmware supports four logical output channels and four physical output channels. The physical output channels correspond to the outputs on the back panel. Each of these can be associated to a logical channel. In normal operation, the physical channel N is associated to the logical channel N.

However, added effects can be achieved by changing the mapping from output channels to logical channels. For example, you can have all four physical channels on the back panel controlled by one logical output channel.

We now explain the operation of the main loop. As can be seen in Fig.1, the three inputs consisting of the Left and Right audio inputs and the Microphone inputs are digitised and mixed according to the balance settings under AUDIO>Balance. Any combination of these three channels can be used as the input signal. The result of this software mixing is passed to the FFT (fast Fourier transform) system.

The output of the FFT resolves the captured slice of the input audio waveform into 128 ( $2^7$ ) frequency amplitudes. These are equally spaced from 0Hz up to the sampling frequency. The smallest frequency that the FFT can resolve is  $F/128$ , where F is the sampling frequency. For example, when F is 48kHz we can resolve down to 375Hz or  $\pm 137$ Hz. If you are not very interested in the audio sub-band above, say, 10kHz, then you can lower the sampling frequency to 20kHz and the FFT will be able to resolve frequency components down to 156Hz or  $\pm 78$ Hz.

The audible spectrum for humans is nominally from about 20Hz to 20kHz. Although the sampling frequency of the ADC system can be set anywhere from 16kHz up to 50kHz, keep in mind that according to the Nyquist sampling theorem the highest frequency that can be resolved using a sampling frequency F is  $F/2$ .

This means that aliasing will occur at least somewhere in the audible spectrum if the ADC system's sampling frequency is set below about 44kHz. Aliasing is usually an unwanted characteristic of a digitising system. However, since most music has very little high harmonic content, in fact little content above 4kHz, it may be desirable to lower the sampling frequency in order to increase the resolution of the FFT.

The FFT system computes logical output channel levels in two acquisition modes. These can be set in the CHANNELS>Mode submenu.

The two acquisition modes are PEAK and AVERAGE. In AVERAGE mode, the average of the relevant frequency components falling within the channel's passband (set by the minimum and maximum frequencies for the channel) will be the output level requested in the output stage. In PEAK mode, however, only the maximum level within the channel's passband will be the output level requested in the output stage.

There is an optional Equaliser module, which can be enabled or disabled. The levels of the equaliser can be changed, however, by going to the AUDIO>Equaliser submenu.

The equaliser has eight bands set to affect preset portions of the audible spectrum. The current equaliser bands can be seen under the INFORMATION>Equaliser submenu, and cannot be changed by the user (it can, however, be changed by reprogramming the device).

Note that the equaliser affects the output of the FFT, not the input. After any equalisation is performed, the levels

## Warning!

The DSP Musicolour operates from the 230/240V AC mains, and many internal components and sections of the PC board tracks are also at mains potential. **Contact with any of these could be FATAL.**

**DO NOT TOUCH any of these parts unless the power cord is unplugged from the mains supply. DO NOT CONNECT this device to the mains unless it is fully enclosed in the specified case.**

**This project is not for the inexperienced. DO NOT BUILD IT unless you know exactly what you are doing and are completely familiar with mains wiring practices and construction techniques.**

of the logical output channels are set by the FFT system, if the chaser mode is set to OFF (see the CHASER>Mode submenu below).

If the chaser mode is not set to OFF then the level data produced by the FFT system is ignored and the data produced by the current chaser program (see the CHASER>Program submenu below) is used to set the logical output channel levels instead. If the chaser mode is set to TRIGGERED, then the trigger pulse (produced by the FFT system) is used to step through the chaser program.

## Triggering

Triggering can either occur directly from the Trigger channel or from the Silence detection. Silence detection triggers when there is a relative silence in the input Left or Right audio signals (the MIC input is not used for the silence detection).

The trigger can be considered a separate logical channel, which has its own selectable passband and threshold. When the threshold is reached, the trigger occurs. The trigger is used by the chaser system to trigger the current chaser program in TRIGGERED mode.

Tips: if, for example, you want bass response triggering a pre-set chaser program, you would set the TRIGGER minimum frequency to 0Hz and the maximum frequency to around 300Hz. Then adjust the threshold level to get an acceptable level of triggering.

## Light Chaser

The chaser program is either executed at the rate set in OUTPUT>Output Rate, or each step in the program is triggered. Both the Chaser system and the FFT system produce a set of output levels for the logical output channels. Depending on the chaser mode being used, the chaser levels or the FFT levels will be used to change the levels of the logical output channels. These will then affect the physical output channels.

## Channel modes and settings

Each of the four logical output channels can operate in one of four primary modes: DIRECT mode, CONTINUOUS mode, ZV mode (zero voltage switching) or STROBE mode.

In the DIRECT and CONTINUOUS modes, the brightness of the logical output channel is varied in 256 levels (8 bit resolution). The output brightness is approximately



linear, as the firmware uses an internal dimming curve to correct the non-linearity inherent in phase control. The difference between DIRECT and CONTINUOUS mode is how the output level is set by the output system.

The main difference between the DIRECT and CONTINUOUS modes is that while in DIRECT mode the brightness is set directly, in CONTINUOUS mode, the brightness is 'continuously' modified from the current brightness level.

In other words, in CONTINUOUS mode, if the requested level is higher than the current level, the current level is increased by the ATTACK setting for the channel, while if the requested level is lower than the current level, the current level is decreased by the DECAY setting for the channel. Setting different ATTACK and DECAY levels for the channel can affect the level of the output logical channels in CONTINUOUS mode.

In ZV mode, the output channel responds as in DIRECT and CONTINUOUS modes, except that the output is not a brightness level but a digital output. The output is either fully on or fully off. This mode approximates a zero voltage switching mode and can be used to reduce RF interference or achieve a digital effect.

In STROBE mode, the output level sets the frequency of the logical output channel rather than the brightness level. The strobe frequency will be set from the maximum (equal to the mains supply frequency, either 50Hz or 60Hz, down to 1/256th of the mains supply frequency; ie, around 0.2Hz).

## Quiescent level or filament preheat

In all channel modes except STROBE, each logical output channel has a settable quiescent level, which is used to reduce the stress on the filaments in your incandescent lamps and to reduce surge currents through the triacs at switch on.

The quiescent level can be set by going to OUTPUT> Quiescent Level and is settable from 0 to 25% of the full brightness level. Note that if the channel mode is ZV and

the Quiescent Level is not 0%, the channel may seem to be continuously on, depending on the ZV threshold. In this case, you should set the Quiescent Level to 0% or disable ZV mode, or change the ZV threshold by going to OUTPUT>ZV Threshold.

## A closer look at the operation of the Musicolour

The triacs are controlled through the optocouplers using the four output compare channels of IC1 (dsPIC30F4011). In order to maintain a constant brightness of the output lights, it is necessary for the switch-on pulses to the triacs to be synchronised to the frequency of the mains supply.

To achieve this, the microcontroller uses the INT0 external interrupt pin, which is supplied by one side of the transformer's secondary winding. An interrupt can be triggered on a rising or falling edge of INT0. Now, a low level on INT0 is any voltage lower than about 1.5V, while a high level is considered to be anything above 3.5V.

We have a 5V supply, but a 7.5V secondary winding. This means that the triggers to INT0 (which is the microcontroller's zero detection interrupt) are asymmetrical. The measured duty cycle is about 42% rather than the expected 50%. The firmware corrects this asymmetry, adjusting the value of a phase counter to take account of this.

Compare Fig.2 (without software correction) and Fig.3 (with software correction). In the scope screen grab of Fig.3, the yellow trace is the output of the triac and the green trace is the trigger pulse.

You can see that the trigger pulse period is only 8.5ms, whereas for symmetrical triggering it should be close to 10ms (this is the 100Hz rate, which is twice the mains frequency in the UK) as shown in Fig.3.

## User operation of the DSP Musicolour

The Musicolour has many settings that can be changed by the user. As mentioned, the preloaded default values

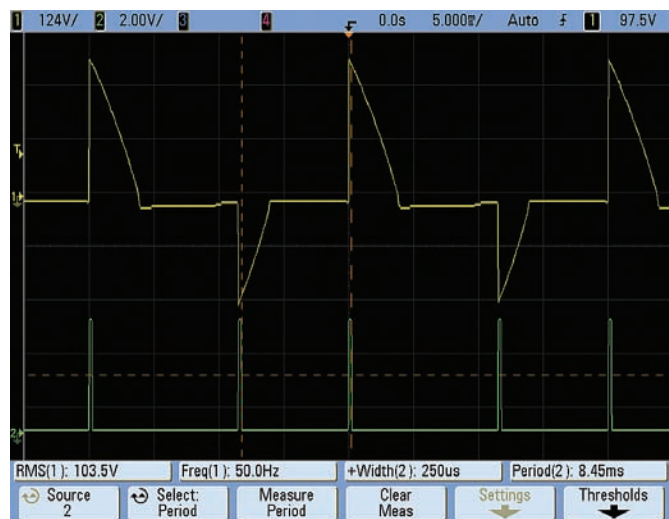


Fig.2: one of the physical output channels being switched without software correction for asymmetrical phases. The yellow trace is the output of the triac, while the green trace is the trigger pulse applied to the gate through the optocouplers.

You can see that the triggering is asymmetrical with a period of about 8.5ms, rather than the expected 10ms. Without software correction, the output brightness of the lights can vary and appear to flicker slightly.

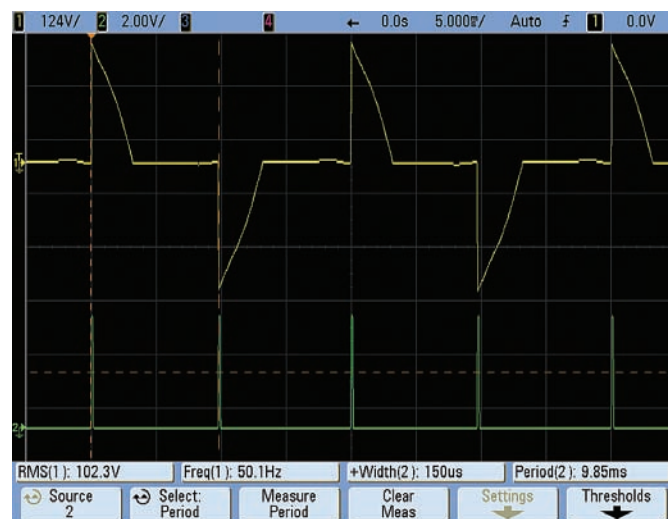


Fig. 3: the same set up as in Fig.2, but with software correction. The period is now much closer to the correct value of 10ms.

The firmware automatically corrects this asymmetry when driving the triacs. It does so in real time at a frequency twice the mains line frequency. Symmetrical triggering is desirable because it helps to maintain a stable and constant brightness on the physical output channels.

should be adequate for most applications. You can go to the *EPE* website and download more complete user instructions for the DSP Musicolour that were too long to include here.

## Front panel

There are seven pushbuttons on the front panel that are used to navigate through the menus and change internal settings. Some buttons have multiple functions, according to context. The SELECT potentiometer is also context-sensitive, and is used to change settings.

The incorporated LEDs in each of the buttons will light depending on the context. Usually, a lit or flashing button will mean that the button has an active function in the current menu. When the firmware is executing the main loop, the LEDs will indicate the state of the output channels and the current operating mode.

## Adaptive potentiometer controls

The DSP Musicolour firmware implements adaptive potentiometer controls. This means that if a setting is to be modified using the SELECT potentiometer, the setting will begin to change only when the potentiometer position first matches the current value of the setting. This gives the potentiometer a kind of memory, and is used to seamlessly change internal settings depending on the current menu.

## Menu system

The settings of the DSP Musicolour are changed through a hierarchical menu system. When it is in the main loop, pressing the SET button allows you to enter MENU mode.

Keep in mind that some of the behaviour of the Musicolour is dependent on its current settings. For example, the display will be blank if the screen saver has been set to NONE and there is no key activity for the period of the screen saver timeout.

## Using the Chaser Modes

Go to the CHASER>Mode submenu. Here you can choose Normal or Triggered modes. In NORMAL mode, the currently selected Chaser program is executed. In TRIGGERED mode, the currently selected Chaser program is executed, but the stepping through the program depends on the trigger (affected by the music).

If you are using TRIGGERED mode, you should know that the triggering will depend on the current settings for the trigger channel. Go to the TRIGGER submenu. There you should set the pass-band and threshold. Set the mode to OFF to run the output channels from the FFT.

Once you have set the Chaser mode, you then select the Chaser Program that you wish to run by going to CHASER>Program.

## Conclusion

As you can see, the DSP Musicolour offers an amazing repertoire of features – far too many to allow us to describe in detail here.

Next month, we plan to have more information on driving the DSP Musicolour, as well as an optional PC board that gives you complete remote control. What? A lightshow with remote control? You betcha!

## Quick setup checklist

Here's how to set up the DSP Musicolour quickly, together with the relevant settings that will affect its operation:

1. Set the ADC system's sampling frequency:  
go to AUDIO>Sampling Frequency.
2. Set the mixing settings for the input signal:  
go to AUDIO>Balance.
3. Set the minimum and maximum frequencies for each logical output channel: go to CHANNELS>Min Freq and CHANNELS>Max Freq. Alternatively, go to CHANNELS>Freq to set a non-overlapping frequency mask.
4. Set the gain for each logical output channel:  
go to CHANNELS>Gain.
5. Set the mode for each logical output channel:  
go to CHANNELS>Mode.
6. Set the output connections of the logical channels:  
go to OUTPUT>Logical Channels.
7. Set the CHASER>Mode and CHASER>Program
8. Exit the menu system.

**Tip:** Every submenu has a Default option to reset all values in that submenu to default values.

## Simple setup guide

Assuming you have a music source connected to an audio amplifier, connect the output terminals of your amplifier to the speaker terminals on the back panel of the DSP Musicolour.

Next, adjust the sensitivity of the Left and Right channels using the Left and Right potentiometers on the front panel.

Load default values by going to the menu. Press SET while in the main loop to be directed to the menu. Scroll down to the DEFAULTS submenu using the UP and DOWN buttons on the front panel. Press SET to enter the DEFAULTS submenu. Scroll down to 'Load Defaults' and press SET. This will restore all default values. Exit the menu system by pressing CH 4/D (the back button while in menu mode) and the DSP Musicolour should start running the main loop in Automatic mode. The output channels will respond to the music.

Remember that the DSP Musicolour has many user options.

As a summary, you should know that:

- (a) Each of the four physical output channels must be connected to a logical channel. Two physical channels can be connected to the same logical channel. Go to OUTPUTS>Logical Channels to set these.
- (b) The input signal source is an arbitrary mix of the Microphone, Left and Right audio inputs. You set this in the AUDIO>Balance submenu.
- (c) The inputs are sampled at the set sampling frequency. Go to AUDIO>Sampling Frequency to set this.
- (d) For each logical channel, you should select its pass-band (the minimum and maximum frequencies). Only frequencies in the input signal that fall in this pass-band will affect that logical channel.
- (e) For each logical channel, you can select the gain. The higher the gain the more sensitive the channel will be to pass-band frequencies in the input signal.
- (f) For each logical channel, you should select its mode. This affects how the channel responds to level requests. Choose from PEAK or AVERAGE acquisition modes. These determine how the FFT data affects the level of the logical output channel. This level is interpreted differently according to whether the channel is in DIRECT, CONTINUOUS, ZV or STROBE mode. So you should choose one of these four modes as well.



## User operating instructions: menu system

The Musicolour uses a hierarchical menu system. From the main loop, press the SET button to enter the menu system. You will be directed to the main menu, where you

may scroll up or down between submenus by using the UP and DOWN buttons. Use the SET button to enter a submenu. In any submenu, you may use the CH4/D button

to go back to the previous menu (if you are in the main menu, you will be directed back to the main loop).

### Submenus available in the main menu:

1. **CHANNELS:** this submenu allows you to change any settings related to the four logical channels.
2. **TRIGGER:** this submenu allows you to change the trigger passband and the trigger threshold.
3. **CONSOLE:** this submenu contains user applications, allowing the Musicolour to function as a light dimmer or communications terminal.
4. **OUTPUT:** this submenu is used to set the chaser mode, the chaser program, the output rate, the quiescent level of each physical channel and to define the logical to physical channel translation.
5. **AUDIO:** this submenu is used to change the equaliser settings, the software mixing/balance of the input signal and the sampling frequency.
6. **DEFAULTS:** this submenu is used to save and recall settings and to load default values.
7. **ADVANCED:** this submenu is used to access advanced features, including calibration, software upgrade and tuning.
8. **INFORMATION:** this submenu displays information about the Musicolour's operation, such as the mains frequency, the frequency of the ADC system and the screen refresh frequency. The error in the overall accuracy of the timing system can also be seen.
9. **DISPLAY:** this submenu is used to change the display's settings, including the screen refresh frequency, the screen brightness and the screen saver time out period.
10. **SYSTEM:** this submenu can be used to change system settings, the firmware version is displayed, the baud rate of the UART can be changed, the remote control system can be enabled and other system settings changed.

Here are the major submenus used at this stage:

### CHANNEL submenus:

**CHANNELS>Min Freq:** Press the channel buttons CH1-CH4 to display the current minimum frequency for that logical

channel; Use the SELECT potentiometer to change the minimum frequency.

**CHANNELS>Max Freq:** Press the channel buttons CH1-CH4 to display the current maximum frequency for that logical channel; Use the SELECT potentiometer to change the maximum frequency.

**CHANNELS>Freq:** this is similar to the **CHANNELS>Min Freq** menu, except that after exiting, the minimum and maximum frequencies for the four channels are set in non-overlapped fashion.

**CHANNELS>Gain:** Press the channel buttons CH1-CH4 to display the current gain for that logical channel. Use the SELECT potentiometer to change the gain.

**CHANNELS>Mode:** Press the channel buttons CH1-CH4 to display the current mode for that logical channel. Use the UP and DOWN buttons to scroll through the available modes.

**CHANNELS>Attack:** Press the channel buttons CH1-CH4 to display the current attack rate for that logical channel. This is only relevant when the channel is operating in CONTINUOUS mode. Use the SELECT potentiometer to change the attack rate.

**CHANNELS>Decay:** Press the channel buttons CH1-CH4 to display the current decay rate for that logical channel. This is only relevant when the channel is operating in CONTINUOUS mode. Use the SELECT potentiometer to change the decay rate.

**CHANNELS>Test Channel:** Press the channel buttons CH1-CH4 to test the relevant logical channel with a range of output level requests from 0 to full level. This can be used to test the current settings for the channel.

**CHANNELS>Defaults:** Press SET to restore default CHANNEL submenu values.

### TRIGGER submenus

**TRIGGER>Min Freq:** Press the UP and DOWN buttons to set the minimum frequency defining the trigger pass-band. Exit using the SET button.

**TRIGGER>Max Freq:** Press the UP and DOWN buttons to set the maximum frequency defining the trigger pass-band. Exit using the SET button.

**TRIGGER>Threshold:** Use the SELECT potentiometer to change the threshold level for the

trigger. Triggering will occur when the input signal has an amplitude component within the trigger pass-band that is greater than the trigger threshold. The level is indicated as a horizontal bar. Exit using the SET button.

**TRIGGER>Defaults:** Press SET to restore default TRIGGER submenu values.

### CONSOLE submenus:

**CONSOLE>Dimmer:** Press the channel buttons CH1-CH4 to select the relevant logical output channel. Use the SELECT potentiometer to change the output level of this channel. Here the Musicolour functions as a four channel light dimmer.

**CONSOLE>Com:** The Musicolour enters an echo terminal mode. Received data from the UART is displayed on the display. The UART can be enabled using additional hardware.

### OUTPUT submenus:

**OUTPUT>Chaser Mode:** the current chaser mode is displayed. Press the SET button to scroll to the next available mode.

**OUTPUT>Chaser Program:** the current chaser program is displayed. Press the UP and DOWN buttons to set the program. Press SET to exit.

**OUTPUT>Output Rate:** the current output rate is displayed. Use the SELECT potentiometer to change the rate. Press SET to exit.

**OUTPUT>Quiescent Level:** Press the channel buttons CH1-CH4 to select the relevant logical output channel. Use the SELECT potentiometer to change the quiescent level of this channel.

**OUTPUT>Logical Channels:** Press the channel buttons CH1-CH4 to select the relevant physical output channel (on the back panel). Use the UP and DOWN buttons to change the logical output channel associated to that physical channel. In Normal operation, you set CH1=1, CH2=2, CH3=3, CH4=4; if for example, you wish to have logical channel CH1 control two physical outputs on the back panel, you could set CH1=1 CH2=1 CH3=3 CH4=4; If you would like to permute the channels you can also do that here.

**OUTPUT>Defaults:** Press SET to restore default OUTPUT submenu values.

### AUDIO submenus:

**AUDIO>Equalizer:** The current equalizer settings are shown as vertical bars. Use the UP

and DOWN buttons to scroll to the next setting, and use the SELECT potentiometer to vary the current equalizer setting.

**AUDIO>Balance:** the current percentages of each of the three audio channels contributing to the input signal are shown. Press SET to change these. The levels are then displayed as bars. The first bar from the left is the MIC line level. The next two bars indicate the LEFT and RIGHT levels respectively. Use the SELECT potentiometer to change the LEFT/RIGHT balance. Use the UP and DOWN buttons to change the MIC contribution to the input signal.

**AUDIO>Sampling Frequency:** the current sampling frequency in kHz is displayed. Press SET and use the SELECT potentiometer to vary this value.

**AUDIO>Defaults:** Press SET to restore default AUDIO submenu values.

## DEFAULTS submenus:

**DEFAULTS>Load Defaults:** Press SET to restore all settings to default values.

**DEFAULTS>Save Settings:** Press UP and DOWN buttons to change the memory number to save to. Press SET to save all current settings to non-volatile memory.

**DEFAULTS>Recall Settings:** Press UP and DOWN buttons to change the memory number to load values from. Press SET to load all settings with previously stored values.

## ADVANCED submenus

**ADVANCED>Calibration:** Press SET to automatically calibrate the Musicolour's internal fast RC oscillator against the mains frequency.

**ADVANCED>Software Upgrade:** Press SET to upgrade the firmware. This mode requires a functioning UART connection, which needs additional hardware.

**ADVANCED>Tune Oscillator:** Press UP and DOWN to change the internal calibrating value for the system clock. This value is updated by the automatic calibration above. You can manually adjust the value here.

## INFORMATION submenus

There are no settings to change here. Only the values of certain system parameters are displayed. This is for operating information like the mains frequency, the screen refresh rate, the sampling frequency, the system clock, the error in the system timing from the ideal, etc.

## DISPLAY submenus:

**DISPLAY>Brightness:** Press SET to change, using the SELECT potentiometer, the brightness of the display.

**DISPLAY>Frequency:** Press SET to change, using the SELECT potentiometer, the screen refresh frequency. Note that strange display effects can occur at low screen refresh frequencies. If this is the case, increase the frequency. Usually a level around 65Hz or higher is adequate.

**DISPLAY>Timeout:** Press SET and use the UP and DOWN buttons to select the timeout period for the screen saver.

**DISPLAY>Screen Saver:** Press SET and use the UP and DOWN buttons to select the current screen saver.

**DISPLAY>Display Defaults:** Press SET to restore all DISPLAY submenu defaults.

## SYSTEM submenus:

**SYSTEM>Version:** displays the current firmware version.

**SYSTEM>Uart:** Press UP and DOWN to change the baud rate for the UART. This requires additional hardware.

**SYSTEM>Remote Control:** Press SET to enable or disable the remote control decoding. This requires additional hardware and can be used to control the Musicolour using an RC5 compatible remote control.

**SYSTEM>IrDA:** Press SET to enable or disable the IrDA decoding. This requires additional hardware and can be used to add a wireless infrared serial port. This can be used to send and receive data from a PC.

**SYSTEM>Test:** Press SET to run a test on the display, the output channels and the LEDs. Can be used to check that all these are working correctly.

**SYSTEM>Detected Mains:** this shows the detected mains frequency and is either 50Hz or 60Hz. It should match your area's mains supply frequency.

**SYSTEM>Startup:** Press SET to scroll through the start up modes for the Musicolour. The initial startup can be made quicker by disabling the normal boot-up messages.

**SYSTEM>RF6:** Press UP and DOWN to change the RF6 pin mode. This is an advanced feature that can be useful to debug any problems with the Musicolour. The RF6 output of the microcontroller is a digital output and is available at pin 9 of CON3 on the main board. The system clock frequency can be measured at this pin, as well many other internal operating frequencies like the screen refresh frequency and the ADC system frequency. You will not need to normally use this menu.

**SYSTEM>Reset:** Press SET to reset the Musicolour.

**SYSTEM>System Defaults:** Press SET to load SYSTEM submenu defaults.

## In Depth Explanation of the Main Loop

In more detail the main loop is as follows:

1. The firmware waits until the internal ADC system signals that the buffer has been filled with digitised and software mixed audio data (while waiting all interrupts are active, including all timers, key press detection and display refresh interrupts).
2. Once a full buffer of data has been acquired, the Fourier transform is computed.
3. For each logical output channel, a level corresponding to the channel is computed. This may involve adjusting the output of the FFT with equalisation, it will depend, for each channel on its selected acquisition mode.
4. A request is made, for each logical output channel to set its output level to the previously computed level. The implementation of this step is dependent on the channel's current setting. If a channel should be accepting data from an active chaser program, the level requested in this step is ignored.
5. If a Chaser program is active, it is serviced by the virtual machine. This may involve the triggering channel if the program is in trigger mode. Any output level requests made by the chaser program are set. Again, the implementation of this step is dependent on the channel's current settings.
6. The display is refreshed according to the currently selected display.
  1. Spectrum Fine: the spectrum is displayed on the display.
  2. Spectrum Centered: the spectrum is display in centered mode.
  3. Logical Channel Displayed Single: the output levels of each channel are displayed. The top horizontal bar indicates the first logical channel. The third horizontal bar from the top indicates the second logical channel. Similarly, the fifth and seventh horizontal bars from the top indicate the third and fourth logical channels respectively.
  4. Logical Channel Display Averaging: same as 3 above, except every horizontal bar in between the output channel bars is the average of the previous and next bars.
  5. RMS display: displays the RMS level of the input signal as an analogue meter.
  6. The firmware updates any LEDs on the front panel and returns to step 1. It also responds to key presses.



## Troubleshooting tips

Some solutions to common problems that may help you troubleshoot the DSP Musicolour.

### Problem

You apply power and there seems to be no activity, there is no display.

### Possible cause

Is the fuse blown? Have you installed a fuse?

### Problem

You apply power and there is a sudden short of the mains supply (consequently the fuse blows or the circuit breakers/fuse in your home open). There seems to be a short of the mains supply.

### Possible cause

This could be caused by incorrect link settings for LK1, LK2 and LK3 underneath the mains transformer.

### Problem

One or both voltages at test points TP0 and TP1 are not at normal levels around +5V and +10V respectively.

### Possible cause

One possible cause is that links LK1, LK2, LK3 are improperly set or omitted. Remember, these have to be installed according to the mains supply voltage. Install LK2 and omit LK1 and LK3 if you are using a 220-240V mains supply; install LK1 and LK3 and omit LK2 if you are using a 110-120V mains supply. These links are found under the mains transformer, so you may have to unsolder the transformer to change them. If you have erroneously configured these links for 110-120V operation while you are actually in a 220-240V region of the world, you will get double the intended voltage at test-point TP1. This can very easily destroy REG1 and cause further damage to the main PC board. Disconnect power immediately if the voltages at TP0 or TP1 are much higher than their intended values.

### Problem

The main board seems to be operating correctly, except nothing is shown on the dot matrix LED display.

### Possible cause

The most common cause of this problem is that the 26-way ribbon cable connecting the main board and the display board is either faulty, not all connections are good, or it is incorrectly oriented. If you can verify that the ribbon cable's 26 connectors are good, it may indicate a fault with incorrectly oriented parts. Check the transistors and ICs are correctly oriented on the display PC board. Check also that the dot matrix LED modules are in their sockets the right way around.

### Problem

At least one key does not respond to key presses or its LED does not light up.

### Possible cause

This is most likely caused by the tactile switch being incorrectly oriented, improperly soldered, or its accompanying diode being incorrectly oriented.

### Problem

When in a menu, moving the SELECT potentiometer does not affect the setting, or does so after much turning.

### Possible cause

This is most likely not a problem, but a feature. It is called adaptive control. See the text for an explanation.

### Tips and tweaks

Notice that if the display frequency is set too low you may see strange effects on the display. Increase the screen refresh frequency if this occurs. Also, if the sampling frequency is lower than twice the highest frequency of the input audio, aliasing will occur.


## Troubleshooting in 'safety first' mode

If all goes to plan, you'll build the DSP Musicolour, turn it on . . . and it will work perfectly, first time. But what if it doesn't?

We've warned a number of times that the Musicolour must not be run with the lid off and the mains connected. It is simply too dangerous. So how can you work on an unpowered circuit?

Obviously, you can't. But fortunately, all of the logic and processing circuitry (including the dsPIC) can be run from a 5V DC supply (rated at 500mA or so) so you can troubleshoot with safety.

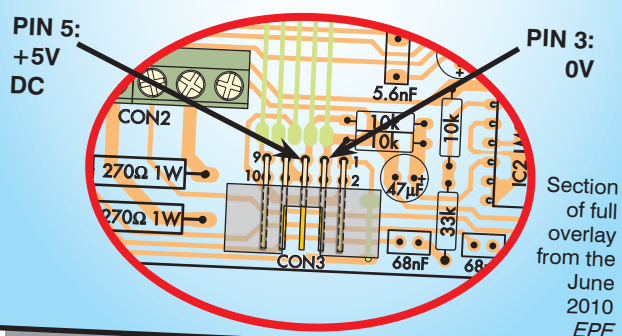If you need to poke around the Musicolour, CON3 can be used to supply power to the circuit. Simply connect +5V to pin 5 and 0V to pin 3 of CON3 and all of the low-voltage circuitry will be powered, up to and including the four opto-couplers. DON'T plug in the mains lead!



# What about the Musicolour Display – the lights!

By Ross Tester

The DSP Musicolour is capable of driving up to 2400W of lights over its four channels, with a maximum of 800W in any one channel.

That's an awful lot of coloured light – far more than you'd normally find at a party, which tends to be on the dark side anyway.

Let's look at the type of lights you can use (and shouldn't use).

First of all, steer clear of halogen (QI) lights. Their problem is the time the filament takes to cool and the light to go 'out'. They also get very hot and this can be a problem with coloured films – depending on the type, they scorch with high temperatures and can even catch fire. That's about the last thing you want.

By far the most popular display/party lights are the coloured ES (Edison screw) PAR38 or R80 bulbs. The coloured PAR38s are usually rated at 120W (their plain white cousins are usually 150W, some 120W).

Incidentally, just in case you wanted to know, PAR38 means Parabolic Aluminised Reflector, 38 eighths of an inch (or 4.75 inches) in diameter. R80 means an 80mm diameter reflector light globe. So there!

The biggest (money) problem with coloured light globes is the price – they are significantly more expensive (about four times or more) than white ones. But I have a sneaky solution here: paint white globes and save heaps!

You can't use ordinary paint, of course – it is opaque. But you can buy translucent glass paint at better craft stores in a wide variety of colours. The most common colours for light displays are also the easiest to get – red, yellow, blue and green.

This paint is intended for making (fake) 'stained glass' windows, but I've found it to be quite tolerant of high temperatures, so it can be painted directly onto white globes. The brand I use is Vitrail, from France. But I've also seen other brands of this type of paint advertised on eBay (just make sure it is translucent/transparent when dry).

I've used it for years instead of buying coloured globes and it works very well. You simply paint it on so that the glass has an even covering; usually only one coat is required.

Allow it to dry before turning on the light – even then, you're likely to get some coloured vapours given off and it does tend to stink a little! If I'm in a real hurry, I might



apply a little heat from the light globe – say ten seconds on, a minute off – to impart a little forced drying.

OK, so that's the coloured globe side covered. Now, how about their mounting?

Simple, I thought: just go and buy some ES batten lampholders, mount them on a length of flat timber and wire them up. Yeah, simple all right: have you seen the price of ES battens recently?

You can get a standard BC (bayonet cap) batten lampholder for a few pounds just about anywhere. The same things in ES (Edison screw), which are required for the PAR38 and many R80 bulbs, tend to start at around a tenner and go up from there.

But, I 'cheated' here too. In our local hardware store, I spotted a PIR movement detector security light, complete with two ES lampholders and two 150W PAR38 bulbs, all for under a tenner. So I bought two of these, giving me four ES lampholders and four PAR38 bulbs.

I discarded the two PIR sensors (anyone know what to do with two brand new PIR sensors?) and mounted the two sets of two ES lampholders on a length of flat timber and wired them (individually) to short 240V mains leads.

Even here I was able to save, by using old 240V leads. Call it the scrounger in me, but every time I discard any electric appliance, if the mains lead is OK I cut it off and save it – just in case. Well, here's the case and phhhhhh to all those who have criticised me for hoarding rubbish saving and recycling perfectly good stuff!

In fact, I used two such salvaged mains leads and two old IEC mains leads, which had also been saved from the scrapheap (actually rescued from the last council clean-up). The

IEC plugs themselves were not needed (not now, at least!) so I cut them off with maybe 250mm of mains lead attached (just in case!) and put them back in my 'spare mains lead' box. You never know. . .

That gave me four mains leads, complete with three-pin plugs, about 1.5m long. Perfect!

I've shown a photo of my 'cheapo' Lamp Display Unit above. While this is very obviously only one approach, it gives you an idea of what you can do to make a very reasonable lightshow for a very reasonable price.

The ES bases even have some very handy terminal blocks inside, so wiring them up is delightfully easy. Each light operates completely independently to any other, so all are wired separately.

Remove the wires from the PIR unit and discard it. Connect the mains (brown wire) in one of your mains leads to the white wire going to the lampholder, the neutral (blue) to the blue wire and the earth (green/yellow) to the green/yellow wire in the terminal block.

Repeat for the second mains lead and ES base, then fasten the mains leads under the anchor strip provided (there is just room). Screw the assembly onto a suitable piece of timber. Put the top on, screw it all up and put your two PAR38 bulbs into their holders. Connect both mains plugs to a suitable outlet to ensure both lights work.

Repeat all this for the other ES base assembly, check it – and you're ready to plug it into your DSP Musicolour and light up your life. Oh, you did remember you had to build the Musicolour first?



# How To Solder SURFACE-MOUNT DEVICES



*Many electronics enthusiasts hesitate to build projects involving surface-mount devices (SMDs) because they're 'scared' by the prospect of soldering such tiny parts to a PC board. But it can be done; Jim Rowe shows how.*

**IT'S TRUE THAT SMDs** are not really intended for manual assembly. They're designed for automated pick-and-place machines and reflow soldering ovens.

The problem is that more and more ICs and other components are becoming available **only** in SMD form. As technology marches on, it's becoming necessary for everyone to get used to working with SMDs.


You may already be familiar with simple SMDs, like resistors, capacitors, diodes and transistors. Some of these are shown in Fig.1. Note that they're all shown **twice** actual size, for clarity.

We've used these in various projects published in the last few years, and shown how they can be soldered onto a PC board: use a soldering iron with a fine conical or flattened conical tip

and very fine (0.71mm OD) resin-cored wire solder.

How this is done is shown in Fig.2 and Fig.3. The basic idea is to hold the chip or device in place while you tack-solder one or two of its leads to hold it in position. This then allows you to solder all the leads to their pads in the usual way.

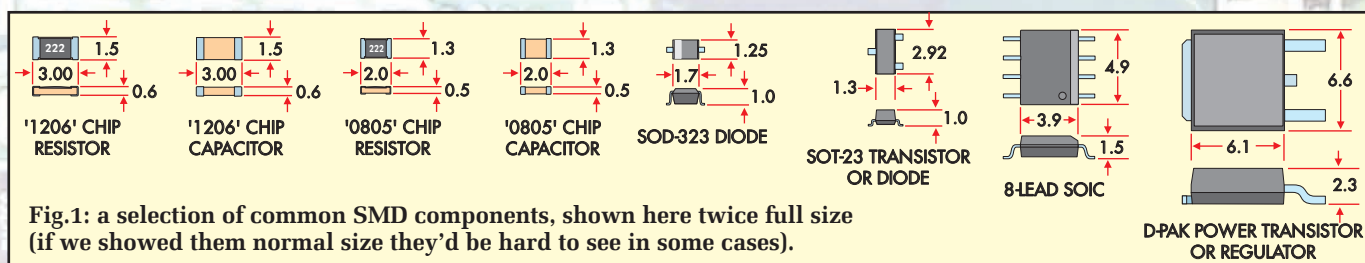It needs to be done very carefully and fairly quickly, so you don't damage either





the SMD or the PC pads by overheating. You also need to make sure you don't apply too much solder, which can cause fine solder 'bridges' to short between copper pads or tracks.

If you do get solder bridges, they can be removed by applying the end of some fine desoldering braid to the top of the 'bridge' and briefly applying the tip of your soldering iron to the top of the braid, so the end of the braid heats up to the solder's melting point and 'sucks up' the excess solder by capillary action.

OK, so what is the real problem with SMDs? Put simply, it's not the resistors, but the large SMDs with umpteen dozen closely spaced pins.

## Fine-pitch ICs

More and more VLSI (very large-scale integration) devices now come in SMD packages, like the one shown opposite and those in Fig.4 – quad flat packs (QFPs) with anywhere between 44 and 208 leads (pins).

The lead pitch can be as fine as 0.4mm – less than 16% of the 0.1-inch/2.54mm pitch used in most familiar dual in-line IC packages.

The width of the leads can also be as fine as 0.18mm (that's right – only 180µm!), so the actual spaces between the leads can be as small as 0.22mm or 220µm.

Now it is possible (just) to solder a 44-lead MQFP device with 0.8mm pitch leads like the IC shown in Fig.4, using a fine-tipped soldering iron and the technique shown on the right in Fig.3.

That's providing you are extremely careful, have a very steady hand and don't mind having to use the soldering braid to remove the almost inevitable solder bridges. If you can do this consistently, then you are a champion!



Close-up view of a 44-lead MQFP device with 0.8mm pitch (lead spacing), after being reflow soldered using a low-cost snack oven.

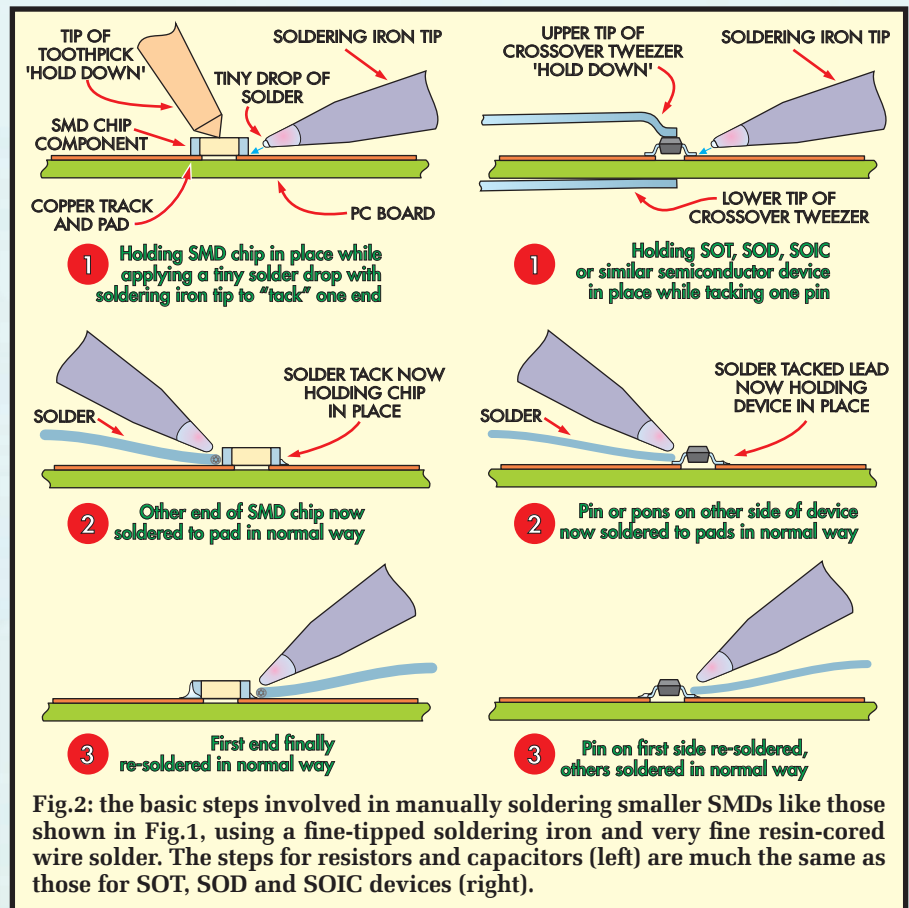


Fig.2: the basic steps involved in manually soldering smaller SMDs like those shown in Fig.1, using a fine-tipped soldering iron and very fine resin-cored wire solder. The steps for resistors and capacitors (left) are much the same as those for SOT, SOD and SOIC devices (right).


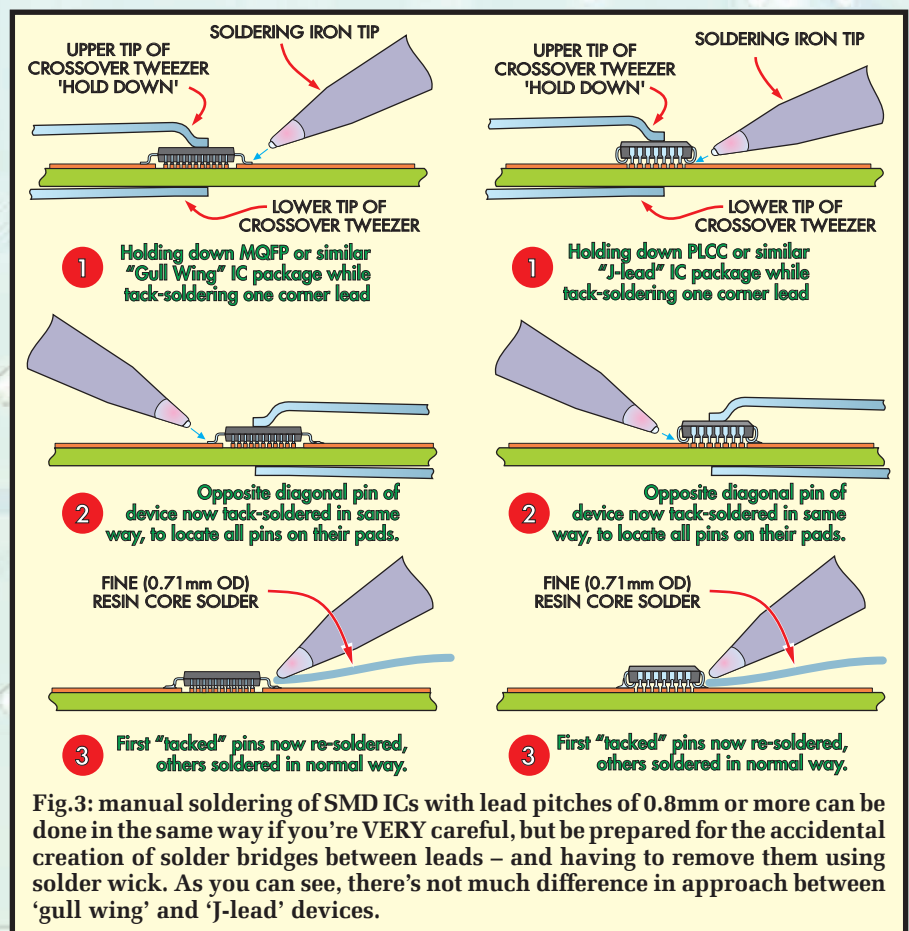


Fig.3: manual soldering of SMD ICs with lead pitches of 0.8mm or more can be done in the same way if you're VERY careful, but be prepared for the accidental creation of solder bridges between leads – and having to remove them using solder wick. As you can see, there's not much difference in approach between 'gull wing' and 'J-lead' devices.

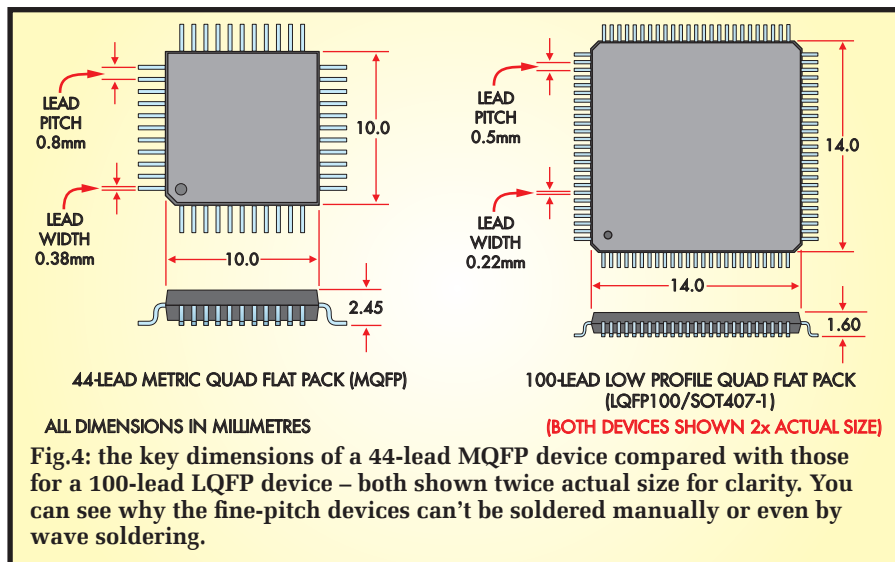

## Constructional Project



The real problem arises when it comes to devices with lead pitches of 0.4mm or 0.5mm, like the 100-lead LQFP device shown in Fig.4. These packages are not even suitable for automated wave soldering, let alone manual soldering. The leads and gaps between them are just too narrow.

### Reflow profile

The only way to solder these devices is by reflow soldering. This process involves applying solder paste to all of the tiny copper pads on the board (using a laser-cut stencil and squeegee system), then placing the SMDs accurately in position on the board. Once the SMDs are in position, the boards are then placed on a conveyor belt and passed through an 'IR reflow oven' at a controlled rate, using infrared radiant heating.

Inside the oven, they move through areas with temperatures set for preheating, followed by a 'ramp up' to above the melting point of solder and then a 'ramp down' to well below the melting point. This is known as a 'reflow soldering profile'.

Using this approach, SMDs with a lead pitch of 0.4mm can be soldered to boards safely and with a high degree of reliability, at the same time as all of the other SMD components.

The main drawback is that a commercial IR reflow oven is very expensive (many thousands of pounds) and thus beyond the reach of

enthusiasts and even many small manufacturers. Getting laser-cut solder paste stencils made from your PC board CAD file is not cheap either.

So, the challenge is to find a much cheaper way of soldering these fine-pitch SMDs on to PC boards. Fortunately, there is a way!

### About solder paste

Solder paste is available from the better electronics stores. It consists of tiny spheres (<50µm in diameter) of tin-lead solder (63% tin, 37% lead), suspended in a water-soluble paste or gel of flux.

It's typically sold in fairly large plastic syringes, holding about 80 grams of solder paste. This is actually far too much for the average enthusiast, because the ingredients in the flux apparently have a shelf life of only six months after manufacture, even when stored in a refrigerator. Yet 80g of paste is enough to solder many hundreds – even thousands – of SMDs.

So, while solder paste is available, it's a pity that it isn't sold in much smaller quantities – say 5g or 10g, resulting in a lot less wastage.

When you buy solder paste, make sure you store it in a refrigerator so you'll at least maintain its six-month working life. Do **NOT** store it in a fridge that is also used to store food. If you must, place the syringe in an air-tight container, because both the solder spheres and the flux give off toxic fumes – see later.




### Applying the paste

As mentioned earlier, large-scale manufacturers use laser-cut stencils and a squeegee system to apply just the right amount of solder paste to every pad on the PC board where an SMD lead or contact area is to be soldered.


This is shown in the upper two diagrams of Fig.5. This technique simply isn't practical for small manufacturers or enthusiasts.

A much simpler approach involves applying a thin 'stripe' of paste along the pads for the SMD leads, as shown in the lowest diagram in Fig.5.

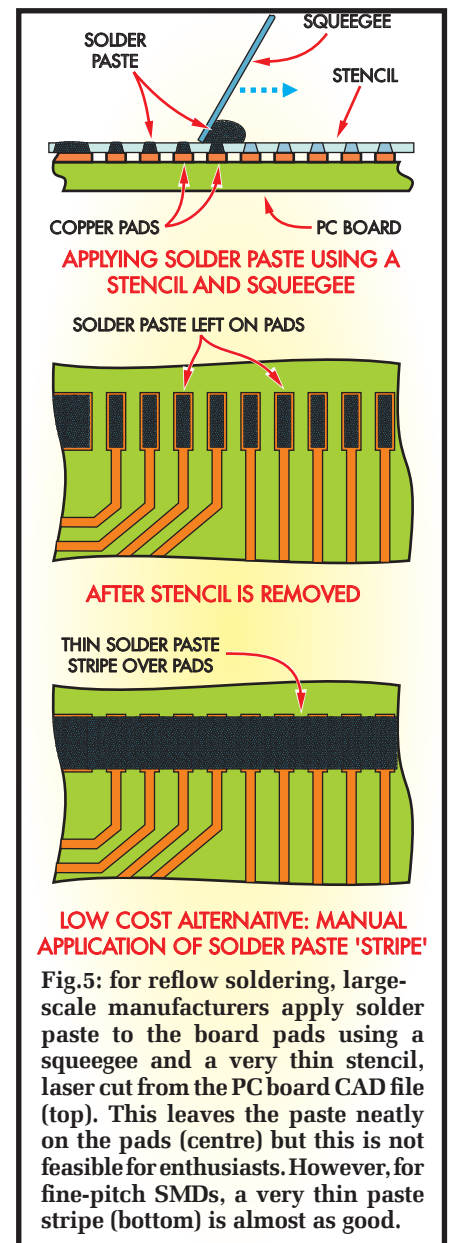
The stripe of paste is only a millimetre or so wide and can be applied using a fine brush, a very narrow roller applicator or a fine spatula with a 1mm wide tip.





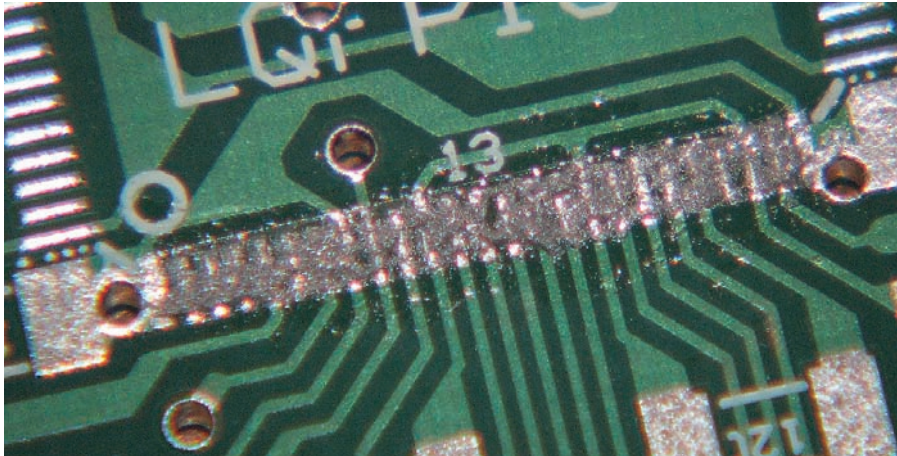

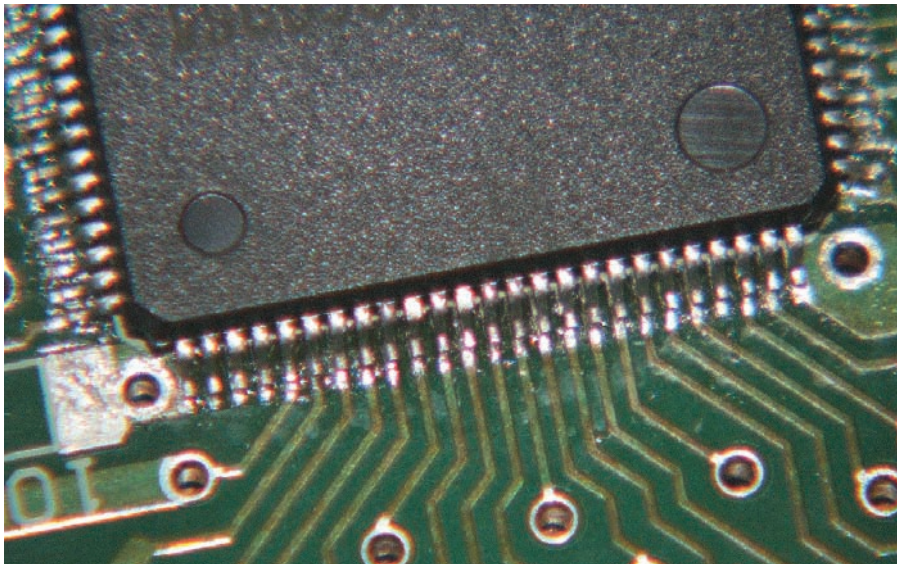Above: a close-up view showing a thin 'stripe' of solder paste applied manually to the pads for one side of a 100-lead LQFP device, with the tiny solder spheres just visible. This stripe is a tad uneven in thickness – a little too thick near the left end, and a little too thin towards the centre.



A close-up of the same board after the device had been reflow soldered using a snack oven. Despite the 0.5mm lead pitch, there were no solder bridges.

You'd think that applying a continuous stripe of solder paste in this way would be asking for trouble because it would form bridges between pads, during the reflow soldering process. However, the secret of this approach is to make the paste stripe very THIN – only about 100µm wide or two solder spheres thick.

If it's no thicker than this, the result is that surface tension and capillary action cause the solder spheres to 'pull themselves together' into the gaps between each SMD lead and its board pad, when they melt during the reflow soldering. As a result, most of the solder spheres in the paste between the pads get sucked into the molten solder directly under each SMD lead, leaving very few to form bridges.

### Not too thick, not too thin

If you make the paste stripe too thick, there WILL be enough spheres left in the gaps between pads to form bridges.

On the other hand, if you make the stripe too thin, there will be insufficient spheres to pull together and form a good bond between each SMD lead and its pad underneath. So, erring in

this direction results in 'missing joints' after the reflow soldering process – not at all easy to repair!

The most important thing about this manual approach to applying the solder paste is to take your time and to make the stripe width as you can. It's easiest to do this with the board under a magnifier lamp or even a low-power stereo microscope with illumination.

I've also found that a very thin and narrow-tipped (about 1mm) spatula seems to make it easier to apply and even-up the paste stripe, although a very narrow 'applicator wheel' (I made one myself) was almost as good and much easier than a fine brush.

Whatever you use, the main ingredient is time and patience – applying solder paste is a bit like trying to spread microscopic caviar evenly on a sheet of glass.

In fact, since you have plenty of paste, do a few dry runs on a sheet of PCB copper laminate.


### Placing the SMDs

Once the solder paste has been applied to the board, you can place your fine-pitch SMD(s) in position, with their leads over the board pads, ready for the reflow soldering process.

Large-scale manufacturers use a pick and place machine to position all of the components on the board in one pass – not just the fine-pitch SMDs, but everything else as well. Then all parts can be soldered to the board in a single pass through the reflow oven. But that's not really feasible if you're placing all of your components manually.


Our method is to place the fine-pitch ICs on the board first, then do their reflow soldering. After the board cools down you can then inspect the results, and if all is well you can proceed to solder in the rest of the components one by one, using the fine-tipped soldering iron approach illustrated in Fig.2 and Fig.3.

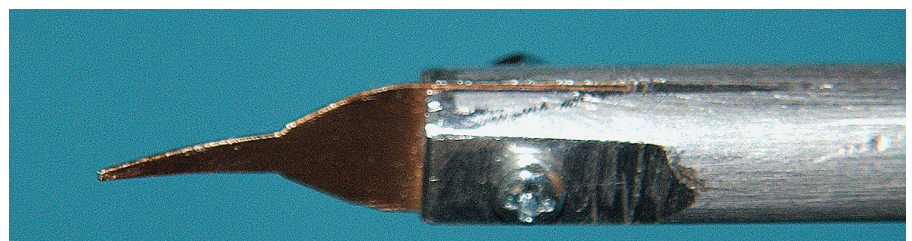You may be wondering how accurately you have to place the fine-pitch IC packages in position, before reflow



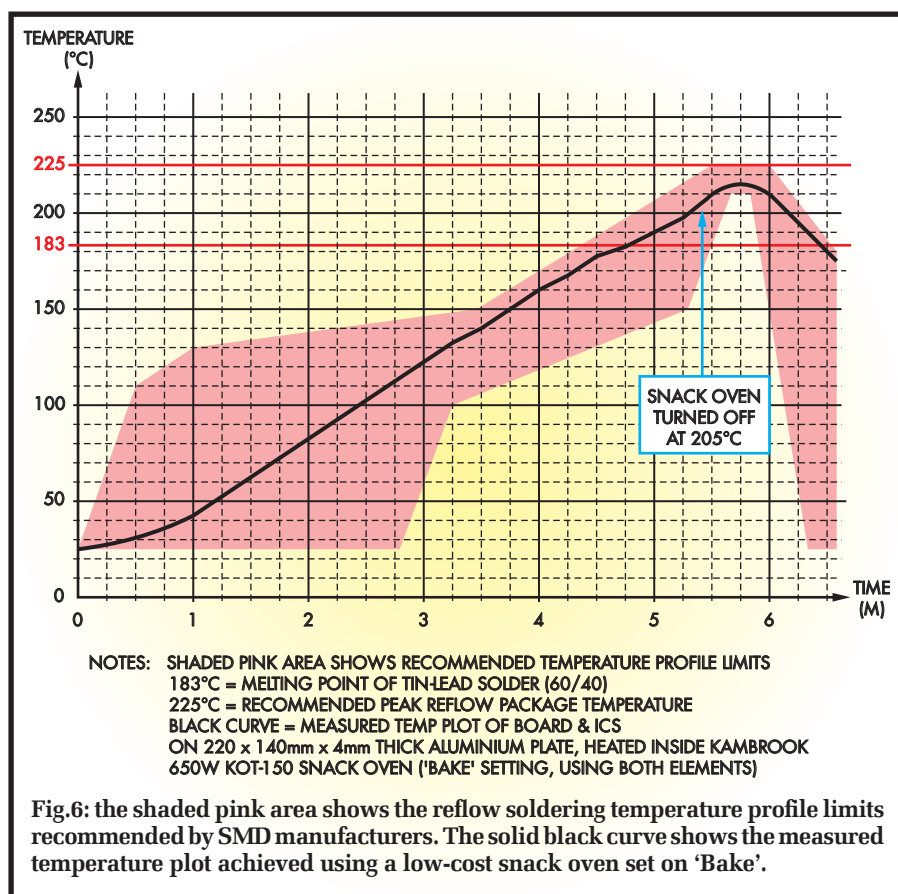The business end of a 'mini spatula' made by the author for applying a stripe of solder paste on pads for fine pitch SMDs. It's shown here about 3× actual size.





soldering. The answer is placed fairly accurately, but not fanatically so. The main thing is to make sure that every device lead is over its corresponding PC board pad and closer to that pad than it is to any other pads nearby.

If you achieve that, when the solder spheres in the paste melt and coagulate during the reflow process, surface tension and capillary forces in the molten solder will automatically 'pull' all the leads centrally into position over their pads.

So, the idea is to carefully lower the IC package (orientated correctly, of course) into position using a 'vacuum pick-up tool' or similar, and then nudge it gently into the correct position using a fine jeweller's screwdriver or pick tool. Again, it's easiest to do this under a magnifier lamp or stereo microscope, preferably one where you can rotate the board and IC until you're happy that all leads are over their pads on the board.

Once all the fine-pitch SMDs have been placed carefully in this way, your board will be ready for reflow soldering. Be very careful not to bump or jar it, because the SMDs could easily be jolted out of position.

### Reflow soldering

Now, how do we do the actual reflow soldering? If you use an online search engine to track down info on reflow soldering, you'll find that quite a few people have tried doing it with an electric frypan or skillet.

The basic idea is to place the PC board in the centre of the frypan, applying power until the solder paste clearly melts and flows under each SMD lead. You then turn off the power and allow it all to cool down.

This can work – but there is a big risk of scorching the underside of the PC board; inevitably the underside of the board must be raised to a temperature considerably higher than the melting point of solder.

This board-overheating problem tends to be made worse because the heating element in the underside of most frypans is circular in shape. This produces uneven heating of the PC board, with a cooler region in the centre, surrounded by a ring of heat.

So, depending on the location of your fine-pitch SMDs on the board, the reflow operation can easily result in a ring of scorching on the underside of the board. The result is a totally

unusable board, and the SMDs won't be salvageable either.

### Get an old frypan

If you decide to try the frypan approach, ***please don't use a frypan that is also used for cooking food.***

The fumes given off by solder paste during the reflow process are quite toxic and are likely to be absorbed by the frypan metalwork and/or Teflon coating. So the toxins may well be transferred into any food cooked in the frypan afterwards.

Buy a cheap frypan specifically for the job, and mark it clearly **'NOT TO BE USED FOR COOKING FOOD'**.

Because of the toxic fumes given off during reflow soldering, it's also very desirable to do it in a well-ventilated area – preferably outdoors. This applies regardless of whether you use a frypan or some other heating device.

Having read the references on the web about reflow soldering using a frypan, I decided to try it, but with a slightly different approach.

I bought a cheap frypan, then did a few experiments with it. To try getting around the board scorching problem, I cut a 'heat spreader' plate from 4mm thick aluminium sheet and placed this in the centre of the frypan with my test board sitting on it.

This did seem to make the heating fairly even, but there was still a major problem. Even with the frypan's thermostat set for maximum, the temperature on the top of the PC board never reached the melting point of solder (183°C), let alone the 215° level that is necessary to ensure good reflow.

Presumably, the small air gap between the bottom of the frypan and my spreader plate added too much thermal resistance. I removed the spreader plate and tried again, with the board placed directly on the bottom of the frypan.

This time the temperature on the top of the board did reach about 210°C and reflow took place. However, when it had cooled down, I noticed that the underside of the board had been scorched in areas that had been directly over the circular heating element.

So, reflow soldering with a frypan is just not worth the risk of PCB damage.

### In the oven

Another 'cheapo' reflow technique that you'll come across on the web

involves the use of a small electric 'snack' or toaster oven. Almost all these use a pair of heating elements, one at the top of the oven compartment and the other at the bottom.

Whatever you're going to heat up in the oven goes on a tray supported by a wire mesh 'drawer' in the centre, which is linked to the oven door so it slides in or out when the door is closed or opened.

Often, there's a switch which allows you to select either the top element (Grill) or the bottom element (Reheat) or both at the same time (Bake). Each element draws about 325W, so the oven uses about 650W when both are used together. Since the reflow operation only involves drawing this power for five or six minutes at most, this isn't a problem.

The main advantage of using this kind of snack oven for reflow soldering is that the heating is done by infrared radiation, on the top of the board as well as from below, just like a 'proper' IR reflow oven. The main difference is that your board stays fixed in the oven during the whole process, rather than moving through different temperature regions on a conveyor belt.

This means that you have to arrange for the reflow temperature profile to be provided in some other way. This turns out to be easier than you would think.

I decided to try the snack oven approach for myself, so I bought a Kambrook KOT-150 snack oven which cost just £20. It has no thermostat – just an electromechanical timer and the element selector switch. But the lack of a thermostat is not a problem, and the timer didn't turn out to be all that necessary either.

### First bake

My first test with the snack oven was to clamp a thermocouple temperature probe onto a test board, which was then placed in the small pressed tinfoil tray that came with the oven. The tray was then placed on the oven's sliding mesh drawer and the oven door closed carefully so that the thermocouple lead could exit through a small gap at the top of the door.


The oven was set to 'bake' (both elements on) and the timer knob set to apply power for about 10 minutes. I then proceeded to take temperature measurements every 15 seconds.



Here's the setup we used to successfully reflow solder fine-pitch SMDs. The board assembly is clamped on a 220 × 140mm plate of 4mm-thick aluminium plate, with a thermocouple probe clamped to the board copper near the 100-lead device. Shortly after this shot was taken the snack oven was turned on and then turned off as soon as the digital thermometer reading hit 205°C.

The resulting temperature characteristic turned out to be very close to the solid black curve in Fig.6, which also shows (shaded pink area) the reflow temperature profile limits for fine-pitch SMD IC packages recommended by chip manufacturers like NXP/Philips.

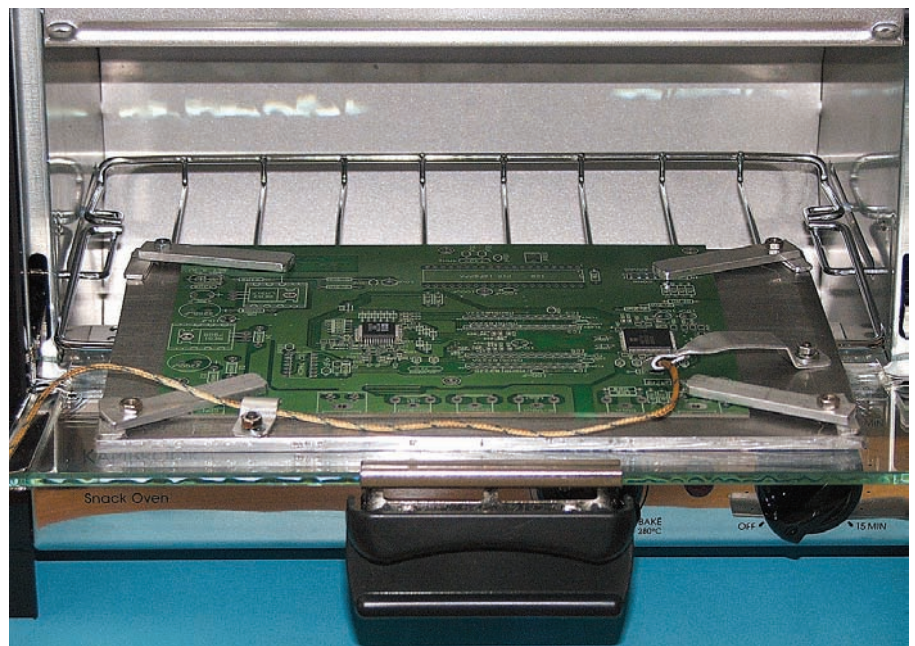As you can see, the warm-up characteristic is nicely within the recommended limits. By turning off the power to the oven when the temperature on the top of the board just reached 205°C, the board temperature coasted up nicely to a peak of 215°C and then began to coast down again. It



As soon as the temperature coasted down to about 165°C, the door of the snack oven was carefully swung down to allow the entry of more air to speed up the cooling. Both SMDs on this board had been reflow soldered very nicely, with no solder bridges between leads or pads. The board had not been damaged in any way either, so we can recommend the snack oven approach.



## Constructional Project



**It's not elegant but it works: an SMD chip baking oven, made by converting a discarded blower heater. The reflector part of the heater was flattened and bent into a small rectangular oven shape, then re-attached to the front of the blower heater element (just visible through the opened front door).**

dropped down below the 183°C solder melting point temperature about 6.5 minutes after switch-on, so after waiting about one more minute, I carefully opened the door and drawer to allow cooling to occur more rapidly.

When the test board had cooled right down, I took it out of the tray and checked underneath to see if there had been any scorching. There was none at

all – even the silk screen printing on the underside of the board showed no discolouration.

### Trial run

Encouraged, I decided to carry out a reflow soldering test on another PC board. This was prepared with solder paste stripes around the pads for a fine-pitch IC, and then an SMD

device was carefully placed over these pads. It was here I made my first mistake.

In an effort to make the process a little more controlled, I drilled four 3mm holes in the oven's tinfoil tray, so the board could be fastened into it using four M3 machine screws and nuts. One of the screws was also used to attach the clamp for the thermocouple probe, to hold the probe securely in position with its bead in contact with the board's top copper close to the SMD chip.

The board and tray were carefully placed on the oven's mesh drawer and the oven door gently closed so they slid smoothly inside. Then power was applied to the oven again and the top-of-board temperature was checked every 15 seconds as before.

All went well, with exactly the same temperature profile as before. But then, just as the temperature reached about 200°C (just before I would turn off the power), there was a 'ping' sound – apparently the tinfoil tray had been under stress as a result of the board being bolted inside and the stress was relieved suddenly when the temperature reached 200°.

Having turned off the power as soon as the temperature reached 205°, I waited impatiently while the

### Ten Tips for successful DIY reflow soldering of SMDs

1. Store your solder paste in a sealed container in a fridge, to prolong its useful life.
2. Take care to apply the solder paste in a 'stripe' along the centre of the SMD lead pads on the PC Board, with the stripe no more than about 1.5mm wide and (most important) very thin – no more than about 100µm or two solder spheres. As even in thickness as you can make it, also – no lumps or voids.
3. Use a small snack oven for reflow soldering. Clamp the PC board on the top of a flat heat diffusion support plate made from 4mm thick aluminium sheet, say 220mm x 140mm in size (to fit comfortably in the snack oven). Also monitor the temperature on the top of the board near one of the SMDs, using a thermocouple probe connected to a digital thermometer.
4. Place the SMD chip(s) in position on the board carefully, with all leads as near as possible to their corresponding board pad. You don't have to be fanatical about this though: the chips will auto-locate during reflow, providing each lead is closer to its own correct pad than to the pads on either side.
5. Place the board and its support plate on the oven's slide-out drawer very carefully, so as not to bump or jolt the SMDs from their positions. Then carefully close the oven door so they slide smoothly into the oven – again without jarring.
6. Use both the upper and lower heating elements of the oven for reflow solder heating. This is usually achieved by selecting the Bake setting. Using both elements gives more even heating, closer to that in a proper IR reflow oven.
7. Switch on the oven, monitoring the temperature on the top of board using the thermocouple probe and digital thermometer. The temperature should rise fairly smoothly, reaching the melting point of tin/lead solder (183°C) in just under five minutes. Take care not to bump or jar the oven after this.
8. As soon as the temperature reaches about 205°C, turn off the oven power without bumping anything. The temperature will continue rising, to reach a peak at around 215°C to 220°C. It should then begin falling again.
9. Wait until the temperature drops below the melting point of solder – say down to about 165°C. Then it should be safe to open the oven door so the drawer and its contents slides out, to speed up further cooling.
10. When the board has cooled down to around room temperature, remove it from the support plate and check the solder joints on all SMD leads with an illuminated magnifier or stereo microscope. If there are any solder bridges, these can be cut away using the tip of a hobby knife or 'sucked' off using desoldering braid and a fine-tipped soldering iron.

temperature peaked again and crept downwards once more. Once it had dropped to about 165°C I carefully opened the door, so the drawer and tray slid outwards.

Then I examined the SMD chip with a magnifying glass, only to discover that the stress relief 'ping' at 200°C had caused the SMD chip to be jolted out of position. The reflow soldering had actually occurred quite nicely but with the chip and its leads in the wrong position.

## On the plate

However, the overall result still confirmed that the snack oven was quite suitable for reflow soldering. I decided to make a much sturdier PC board support plate, to replace the flimsy tinplate tray. The new plate was a 220 × 140mm rectangle of 4mm-thick aluminium plate and had a 3mm hole drilled near each corner, for the board hold-down clamp screws.

The holes were countersunk underneath so that countersink-head screws could be used to hold down the board, without producing bumps underneath the plate. This was to make sure that the plate and board could be moved smoothly on the oven's mesh drawer.

Another board was prepared with solder paste and a fine-pitch SMD chip placed carefully in position. Then the board was clamped to the top of the new support plate, the thermocouple probe fitted and the complete assembly placed inside the oven.

This time, everything went really well. There were no 'pings', the solder reflowed nicely, and when it all cooled down again, a board inspection showed that the SMD chip had settled itself in the correct position and was nicely soldered. And there were no solder bridges!

So, we are able to report that reflow soldering of fine-pitch SMD chips can be done successfully using a low-cost snack oven like the one shown in the pictures. Listed on the page opposite are the 10 important 'rules of thumb' when it comes to using a snack oven to reflow solder fine-pitch SMD chips. If you follow these rules carefully, success is almost guaranteed.

Finally, what about using a 'fan-forced' snack oven? **Not** a good idea! The fan could easily blow the SMDs out of position!

EPE

## Footnote: About MSL Rating

If you're going to be using reflow soldering for SMDs in plastic packages, you should know a bit about the way these devices are rated in terms of MSL or 'moisture sensitivity level'.

Basically, it has been discovered that SMDs in plastic packages have a tendency to absorb moisture when they're stored in typical 'shop floor' or workshop conditions for any significant period of time. The degree of moisture absorption depends on a variety of factors – including the size of the device package, the number of leads and the relative humidity level in the storage environment.

The problem is, that when SMDs are heated up during reflow soldering, this absorbed moisture tends to turn into steam and build up sufficient pressure to cause cracking and other damage inside the package. It can easily damage the chip inside and/or its bonding wires, even if no cracks are visible on the outside of the package.

To minimise the risk of this kind of damage during reflow soldering, chip manufacturers nowadays bake most plastic-package SMDs (especially those in fine-pitch packages) for many hours at 125°C in a very dry and inert atmosphere, to drive out any moisture. Then they are sealed in hermetic packaging (dry packs) and the idea is that they should be left in this packaging until just before they're subjected to reflow soldering.

Now, because this last-minute unpacking isn't practical, even for big manufacturers, and in any case isn't really necessary for some devices, semiconductor industry standards bodies like JEDEC (formerly the Joint Electron Device Engineering Council) have established a system whereby each device is given a rating to show how long it can be safely left out of its hermetic packaging in a typical 30°C/60%RH workshop or factory

environment, before reflow soldering. There are eight of these MSL rating levels, ranging from MSL 1 for packages which are deemed impervious to moisture, up to MSL 6 for packages which are very sensitive to moisture and must be reflow soldered within no more than six hours after being removed from their dry packs.

You'll find this MSL rating printed on the dry packs of most SMD devices in plastic packages, and certainly for those in fine-pitch packages (which are almost always rated at MSL 2 or higher). The table below shows the significance of the various MSL levels.

So, what do you do if you want to reflow solder an SMD with an MSL level of 2 or higher, and you know it has been out of its hermetic packaging for longer than its rated safe time? Alternatively, what if it hasn't been out for that long, but has been subjected to very high relative humidity?

The good news is that it can be restored so that it can be safely reflow soldered by baking for about 24 hours at a controlled temperature of between 115°C to 125°C. This can be done in a small fan-driven hot-air oven, provided the device is placed in a small metal box to ensure even heating. The box should also have some small vents to allow the escape of any moisture that is released during the baking.

I made up a small baking oven by converting a fan-type room heater that had been dumped at council clean-up time. The fan motor, fan and heating element were all in perfect working order, as was its thermostat switch.

So, all I had to do was remove these components and convert the heater case into a recirculating-air oven. Then the 'works' were reinstalled and the thermostat tweaked to cycle the oven temperature around 118°C, which produced a rough but quite serviceable DIY baking oven for plastic package SMDs.

### JEDEC MOISTURE SENSITIVITY LEVEL (MSL) RATINGS

MSL rating	Safe exposure time at ≤ 30°C/60%RH before reflow soldering
1	Unlimited (non moisture sensitive)
2	1 year
2a	4 weeks
3	1 week (168 hours)
4	72 hours
5	48 hours
5a	24 hours
6	6 hours (extremely moisture sensitive)



# ColdAlert Hypothermia Alarm

By DAVID CLARK

**A low-cost PIC-based alarm to help an elderly or vulnerable person stay warm.**

USE the ColdAlert as an excuse to turn up the central heating! Or perhaps, more seriously, use it as a hypothermia alarm to help an elderly or vulnerable person stay warm over the winter months. The ColdAlert hypothermia alarm is a smoke-alarm-style low temperature detector, with a fixed alarm threshold. It will give an audible and visual indication of low temperature, and features a built-in test facility.

For most people, keeping warm is simply a matter of turning up the heating when they 'feel a bit chilly'. Some people, however, cannot tell when they are getting too cold, and these individuals are at risk of hypothermia. This is a condition where the body's core temperature falls below 35°C, and it can be fatal.

Elderly people are particularly vulnerable as there can be a reduced perception of cold accompanied by a lack

of shivering due to underlying health conditions, and their room temperature should be kept above 18.3°C. This hypothermia alarm addresses the problem by giving a visual and audible indication of an ambient temperature of below a nominal 19°C.


### In use

The device is designed to be used like the familiar smoke alarm found in many homes. Once running, it can be ignored other than by doing a simple check, ideally every day, to ensure that the battery is not discharged, and that the device is working. Similar to a smoke alarm, this is achieved by just a press of a 'Test' button, followed by checking that two light-emitting diodes (LEDs) light and that a buzzer sounds.

In normal operation, a green LED lights up for about a half a second every minute, indicating that all is well and that the ambient temperature is above 19°C. If the temperature falls below this level, a red LED will light and a buzzer sound, both at a frequency of about once per second.
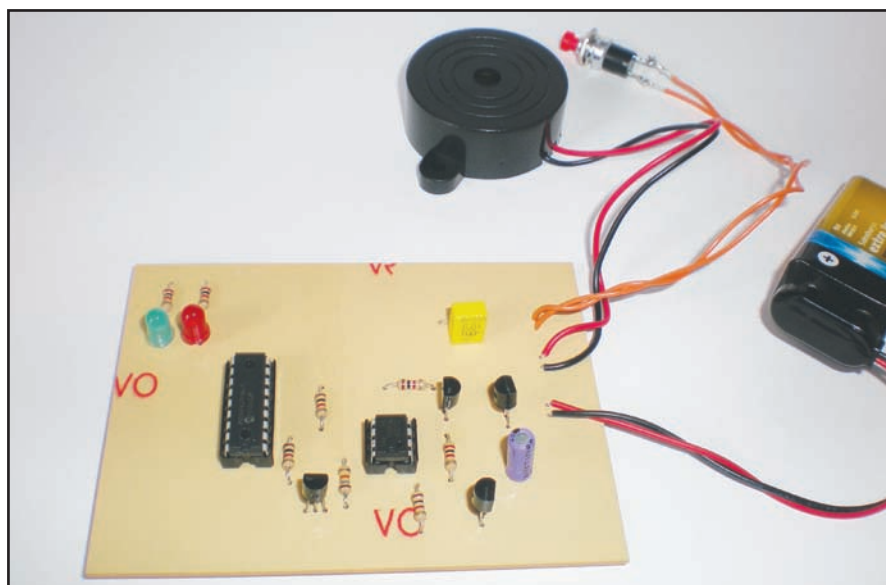
### Circuit brief

The full circuit diagram for the ColdAlert Hypothermia Alarm is shown



## Parts List – ColdAlert Hypothermia Alarm

- 1 PC board, code 761, available from the *EPE PCB Service*, size 100mm × 75mm
- 1 case, type and size to choice (optional)
- 1 pushbutton switch, push-to-make (S1)
- 1 3V to 15V wire-ended piezo buzzer (WD1)
- 1 9V battery, with snap-on clip and leads
- 3 2-way PC-mount terminal blocks (TB1-TB3 optional)
- 1 8-pin IC socket (IC2)
- 1 18-pin IC socket (IC4)

Multistrand plastic-covered connecting wire; solder pins; solder

### Semiconductors

- 2 2N3904 NPN low-power transistors (Q1, Q2)

- 1 LM35DZ centigrade temperature sensor (IC1)
- 1 TS921N CMOS rail-to-rail op amp (IC2)
- 1 LP2950 +5V low-power voltage regulator (IC3)
- 1 PIC16F627 preprogrammed microcontroller (IC4)
- 1 5mm or 3mm red LED (LED1)
- 1 5mm or 3mm green LED (LED2)

### Capacitors

- 1 2.2μF 100V radial elect. (C1)
- 1 10nF polyester (C2)

### Resistors (0.25W 1% carbon film)

- 4 1kΩ (R1, R4, R5, R6)
- 3 2kΩ (R2, R8, R9)
- 1 10kΩ (R7)
- 1 18kΩ (R3)

this is multiplied by a factor of ten by an op-amp (IC2) in a non-inverting amplifier configuration to give the microcontroller a reasonable signal to work with. The 100mV/°C signal passes to one input of the microcontroller's comparator module (at pin 2); the other input of the comparator is fed with an internally-generated voltage from the microcontroller's voltage reference module.



Under software control, this reference voltage is set to 18.9°C when there is no alarm condition, and 20.5°C when there is an alarm condition, in order to provide hysteresis and prevent unwanted 'flip-flopping' between alarm and no-alarm when the ambient temperature is crossing the alarm threshold value. This is illustrated in Fig.2.

The microcontroller also takes care of switching on and off the green 'OK' LED, the red 'ALARM' LED, and the buzzer, as appropriate, as well as the timing for these events.

in Fig.1. At the heart of the project is a PIC microcontroller (IC4) and a temperature sensor.

The LM35 temperature sensor (IC1) provides an output of 10mV per °C, and

**Fig.2. Hysteresis effect at the alarm trigger and alarm clear points**

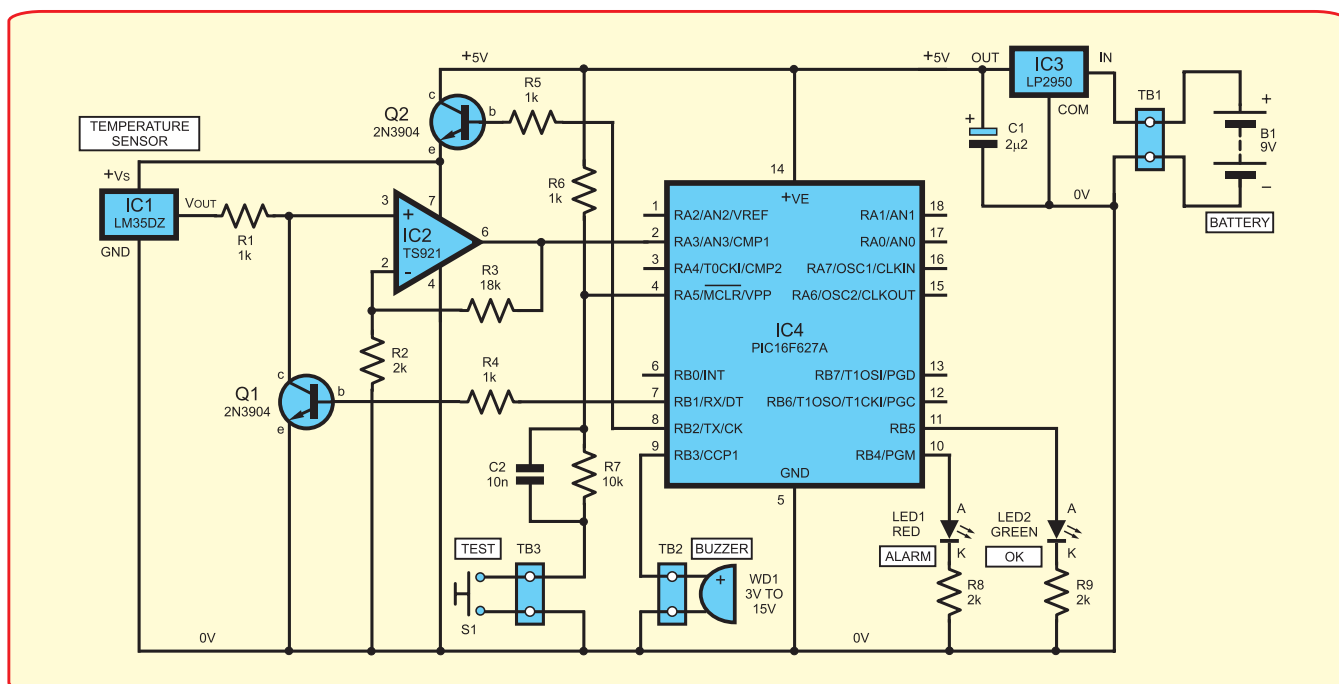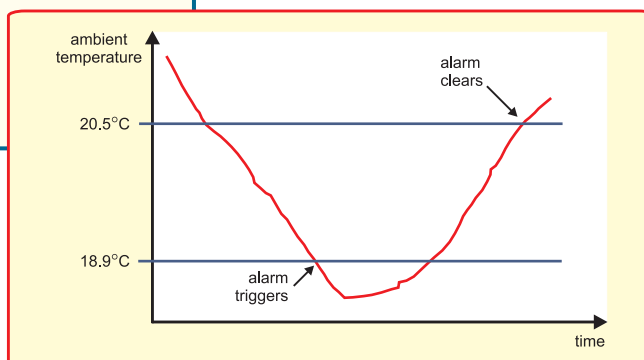

**Fig.1. Complete circuit diagram for the ColdAlert Hypothermia Alarm**



## Alarm test

In order to give confidence that the ColdAlert hypothermia alarm is working properly without having to put it somewhere cold, a built-in alarm test is provided. This works by shorting the output of the temperature sensor to 0V (via a resistor), thus simulating a genuine low ambient temperature and not merely setting a software-generated alarm.

When the 'Test' button is pressed, a two-part check is instigated. The microcontroller is reset via the MCLR (negative logic) pin, and it begins its software routine from the beginning. Components C2 and R7 ensure that pressing the test button causes a reset pulse and does not hold the microcontroller off for as long as the button is held pressed.

After the usual initialisation of microcontroller modules, the next section of the software includes instructions that switch on both LEDs and the buzzer for approximately two seconds – the user must satisfy him- or herself that both LEDs light and that the buzzer sounds. If all is satisfactory, the 'output' part of the alarm is fine. If this is not the case, there is a fault with driving these devices, or an actual device, and the hypothermia alarm must not be used.

Next, again under software control, transistor Q1 is switched on, which generates a simulated low temperature output from the temperature sensor. After two seconds has elapsed, the software tests to see if the internal comparator has generated an alarm; if it has, the 'input' part of the alarm is working, and the software switches Q1 off and proceeds to its main loop, the normal working condition.

If the comparator has not generated an alarm, the software goes into an unending loop and does not proceed to the main loop; both LEDs and the buzzer remain on; in other words, the faulty system cannot be used. The whole cycle can be repeated from the beginning at any time by repressing the 'Test' button.

## Normal operation

The main loop takes care of normal operation, which is a temperature check once every minute approximately. If the temperature is higher than the safe threshold, the green LED will

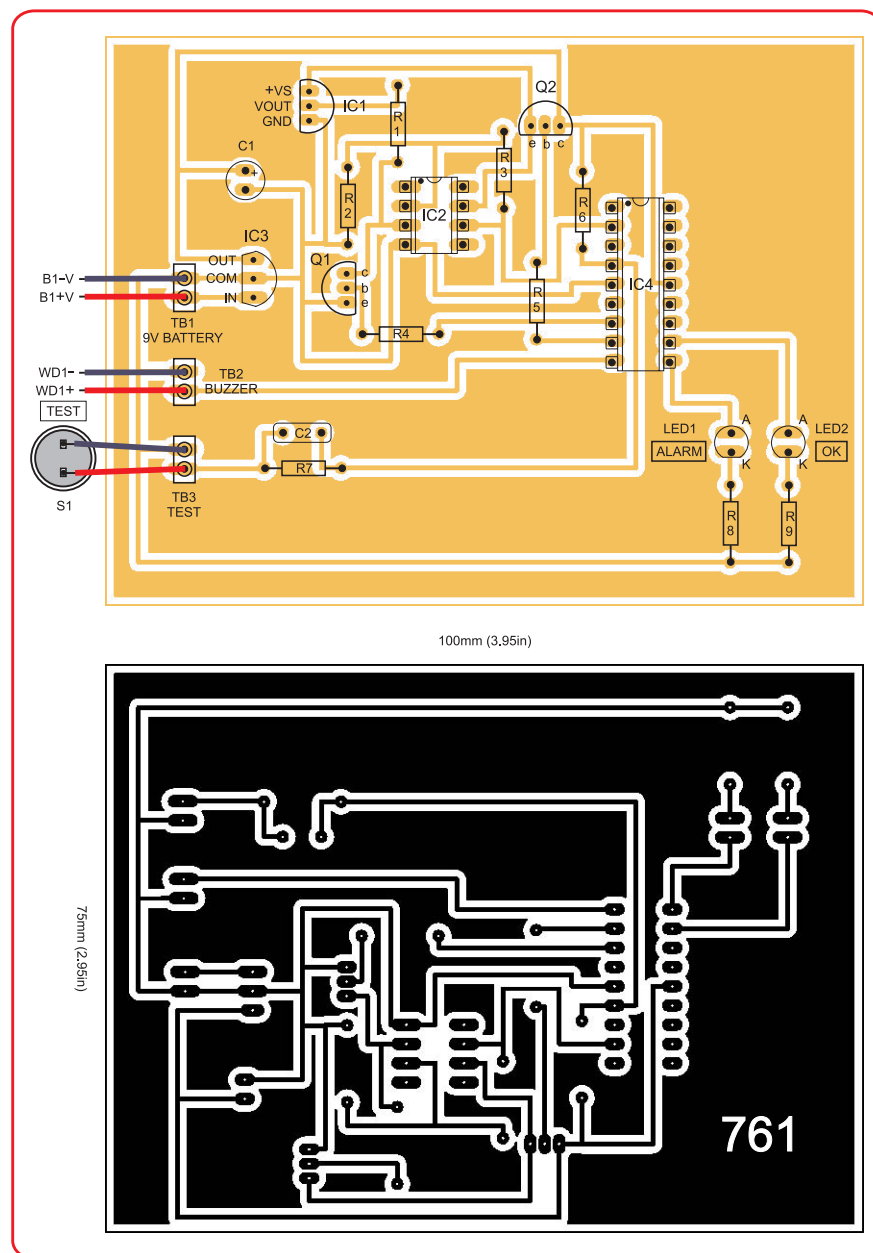


Fig.3. Printed circuit board topside component layout, off-board lead-off details and full-size underside copper master

light for half a second; if it is lower, the red LED will light and the buzzer will sound, as described earlier.

The main loop also takes care of adjusting the voltage reference in order to generate the hysteresis effect already described. As part of normal operation, timing loops are called where necessary, not only for timing the relatively long periods required for operating the LEDs and buzzer, but also shorter 'settling' times for the external temperature sensor and transistors, and internal microprocessor modules.

## Micropower

An important aspect of battery-powered equipment that must be permanently switched on is minimising energy consumption. In the ColdAlert hypothermia alarm, this matter is addressed through three factors. First, extensive use is made of the PIC microcontroller's 'sleep' mode for timing delays.

Second, the supply voltage to the temperature sensor and op-amp is switched off (via transistor Q2) between readings. Finally, a micropower LP2950 voltage regulator (IC3)

is used instead of the more common 7805.

### Battery life

Regarding battery life, an alkaline PP3 battery has a capacity of typically over 500mAh, a lithium version even more. With the hypothermia alarm, current consumption was measured (with a digital multimeter) at around  $200\mu\text{A}$  (when in 'no-alarm' state and with the 'OK' LED off), battery life could be in the order of 1000-plus hours. This might be greatly extended by using, for example, six alkaline or lithium AA batteries (well over 2000mAh).

The use of a low-current LED for the green 'OK' indicator will reduce overall power consumption a bit more, as will increasing the value of resistor R3, but the trade-off is, of course, that the LED will be less visible. There is probably little point in going to great lengths to reduce power consumption in the 'alarm' LED and buzzer, as overall current consumption will be much higher in an alarm condition anyway. Also, hopefully, alarm conditions will be rare.

### Software


A comprehensively annotated software listing (.asm) is available from the *Everyday Practical Electronics* Library site, accessed via [www.epemag.com](http://www.epemag.com), along with the hex (.hex) file. A preprogrammed PIC will be available from Magenta Electronics – see their advert in this issue for contact details.

### Construction

The ColdAlert hypothermia alarm is built on a small single-sided printed circuit board (PCB), which is available from the *EPE PCB Service*, code 761. The topside (component layout) is shown in Fig.3, together with the full-size copper foil master pattern.

Construction is straightforward, the main consideration being the correct orientation of the integrated circuits (ICs), transistors and LEDs, and the correct polarity of the connections to the battery and buzzer.

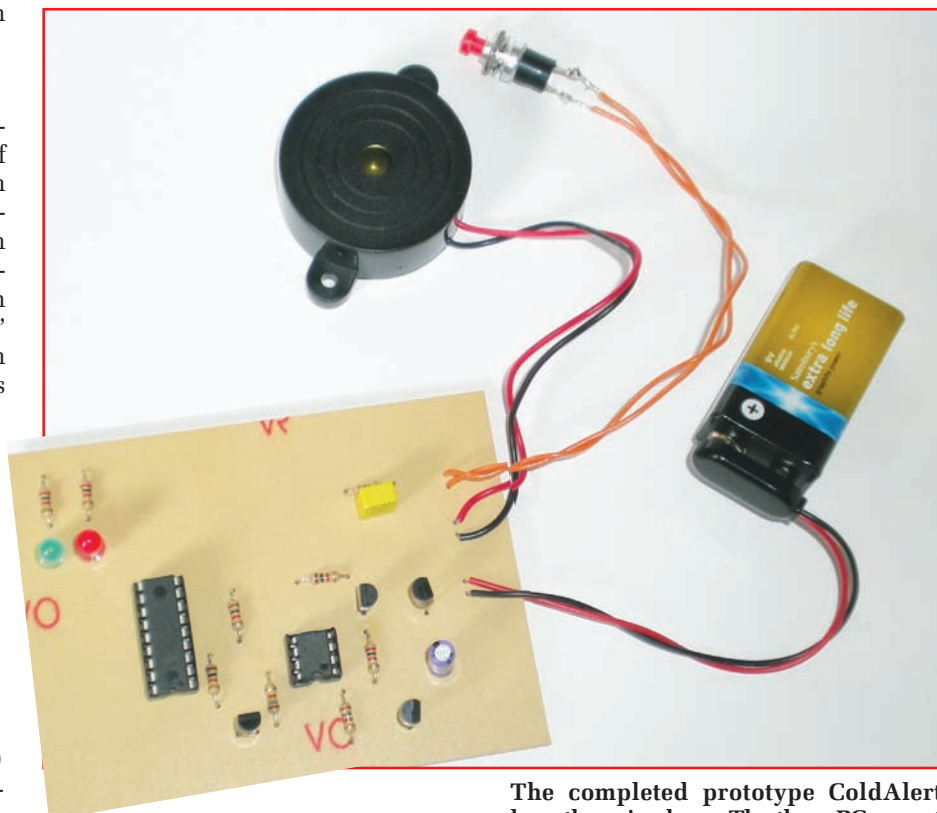The op-amp (IC2) and PIC (IC4) are best mounted in IC holders, particularly the PIC, in case it needs reprogramming for any reason, or if you want to modify the code. In any event, the semiconductors should be fitted last to minimise the possibility of electrostatic damage.



### In case?

There are some problems that need to be considered if you want to fit this project in an enclosure. Most importantly, there needs to be a free flow of air around the temperature sensor (IC1) for it to react as quickly as possible to temperature changes.

Also, the PCB connections to the sensor and the LEDs will need to be extended via wire leads, which will increase the possibility of short circuits or broken connections, naturally making the alarm ineffective. However, it looks neater!

### Finally

There are well over 100 deaths a year in the United Kingdom due to hypothermia in the elderly. Hopefully, the ColdAlert will help prevent this tragic outcome of not being warm enough at home. However, please remember – this is a hobby project and not a medical device. Use it as an

The completed prototype ColdAlert hypothermia alarm. The three PC-mount terminal blocks in the component overlay diagram are optional

AID to, NOT as a substitute for, proper medical and social supervision of a vulnerable person.

Like a smoke alarm, the hypothermia alarm is a preventative device, and, like a smoke alarm, it will be doing its best job if its alarm never sounds – but don't forget to test the alarm at regular intervals.

Source of hypothermia information – *Merck Manual of Geriatrics* website: [www.merck.com/mkgr/mmg/sec8/ch67/ch67b.jsp](http://www.merck.com/mkgr/mmg/sec8/ch67/ch67b.jsp).

**Laser**  **Why tolerate when you can automate?**

 **Home Automation**

 **KAT5 AV transmission and IR control system**

 **Barix Ethernet based MP3, communications and control systems**

[www.laser.com](http://www.laser.com)

**Integrators, Installers, Trade and Retail customers welcome**

 **C-Bus Shop**  
**C-Bus and C-Bus Wireless**

[www.cbushop.com](http://www.cbushop.com)

**Laser Business Systems Ltd**  
Tel: +44 (0) 20 8441 9788  
Fax: +44 (0) 20 8449 0430  
Email: [info@laser.com](mailto:info@laser.com)  
16 Garthland Drive, EN5 3BB



**EPE  
EXCLUSIVE**

# Win a Microchip PICKit 3 Debug Express Kit!

**Have you read the review (*EPE* June 10)  
and would like your own kit?**

**E**VERYDAY PRACTICAL ELECTRONICS is offering its readers the chance to win one of four new MPLAB PICKit 3 Debug Express kits from Microchip. The PICKit 3 Debug Express allows debugging and programming of PIC and dsPIC Flash microcontrollers at a low price point, using the powerful graphical user interface of the MPLAB Integrated Development Environment (IDE).

The PICKit 3 Debug Express works with 8- and 16-bit PIC MCUs and dsPIC digital signal controllers (DSCs), and will support 32-bit PIC MCUs at a later date.

The PICKit 3 Debug Express kit includes:

- PICKit 3 debugger and programmer probe
- 44-pin demo board populated with a PIC18F45K20 MCU
- Free MPLAB IDE
- Free version of the MPLAB C Compiler for PIC18 MCUs.

All this is supported by easy-to-understand lessons and tutorials, and a host of other software utilities, examples with source code and full documentation.

## HOW TO ENTER

For your chance to win a PICKit 3 Debug Express Kit, visit: [www.microchip-comps.com/epe-pickit3](http://www.microchip-comps.com/epe-pickit3) and enter your details in the online entry form.

## CLOSING DATE

The closing date for this offer is **31 August 2010**



**WORTH  
\$69.99  
(approx. £50.00)  
EACH**

# World's Lowest Power Microcontrollers with USB OTG

**8- & 16-bit  
USB PIC<sup>®</sup>  
Microcontrollers  
with XLP Technology**

MICROCHIP  
PIC18F14K50

MICROCHIP  
PIC18F46J50  
USB Device

MICROCHIP  
PIC24FJ64GB004  
USB OTG

Energizer  
ULTIMATE LITHIUM  
AAA

CERTIFIED **USB**

**XLP**

Extend the battery life in your portable USB application using PIC<sup>®</sup> microcontrollers with integrated USB and XLP technology. Get the world's lowest power USB microcontrollers with the flexibility to communicate as an embedded host or device.

- Combine eXtreme Low Power with Full-Speed USB device, embedded host, dual role and On-The-Go
- Widely available through worldwide distribution channels
- Download FREE USB stacks and drivers including thumb drive support
  - Host, OTG and Device Stacks
  - Class Drivers (HID, Mass Storage, CDC Drivers)
  - Thumb Drive Support (Mass Storage Driver, SCSI Interface, File Management)

## GET STARTED IN 3 EASY STEPS

1. Purchase a USB Starter Kit
2. Download Free USB Software
3. Order Free Samples

[www.microchip.com/usb](http://www.microchip.com/usb)



Microchip USB Starter Kit

Family	Flash Program Memory (KB)	Pins	USB Type	Sleep Current (nA)	Sleep with Watchdog Timer (nA)	Sleep with Real Time Clock (nA)
PIC18F14K50	8-16	20	Device	24	450	790
PIC18F46J50	16-64	28-44	Device	13	813	813
PIC24FJ64GB004	32-64	28-44	OTG, Dual Role, Embedded Host, Device	20	220	520

## Intelligent Electronics start with Microchip

**microchip**  
**DIRECT**  
[www.microchipdirect.com](http://www.microchipdirect.com)

[www.microchip.com/usb](http://www.microchip.com/usb)

 **MICROCHIP**

Microcontrollers  
Digital Signal  
Controllers  
Analog  
Serial  
EEPROMs





## Recycle It!



BY JULIAN EDGAR

### Fax Machines and Hair Trimmers


This month, fax machines and hair trimmers get the 'short-back-and sides' treatment

**A** LONG with the original Luddites, thermal fax machines are victims of the technological revolution. But you won't find fax machines destroying cotton and wool mills – instead you'll find them forlornly sitting among municipal refuse at the rubbish tip, or for sale for nearly nothing at garage sales, or put out for kerbside rubbish collection. You might even have one yourself, tucked into a back cupboard, never to be used again.

But fax machines are definitely worth pulling apart for the components you'll find inside – often, as is the case with paper-handling consumer goods (think also printers and photocopiers), for the mechanical parts as much as for the electronic bits.




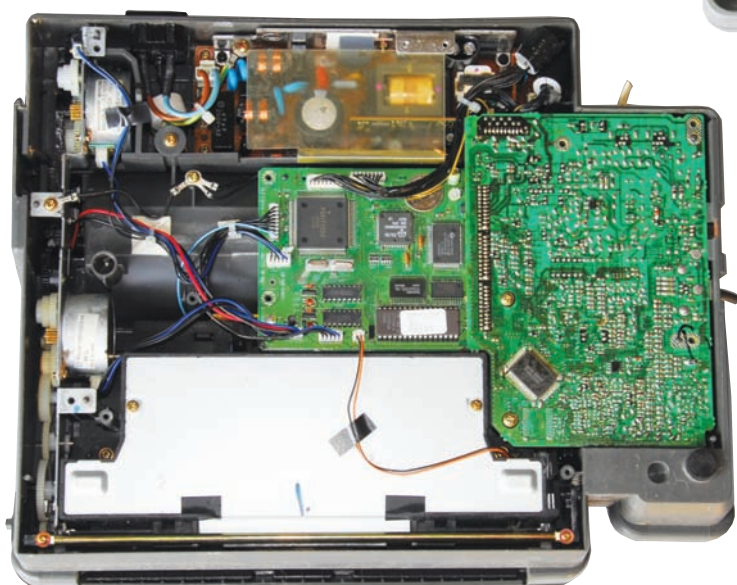▲ This Panasonic KX-F2500 was found at the local tip. The person who had discarded it had kept the telephone handset and the IEC power cord – but that's OK, there are still plenty of good bits left inside. As with most of these sorts of items, the heavier the machine is, the more likely it is to have better quality parts inside. This fax machine was quite weighty.



▲ A few screws later and the insides were revealed. The drive assembly, comprising two stepper motors, gear-trains and one-way clutches, can be seen at left. At the top is a switch-mode power supply and lots of screws and wires can also be glimpsed. This looks like it will be good!

▼ The removed dual stepper motor gear-train. Very usefully, the whole assembly comes out as a single piece. This means that whenever a stepper motor needs to be geared down (think robots or model railways, for example) the reduction gear-train can be used without modification. It also means that where the stepper motor needs to be driven at high speed (for example, when making a hand-cranked alternator) this, too, can be easily achieved.

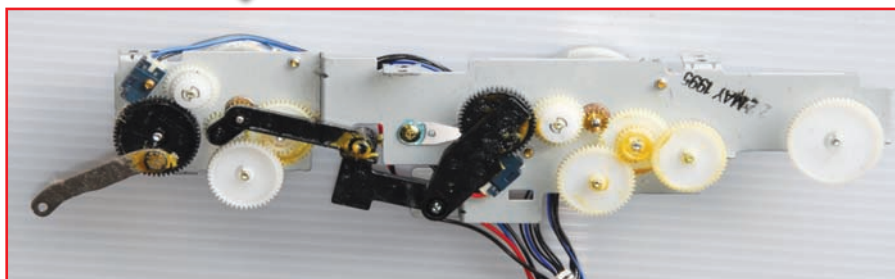

Inside this fax machine – and most of a similar design – you'll find plenty of steel shafts with rubber rollers mounted on them. The rollers are easily removed from the shaft by setting a bench vice so that its jaws are just a little further apart than the diameter of the shaft. The shaft can then be placed in the vice vertically, the rubber roller bearing against the top of the jaws. A hammer and punch can then be used to push the shaft through the roller.



Shown here are three rubber rollers - excellent as anti-vibration mounts, for making grommets or as an additional handle grip on small screwdrivers. Also pictured are six steel shafts (uses? think axles, spacers, hooks...), a variety of springs and some self-tapping and


machine thread screws. Incidentally, the other day I was in a hardware store and I caught sight of their new range of springs. At the prices they're charging for a single spring, I must have accumulated about £100 of salvaged springs!



Here's another goody. It's the lens – and it's sharp and has a useful magnification. In fact, it's perfect for hand-lens use, like reading the values of glass fuses, checking resistor codes and the like. Because I already have enough of them, in this case I didn't bother salvaging the rectangular glass sheet over the LED light or the front-faced mirrors that are also part of the optical system.


I chose not to salvage the switch-mode power supply, miniature pushbuttons or the handful of PCB-mounted LEDs. Instead, I rapidly obtained a microphone, small speaker, two microswitches with levers, a female IEC power cable socket and a fuse.

So what's that long thing up the top? It's one of the beauties out of a fax machine – the LED bar that illuminates the paper when a printout is being scanned. This one comprises 30 surface mount green LEDs, the 'bar' illuminating superbly on 12V. It's perfect for concealed front panel lighting on equipment that needs to be used at night (just mount the light-bar behind a bezel); for decorating a clear PC case; or even for sophisticated glovebox lighting in your car!

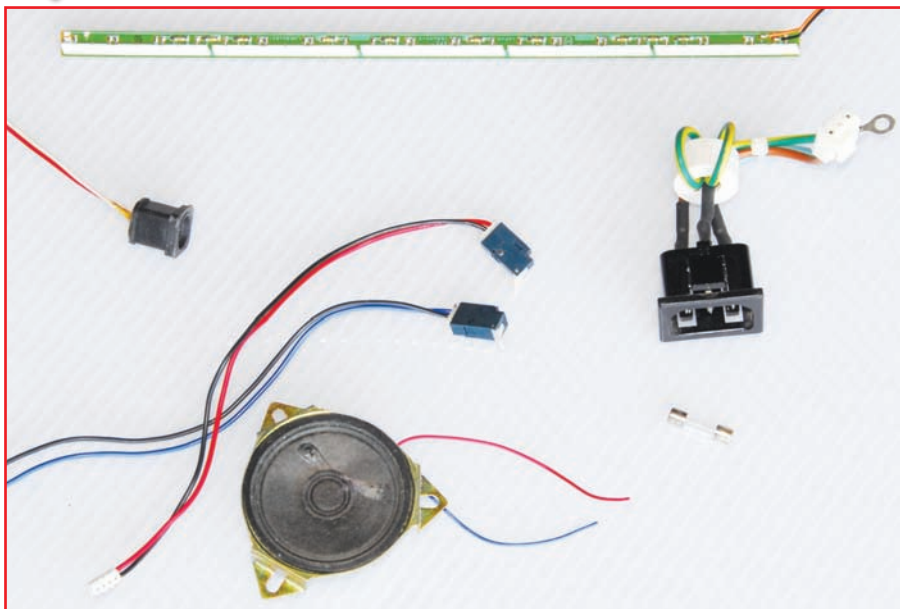




## Recycle It

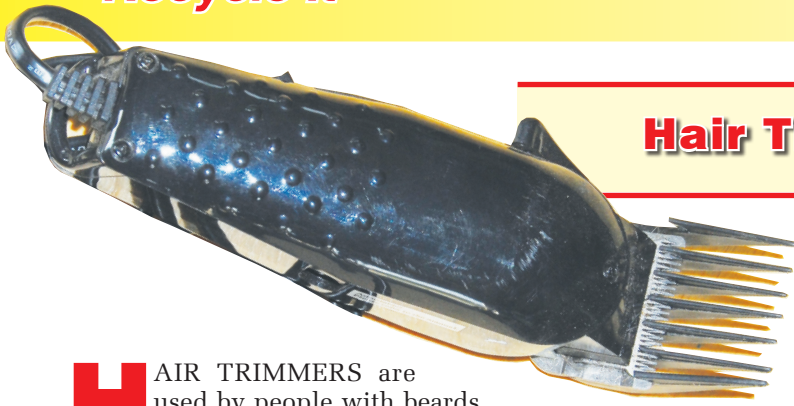

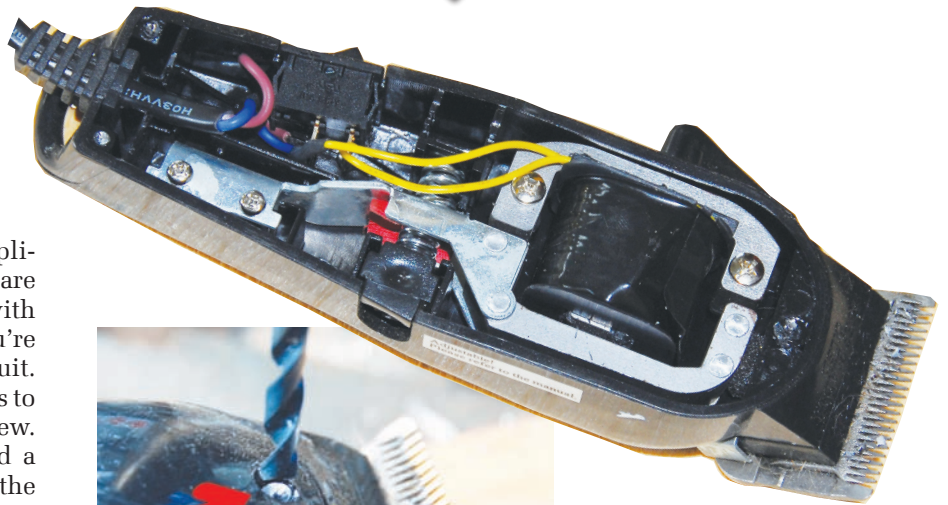
### Hair Trimmers – short cuts

**H**AIR TRIMMERS are used by people with beards – and often by people with dogs! Some people also cut their own hair using a trimmer. Hair trimmers are now very cheap, and so when they clog up or their blades lose their sharpness, they're simply thrown away. But for a small, cheap item, there's a surprising number of parts inside that can be re-used.

As with many other small appliances, these days hair trimmers are often put together with screws with odd-shaped heads – heads that you're not likely to have a screwdriver to suit. If that's the case, the easiest way in is to simply drill out the head of the screw. Three screws were drilled-out and a few moments later, the cover of the trimmer could be pulled off.



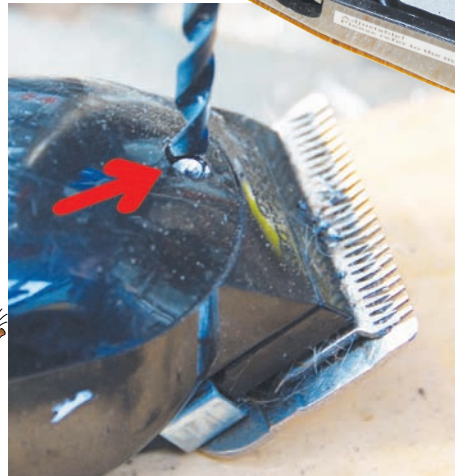Here's the view inside. An electromagnet, connected directly to mains power, pulls in an arm that is connected to the moving section of the blades. As the current alternates, so the blades move back and forth. Adjustable springs set the spacing between the solenoid and the moving plate. With the adjustment correct, the plate and solenoid do not come in contact with one another.



A few moments later and you have available a 10 amp mains power switch, some screws (including two made from stainless steel), a lever, the perfect size to fit to a potentiometer, and two springs.

### Rat It Before You Chuck It!



Whenever you throw away an old TV (or VCR or washing machine or dishwasher or printer) do you always think that surely there must be some good salvageable components inside? Well, this column is for you! (And it's also for people without a lot of dough.) Each month we'll use bits and pieces sourced from discards, sometimes in mini-projects and other times as an ideas smorgasbord.


And you can contribute as well. If you have a use for specific parts which can easily be salvaged from goods commonly being thrown away, we'd love to hear from you. Perhaps you use the pressure switch from a washing machine to control a pump. Or maybe you have a use for the high-quality bearings from VCR heads. Or perhaps you've found how the guts of a cassette player can be easily turned into a metal detector. (Well, we made the last one up, but you get the idea . . .)

So, if you have some practical ideas, do write in and tell us!





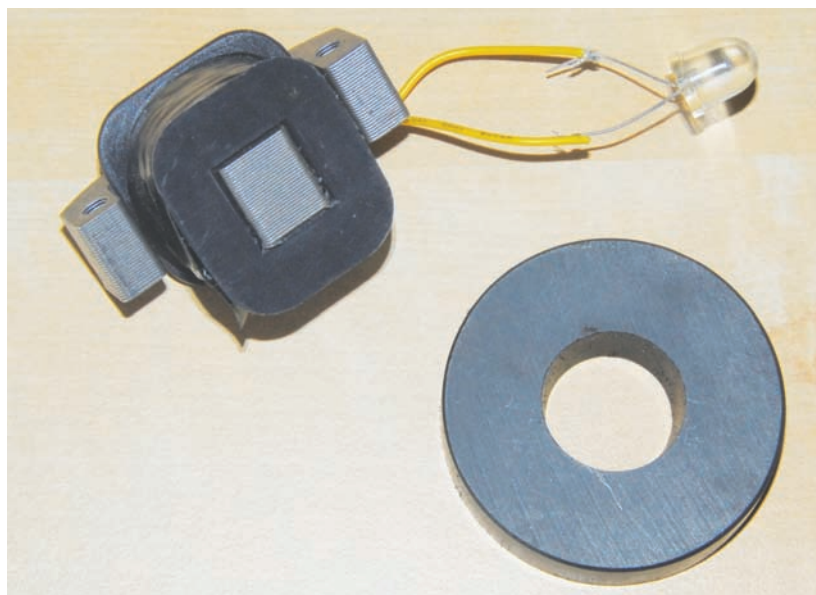An unexpectedly useful part is the larger section of the comb. It's sharp, made from stainless steel and is ideal as a scraper. I use mine to roughen surfaces before gluing them together – and I've never used a better tool for this job!



Finally, there's the mains-power solenoid. I found one of the simplest, yet most intriguing uses is to show children the connection between magnetism and electricity. With the solenoid wired straight to a 10mm LED, a wave of the circular magnet (salvaged from a microwave oven) lights the LED up brilliantly. Instead of the LED you can use a VU or power meter salvaged from a cassette deck or amplifier.

## MIAC<sup>TM</sup>

Now you are in control



The MIAC rugged PICmicro microcontroller is an industrial grade controller which can be used to control a wide range of different electronic systems: for mains switching, motor control, sensor monitoring and much more.

**Free Flowcode 3 with every MIAC**



- ▶ Rugged PIC 18F4455
- ▶ Programmable from USB - download software provided
- ▶ Compatible with third party PICmicro, BASIC and C compilers
- ▶ Includes free Flowcode 3 graphical programming software (no upgrade rights)
- ▶ 8 digital or analogue inputs
- ▶ 4 relay outputs - 8A
- ▶ 4 motor outputs with speed control - 12V, 500mA
- ▶ 4 line 16 character display
- ▶ Control keypad
- ▶ Fully networkable via built in CAN bus
- ▶ Lab View and Visual Basic compatible - DLL supplied
- ▶ In-Circuit Debug over USB with FlowKit

## MATRIX

[www.matrixmultimedia.com](http://www.matrixmultimedia.com)



## Regulators – a hot topic

**Brian Heath** emailed the following question:

*I wonder if you could help me with a problem I have with power supplies. I am an amateur astronomer at the Sherwood Observatory with an interest in Radio Astronomy and have just completed my RSGB intermediate exam. I have built some equipment using my rather basic knowledge in electronics, and for my power supply have built my own with the standard 78XX series regulator and another to a Velleman design sourced through EPE.*

*The problem I find is that a lot of heat is generated by both designs, and I am looking for 12V DC and 6V DC circuits that run much cooler without huge heatsinks. I have searched several sources, but they all use the same technology.*

*The power is for several pieces of equipment, from telescope drives and computer drives for the equipment, to small web cams and video cameras. The current demands are up to 2A. We find that we require several controllers and would like to mount them in one box to suit the particular application, rather than have several supplies through individual transformers.*

*Your assistance in this would be appreciated, as astronomy, while a minority interest, is growing and we are now using more electronic controls, but available designs are lacking. Hoping you can rescue me and my Astronomical Society from this small but important set back.*

Brian also provided some further information about the power source used:

*What I have done in the past is to feed the controller from a 15V to 20V mains transformed AC supply. I then use a bridge rectifier of the correct rating to give me a DC supply. It is from there I am lost. If the circuit has a rectified section then I would use this. We always run cables to equipment in voltages below 24V AC.*

A simplified block diagram of a power supply, based on a linear regulator such as the 78XX series devices that Brian mentions, is shown in Fig.1. A typical circuit for using the regulator is shown in Fig.2.

The 78XX series regulators are generic devices, available from a number of semiconductor manufacturers (for example Fairchild Semiconductor, see [www.fairchildsemi.com](http://www.fairchildsemi.com)), and have been around for a long time. National Semiconductor ([www.national.com](http://www.national.com)) describes the LM78XX devices as obsolete, as they have replaced them with the LM340 series; although the datasheet is still titled 'LM340/LM78XX Series'. The XX in '78XX Series' indicates the regulated output voltage, values of 5V, 6V, 8V, 9V, 12V, 15V, 18V and 24V are available.

In Fig.2, capacitor  $C_1$  is required if the regulator is located a significant distance from the power supply smoothing capacitors, or if the output load capacitance is large. A tantalum, mylar or other capacitor with low impedance at high frequencies should

be used. It should have short leads and be located as close to the regulator as possible. We will discuss  $C_o$  later in the article.

The 78XX series regulators are available in a variety of packages, so you should always check the pinout for the package you have on the manufacturer's datasheet before using it. Choice of package also influences maximum power dissipation and heatsink requirements.

### Power dissipation

The fundamental cause of the power dissipation problem that concerns Brian is the voltage drop across the regulator. Fig.1 shows the current and voltages in and out of the regulator. The voltage drop across the regulator is  $V_{in} - V_{out}$  and the current through the regulator (to the load) is  $I_{out}$ . The power dissipated by the regulator in delivering the output current is  $I_{out} \times (V_{in} - V_{out})$ .

The regulator will also require some internal current to ground, labelled  $I_{gnd}$  on Fig.1. The ground current will result in additional power dissipation equal to  $I_{gnd} \times V_{in}$ . So the total power dissipation is

$$P = I_{out} \times (V_{in} - V_{out}) + I_{gnd} \times V_{in}$$

In most cases, the power due to the drop across the regulator will dominate the power dissipation, so we may not have to calculate  $I_{gnd} \times V_{in}$  to get a good idea of the dissipation.

Using this simplification, if Brian uses a 20V input to a 12V, 1A regulator the power dissipation will be at least  $(20-12) \times 1$ , which is 8W. This is around the maximum

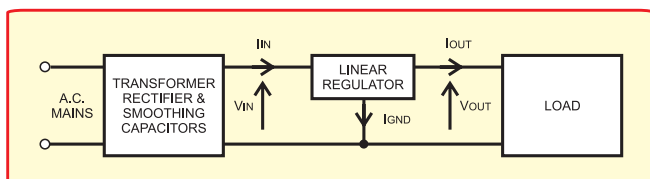


Fig.1. Simplified block schematic diagram for a power supply using a linear regulator


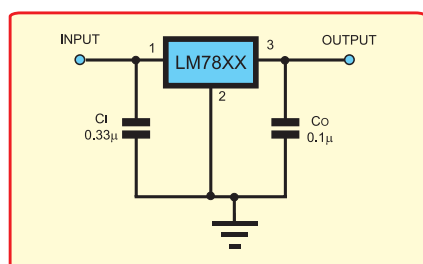


Fig.2. Typical circuit for an LM78XX series regulator

Fig.3. Maximum power dissipation characteristics for LM340/LM78XX in TO-3 package. (National Semiconductor datasheet [www.national.com](http://www.national.com))

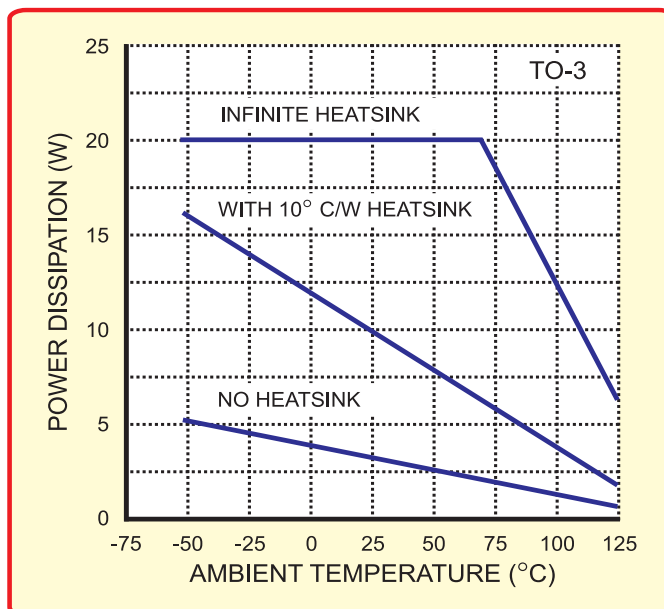

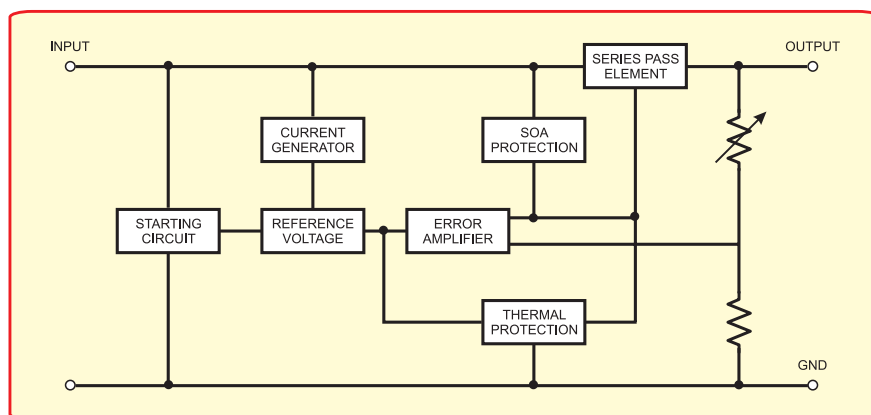


Fig.4. Block diagram for LM78XX series regulators. Based on Fairchild Semiconductor datasheet ([www.fairchildsemi.com](http://www.fairchildsemi.com))

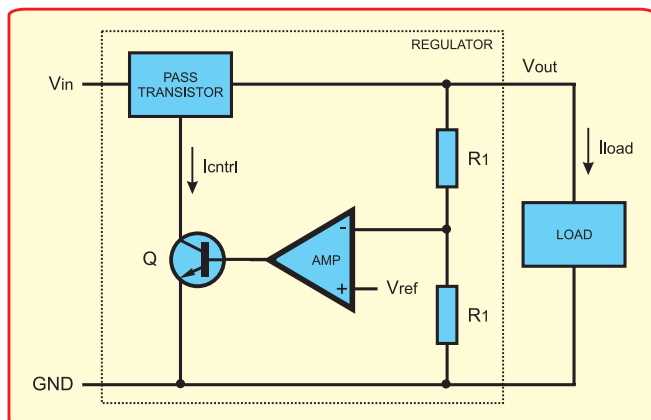


Fig.5. Simplified internal circuitry for the linear regulator

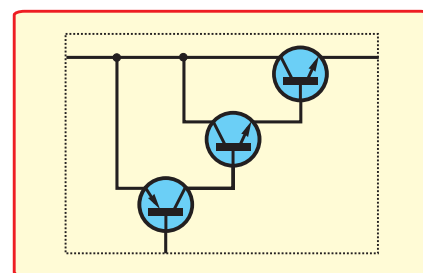


Fig.6. Typical 'pass transistor' for a standard regulator

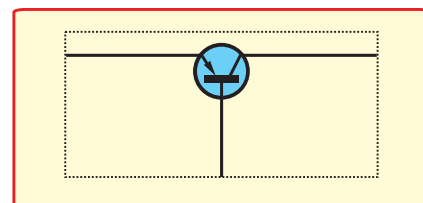


Fig.7. Typical 'pass transistor' for a low dropout (LDO) regulator

inverting input. The increased output voltage will increase the control current to the pass transistor and hence the current to the load, which will tend to increase the output voltage and offset the tendency for decreasing output voltage caused by the increasing load. This negative feedback loop will keep the potential divider voltage equal to the reference voltage and hence keep the output voltage fixed as the load varies.

The 'pass transistor' circuit used inside a standard regulator is shown in Fig.6. This circuit actually uses multiple transistors and requires a minimum of  $2 V_{BE}$  and one  $V_{CE,SAT}$  voltage drop across it, accounting for the typical dropout voltage in the range 1.5V to 2.5V for this type of regulator.

The transistor arrangement shown in Fig.6 is used because its characteristics are helpful in achieving stability of the previously mentioned feedback control loop, which is at the heart of regulator operation. Any feedback control system has the potential of becoming unstable if the conditions under which it operates shift too far from the ideal. In a regulator circuit, such instability takes the form of oscillation of the output voltage.

The standard linear regulator, with the pass circuit shown in Fig.6, is very stable under a wide range of conditions and thus is very easy to use. The price paid for this is the large minimum input to output voltage (dropout voltage) and high power dissipation.

## Low dropout

It is possible to use a different pass circuit, which requires a smaller voltage across it, and therefore to have a regulator with a much lower dropout voltage, and thus potentially much higher efficiency. Such circuits are called 'low dropout' (LDO) regulators and typically use a single transistor as the pass element (see Fig.7). Their downside is that the stability of the control loop is much more sensitive to the external load impedance than with a standard linear regulator. LDO regulators often have dropout voltages of less than 500mV, and low as 20mV for low current loads.

In Fig.2, the regulator is shown with an output capacitor  $C_O$ . This capacitor is not essential for a standard linear regulator, but does improve the transient response of the circuit.

power dissipation of a 78XX regulator in a TO-3 package when using a  $10^\circ\text{C}/\text{W}$  heatsink at  $25^\circ\text{C}$  ambient temperature (from National Semiconductor LM340/LM78XX datasheet, see Fig.3). So it is not surprising that the circuits run hot as Brian describes.

The simplest solution is to reduce the regulator input voltage, but in doing so we have to be aware of the minimum input-to-output voltage difference required by the regulator for it to operate, this is known as the dropout voltage. The datasheet for the regulator chip again provides the figures we need; the dropout voltage is 2V for the LM340/LM78XX at  $I_{out} = 1\text{A}$ .

However, this is not the whole story, with the input-to-output voltage at its absolute minimum, the regulator's performance may be compromised – it may not regulate as well as it should. The datasheet also quotes the minimum input voltage required to maintain regulation, this is 14.6V for a 12V regulator at  $I_{out} = 1\text{A}$  and an ambient temperature of  $25^\circ\text{C}$ . Using this minimum voltage difference we get a dissipation of  $(14.6 - 12) \times 1$ , which is 2.6W.

According to the datasheet graph for the TO-3 package, this is close to the maximum dissipation without a heatsink at  $25^\circ\text{C}$  ambient temperature. It may be too close for comfort though if the power supply is not in a well ventilated case or if it is used in a warm environment. However, the heatsink requirements are certainly less than with a 20V input.

In general, the 78XX series devices tend to need heatsinks when supplying their maximum rated output current of 1A. If they do overheat they should not be destroyed because they include thermal shutdown;

Fairchild describe them as 'essentially indestructible' in the datasheet.

## Safe operating area

An internal block diagram for the LM78XX series regulators is shown in Fig.4. Protection is provided by the 'safe operating area' and 'thermal protection blocks'. If the regulator is overloaded or its output is shorted, the safe operating area circuit will take it into constant-current mode (in which the output voltage is reduced to maintain a constant load current, hence limiting dissipation).

Even with this protection, the regulator may overheat; what happens will depend on the ambient temperature and the size and quality of regulator's heatsink (if there is one). If the regulator reaches its maximum temperature, the thermal protection activates, reducing the load current. Reducing the load current will reduce the heat dissipated by the regulator, so the circuit will reach a point of balance between the dissipation tending to heat it up and the protection circuit winding down the supplied current to reduce the power.

Before returning to the issue of input-to-output voltage drop, it is useful to look at another simplified representation of the regulator's internal circuitry, as shown in Fig.5. The regulator controls the current supplied to the load in such a way as to keep the supply voltage (regulator output voltage,  $V_{out}$ ) constant. It uses a potential divider to produce a fixed fraction of the regulated supply voltage, which is compared to a fixed reference voltage.

If the output voltage decreases the amplifier output will increase because the potential divider is connected to the



The situation is different for LDO regulators – they do require an output capacitor, and the capacitor characteristics are often critical for stable circuit operation. For LDO circuits, it is not just the capacitance of  $C_o$  which is important, but also its equivalent series resistance (ESR). The ESR of  $C_o$  affects the overall impedance characteristics seen by the regulator output and hence the stability of the circuit.

## LM2940

The LM2940 from National Semiconductor is an LDO regulator that is able to provide up to 1A of output current, like the 78XX series devices. Output voltages of 5V, 8V, 9V, 10V, 12V, and 15V are available. The dropout voltage is much smaller than the 78XX series, being typically 0.5V, and no more than 1V over the whole operating temperature range of the device.

The LM2940 is aimed at vehicular applications and has enhanced protection/shut-down features; for example, against protected reverse input voltage. Standard regulator protection features, such as short circuit and thermal overload protection, which we discussed above, are also provided.

The basic circuit for the LM2940 is the same as Fig.2, but the capacitor requirements are different. Like the 78XX series, the input capacitor  $C_i$  is required if the regulator is not very close to the power supply filter. A value of  $0.47\mu\text{F}$  is recommended. Unlike the 78XX series,  $C_o$  is required and must be at least  $22\mu\text{F}$  to maintain stability and must be located close to the regulator. Its value may be larger than  $22\mu\text{F}$  and this will help with maintaining the output voltage during load demand transients.

The equivalent series resistance (ESR) of  $C_o$  is critical and must be maintained over the operating temperature range. The ESR value must be between about  $0.1\Omega$  and  $1\Omega$  (both too low and too high can cause instability), but the datasheet should be consulted for full details.

The requirement for a  $22\mu\text{F}$  capacitor would seem to indicate an aluminium electrolytic part, but these are not recommended in this circuit because their ESR is not stable with temperature. National Semiconductor recommends using a solid tantalum capacitor for  $C_o$ , but this may be expensive. The datasheet also indicates that it may be possible to use a (lower value) tantalum and aluminium electrolytic in parallel to reduce the cost.

Semiconductor manufacturers have worked to develop LDOs with less stringent requirements on the output capacitors. For example, the LP38690 1A low dropout CMOS linear regulators are stable with ceramic capacitors. However, not all types of ceramic capacitor are suitable for regulators quoted as being stable with ceramic capacitors. This is due to the differing properties of different ceramic dielectrics. For example, some have capacitance which is quite voltage dependent. The LP38690, however, may not be suitable for Brian, as these regulators are only available in voltages up to 5V, and are aimed at digital systems such as notebook computers.

## High output current

Brian's requirements for output currents up to 2A go beyond the capabilities of the 78XX series and the LM2940 LDO regulator we have just discussed. Higher current devices are available though, for example the LT1083/LT1084/LT1085 7.5A, 5A, and 3A LDO

regulators from Linear Technology ([www.linear.com](http://www.linear.com)). These are all high efficiency regulators with a 1V dropout voltage and are available in both fixed and adjustable formats.

The available fixed voltages are 3.3V, 3.6V, 5V and 12V, which does not include the 6V required by Brian, so an adjustable regulator would be needed for this. The circuit for the LT1083 series adjustable regulators is shown in Fig.8, together with the formula for setting the output voltage. Another possibility from Linear Technology is the LT1086 Series 1.5A LDO regulators, which also include a 12V fixed output voltage version and an adjustable device.

As expected with an LDO regulator, the LT1083 and LT1086 family devices require an output capacitor for stability. The minimum requirement is a  $10\mu\text{F}$  solid tantalum capacitor. For all operating conditions, use of a  $150\mu\text{F}$  aluminium electrolytic or a  $22\mu\text{F}$  solid tantalum on the output will ensure stability, but often smaller values than this can be used. The datasheet provides all the details needed when choosing a suitable capacitor.

Like the other regulators we have discussed, an input capacitor is required for the LT1083 and LT1086 series devices if the regulator is not close (two inches is quoted on the datasheet) to the smoothing/filter capacitors. A  $10\mu\text{F}$  solid tantalum capacitor is recommended.

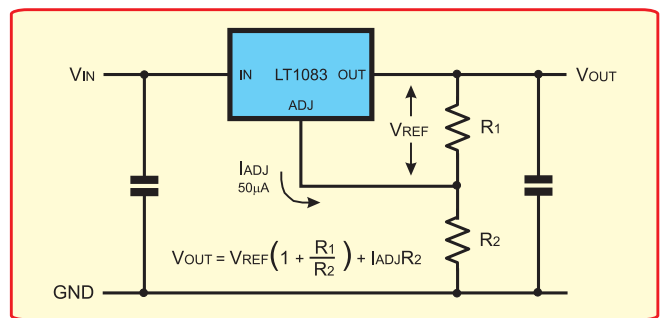


Fig.8. Basic circuit for the LT1083 family of adjustable regulators from Linear Technology ([www.linear.com](http://www.linear.com))

Use of LDO regulators should help Brian with his excessive power dissipation, as long as the input voltage to the regulator is kept at a reasonably low value. Ideally, it should be just above the voltage at which the regulator works correctly, but this may be difficult to achieve if the load current varies a lot and causes the voltage from the circuitry before the regulator to vary.

More sophisticated circuits can be built to overcome this using another regulator to pre-regulate the input to the LDO regulator. The pre-regulator will typically be a very high efficiency, switch-mode regulator. The LT1083/LT1086 datasheets provide example schematics of pre-regulated LDO regulators.

## Datasheets

[www.national.com/ds/LM/LM340.pdf](http://www.national.com/ds/LM/LM340.pdf)  
[www.national.com/ds/LM/LM2940.pdf](http://www.national.com/ds/LM/LM2940.pdf)  
[www.fairchildsemi.com/ds/LM%2FLM7812.pdf](http://www.fairchildsemi.com/ds/LM%2FLM7812.pdf)  
[cds.linear.com/docs/Datasheet/1083ffd.pdf](http://cds.linear.com/docs/Datasheet/1083ffd.pdf)  
[cds.linear.com/docs/Datasheet/108345fg.pdf](http://cds.linear.com/docs/Datasheet/108345fg.pdf)  
[cds.linear.com/docs/Datasheet/1086ffs.pdf](http://cds.linear.com/docs/Datasheet/1086ffs.pdf)

# GRAPHIC DISPLAYS

From  
£39.00



Add colour to your project!

High quality serial graphic displays pre-fitted with a powerful controller for easy interface to your microprocessor. Easily draw lines, circles, text, show images, videos, and much more.  
Screen sizes from 0.96" to 3.2" and up to 256K colours.  
Options include: uLCD, uOled, touch-screen, SD/microSD card support, scripting language, user switch interface and sound. Easy 5 pin interface to host device  
**EZL-176 (1.76" diag) only £39.00 each + VAT**  
See the full range, prices, data-sheets and on-line ordering at:-

[www.milinst.com](http://www.milinst.com)



# Practically Speaking

Robert Penfold looks at the Techniques of Actually Doing it!

**T**HE hobby of electronics is not really comparable to any other pastime. It contains elements of other hobbies, such as computing and metalworking, but it also requires a unique set of skills, and perhaps a wider range of skills than practically any other hobby.

Articles in this series normally concentrate on one specific area of electronic project construction, but this month an overview of project building will be provided. For complete beginners, this should give a good idea of exactly what is involved in building an electronic gadget, the tools required, and whether it is something they would like to try.

## The right stuff

The first task facing the constructor is to obtain all the parts required for the chosen project. The days of going to your local radio and electronic component shop for *all* the parts are now long gone. You might be lucky enough to live reasonably close to a large electronics store that can supply all or most of the components for a particular project, but these days the majority of components are purchased by mail order or online.

Some components will be advertised in the pages of *EPE*, but most will have to be sought in the catalogues of *EPE* advertisers, and possibly in the huge online component catalogues of the major electronic component suppliers. The large companies such as Farnell and RS Components are primarily suppliers to commercial customers, but they will supply to private individuals via their online ordering systems.

It is a good idea to browse some printed or online component catalogues, which usually contain photographs of components and a great deal of useful information. This will help you to familiarise yourself with electronic components and reduce the risk of buying the wrong parts.

The more specialised components, including many integrated circuits (ICs) and other semiconductors, tend to come and go relatively quickly these days. It is, therefore, important to make sure that all the components for a project are still available before starting to buy any of them. This is especially important when building a project from an article that was published more than a few years ago.

## Nuts and bolts

Having assembled all the parts, it is time to start building, and it is probably best to deal with the mechanical side of

construction first. This usually involves nothing more than drilling and cutting some holes in the case. Things such as switches and sockets are mounted in these holes, and there might also be holes to permit the circuit board to be fixed to the case.

With this method, the circuit board is hard-wired to the controls, sockets and switches in the final stages of construction. An alternative approach is to have the controls and sockets fitted along one edge of the circuit board, and fixing these in the case then provides the mounting for the circuit board as well.

Preparing the case is much the same either way. Many of the tools required can be found in the average do-it-yourself tool kit. However, it will almost certainly be necessary to buy some additional tools, but it is better to add them as and when they are required, rather than buying lots of likely looking tools, some of which may never be needed.

It is a good idea to start with a project that is fairly straightforward as far as the mechanical aspects of construction are concerned. There will be plenty of new things to learn when dealing with the electronics, and it is probably best to concentrate on mastering these and to avoid getting distracted by any difficult or very time consuming facets of the mechanical side of construction.

If they are not already present in your toolkit, it will certainly be necessary to obtain some small electricians' screwdrivers. Wire cutters and insulation strippers are also essential. These can be obtained as separate tools, but initially an inexpensive combined wire cutter and stripper tool should suffice. Do not improvise using tools such as scissors and penknives. Doing so is likely to damage the tools, the wires, and yourself!

## Holing out

Drilling holes in metal or plastic cases requires ordinary HSS twist drill bits. Electronic project construction often involves working on a small scale using relatively soft materials, such as plastics and aluminium. A large power drill is usable, but should preferably be fitted in a good quality stand. Something like a small cordless drill or even a hand drill is often better suited to the task. A set of miniature files are useful for 'fine tuning' any holes that are not quite right at the first attempt, and for making non-circular cut-outs such as the rectangular mounting holes required by some panel lights and switches.

Last, and by no means least, you will need somewhere to carry out the drilling and cutting. It does not matter too much if you do not have the luxury of a room

dedicated to hobby pursuits. I would guess that by now there must be many millions of electronic projects that have been built on kitchen tables, or other parts of the house annexed from their normal functions.

Due care must be taken to avoid damaging tables or other work surfaces, and it will probably be necessary to improvise a temporary worktop from a piece of MDF or chipboard. Always make sure that the work area is properly cleared of any sawdust, swarf, or other scrap, once the work has been completed.

## Highly charged

With work on the case completed it is time to move on to the circuit board. It is tempting to start with a fairly large and impressive project, but something fairly simple and straightforward is a more practical choice for a first project. The larger the project, the greater the chances of a mistake being made and the finished unit failing to work. The chances of successfully completing a project are very high if something fairly simple is chosen, and construction is tackled in a methodical and careful manner, with nothing being rushed.

An unavoidable complication of modern electronic project building is that many semiconductors are vulnerable to being zapped by high 'static' voltages. These voltages are a normal part of our environments, and you could well have them in your immediate vicinity while reading this piece. These days, most integrated circuits seem to be vulnerable to static charges, as are some other semiconductor components. If in doubt, always operate on the basis that semiconductors require antistatic precautions. Using antistatic precautions was covered in the *EPE* March '10 issue, and it will not be considered in detail again here.

One important point is to resist the temptation to remove vulnerable components from their protective packaging to have a closer look at them. Any unnecessary handling of static-sensitive components should be avoided. It is advisable to obtain one or two items of antistatic equipment at an early stage, and right away if your first project uses any expensive semiconductors. A conductive wristband and earthing lead can be obtained quite cheaply, and will largely eliminate the risk of accidentally zapping any sensitive components.

## On the board


Most or all of the electronic components are fitted onto a circuit board of some kind. This will usually be in the form of a dedicated printed circuit board that is designed specifically for one circuit. The



board is made from an insulating material such as fibreglass, and it has holes to take the pins and leads of the components.

In its most simple form there are copper pads and tracks on one side of the board. The components are fitted on the other side of the board, which is generally considered to be the top side, the leads are trimmed to length, and then they are soldered to the copper pads on the underside of the board. The copper tracks carry the interconnections between the components, forming the correct circuit.

There are variations on this basic scheme of things, and some boards are double-sided (see Fig.1). These usually have components fitted on only one side, but there are tracks on both sides of the board. There are additional holes that are used to carry connections through the board, and this enables connections to weave across the board from one side to the other, crossing over other tracks on the way. Assuming a ready-made board is used, for the constructor it makes little difference whether the board is a single or double-sided type.

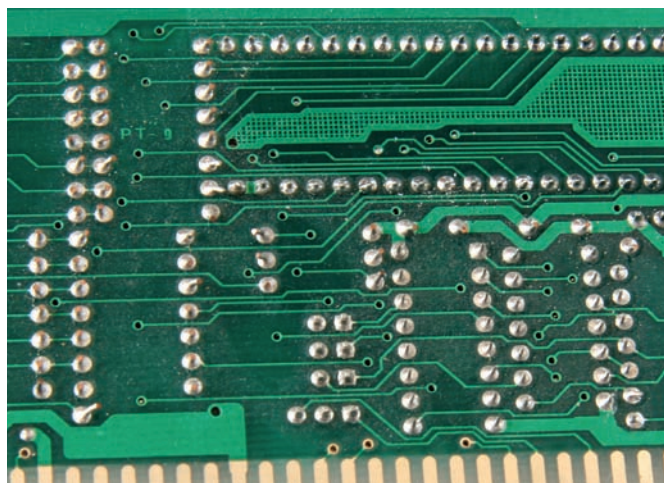

*Fig.1. The underside of a double-sided printed circuit board (PCB). The empty holes have metal plating that carries connections through the board. Some double-sided boards require tiny pins and soldered connections on both sides of the board to provide these connections*

Another variation certainly does make a big difference when it comes to actually building the board, and this is where surface-mount devices (SMDs) are used. Surface-mount components are generally much smaller than their conventional counterparts, which means that most of them are minute. They have no leadout wires, but instead have metal pads that are soldered to 'holeless' copper pads on the board. The board can be single or double-sided.

A further variation is to have a conventional board that also takes a few surface-mount components. This can be necessary if some of the components used in the project are only available in surface-mount versions. Using surface-mount components is, to say the least, a bit tricky, and it is probably best to avoid this type of construction until some experience has been gained building conventional circuit boards.


## Stripboard

Stripboard is yet another type of printed circuit board. It is basically just a form of single-sided circuit board, but it is a

proprietary product that is designed to accommodate practically any circuit. The board has numerous small holes on a 2.54mm  $\times$  2.54mm matrix. Copper strips on the underside of the board run along the rows of holes (see Fig.2.).

Stripboard is used much like an ordinary printed circuit board, with the components fitted on the plain side of the board and soldered to the copper strips on the underside. It is invariably necessary to make cuts in the copper strips at appropriate places, so that some strips can carry more than one set of interconnections. Most circuits built using stripboard also require numerous wires on the top side of the board to link sections of copper strip. These link wires are sometimes required with custom single-sided boards as well.

A custom printed circuit board is generally easier to use than stripboard. With a custom board there is a hole for each component lead or pin and no 'spares'. The situation is very different with stripboard, where the vast majority of the holes are normally left unused, and getting a component in the wrong place is all too easy.

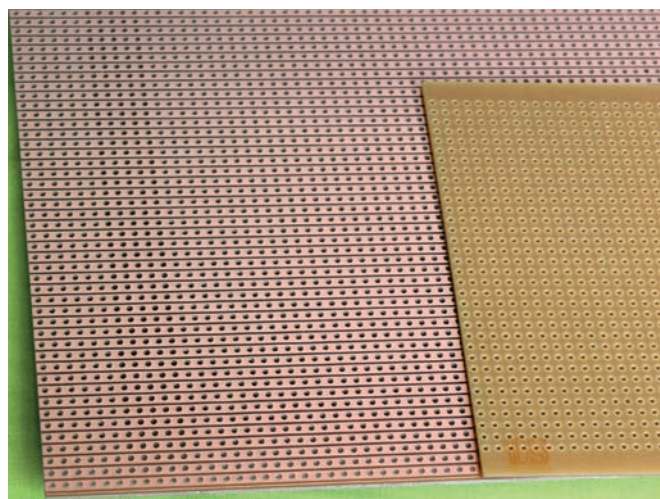

*Fig.2. Stripboard has a matrix of holes with copper strips on one side of the board. It is usually necessary to make breaks in some of the strips, either using a special tool, or a drill bit of about 5mm in diameter, which does the job quite well*

Ordinary printed circuit boards are by no means immune to accidental short circuits between pads due to minute blobs of excess solder, but it is something that seems to be a much more significant problem with stripboard. Initially, it is probably best to take the easier option and build projects based on custom printed circuit boards.

## Soldering on

Whatever type of circuit board is used, it will be necessary to master the art of soldering. A small and inexpensive iron with a rating of about 15W to 20W is sufficient, and it should be fitted with a small bit of about 2.5mm in diameter. The iron should have a proper stand that will hold it safely while it is hot, and act as a heatsink to prevent it from overheating. It is sometimes possible to obtain a soldering kit that includes an iron, a matching stand, and some solder of the appropriate type for project construction.

There is insufficient space here for a detailed description of good soldering technique, but an excellent soldering guide is available on the EPE website, and soldering irons sometimes complete with detailed instructions.

A couple of points to keep in mind are that the surfaces to be joined *must* be clean, and the iron should be applied to the joint first, and then the solder should be fed into it. Do not make the classic mistake of melting some solder on the iron and then applying it to the joint. It is a good idea to obtain some stripboard and a few inexpensive components, such as resistors, so that you can practice and become proficient at soldering before moving on to the genuine article.

## Finishing off

With the completed circuit board fitted in its case, it is then just a matter of adding any interwiring needed to complete the project. This wiring is perhaps less straightforward than fitting the components to a circuit board, but where appropriate, there should be a wiring diagram that clearly illustrates

all the hard wiring. Use a thin insulated multicore wire and not a single-core type. 7/0.2 (seven cores of 0.2mm wire) is suitable for most connections, but a heavier type such as 16/0.2 might be needed where relatively high currents are involved.

There is a strong temptation to switch on a newly constructed project and try it out as soon as it is finished. However, even if you have checked and double-checked everything along the way, it is still a good idea to thoroughly check the completed unit once more for any errors. The unit will probably work first time, but do not panic if it fails to operate properly. The problem will almost certainly be due to a minor error somewhere, and checking everything again will probably sort things out. You can then start thinking about your next project!

Checkout Alan Winstanley's widely acclaimed Soldering Guide at [www.epemag.wimborne.co.uk/solderfaq.htm](http://www.epemag.wimborne.co.uk/solderfaq.htm)



# Ingenuity Unlimited


Our regular round-up of readers' own circuits

## WIN A PICO PC-BASED OSCILLOSCOPE WORTH £799

- 200MHz Analogue Bandwidth Dual Channel Storage Oscilloscope
- Spectrum Analyser
- Frequency Meter
- Multimeter
- USB Interface.

If you have a novel circuit idea which would be of use to other readers then a Pico Technology PC-based oscilloscope could be yours.

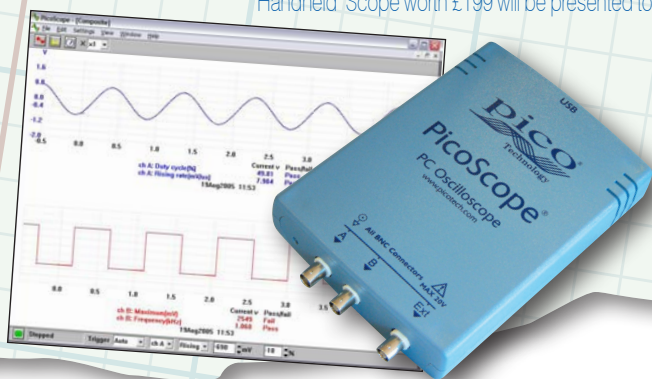After every 20 published IU circuits, Pico Technology will be awarding a PicoScope 3206 digital storage oscilloscope for the best IU submission. In addition a PicoScope 2105 Handheld 'Scope worth £199 will be presented to the runner up.



We pay between £10 and £50 for all material published, depending on length and technical merit. We're looking for novel applications and circuit designs, not simply mechanical, electrical or software ideas. Ideas must be the reader's own work and **must not have been published or submitted for publication elsewhere.**

The circuits shown have NOT been proven by us. **Ingenuity Unlimited** is open to ALL abilities, but items for consideration in this column should be typed or word-processed, with a brief circuit description (between 100 and 500 words maximum) and include a full circuit diagram showing all component values. **Please draw all circuit schematics as clearly as possible.** Send your circuit ideas to: Ingenuity Unlimited, Wimborne Publishing Ltd., 113 Lynwood Drive, Merley, Wimborne, Dorset BH21 1UU. Email: [editorial@epemag.wimborne.co.uk](mailto:editorial@epemag.wimborne.co.uk).

Your ideas could earn you some cash and a prize!

## Clock Generator – Time Out

**T**HIS circuit is a one-shot/continuous clock generator that is useful as a piece of test kit when developing and testing logic circuits. It is especially useful for those who do not have access to a commercial signal generator.

At the heart of the circuit (Fig.1) is a 7555 CMOS timer IC. With switch S1 in position 1, the timer is in its continuous mode. This makes use of a less commonly seen astable configuration, where the timing capacitor C4 is charged by the same resistance that it is discharged by, this resistance being connected between the output (pin 3) and the trigger input (pin 2). Using this astable configuration gives the advantage of allowing the timer to be switched between its astable and monostable (continuous and one-shot) configurations, simply by using a single DPDT switch.

With switch S1 in position 2, the timer is in its one-shot mode and the same capacitor (C4), is again used for timing, but in this mode a different resistance is switched in for monostable timing. The one-shot can be triggered by pressing S2, a normally-open momentary action switch. Capacitor C3 and resistor R2 create a differentiator, acting to produce a narrow trigger pulse. When S2 is released, R1 acts as a pull-up resistor and it also acts in conjunction with C2 to debounce switch S2.

The timing for continuous and one-shot modes can be changed by adjusting potentiometers VR1 and VR2 respectively.

With the component values shown and an unloaded output, the astable frequency can be adjusted from about 0.7Hz up to about 125Hz. The duty cycle is close to 50%. The monostable pulse-width can be adjusted from about 8ms up to about 1.5 seconds.

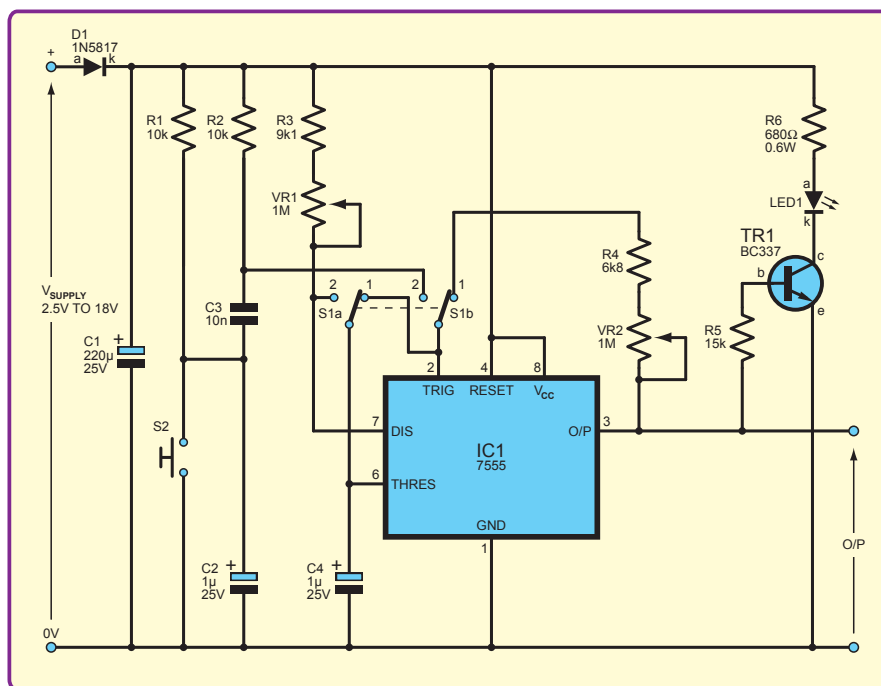


Fig.1. Complete circuit diagram for the Clock Generator



The output is both TTL and CMOS compatible. The circuit's voltage supply can range from 2.5V to 18V, and should be set to match the voltage supply to the IC(s) under test. This is because the timer's output voltage is of a similar magnitude to its supply voltage.

The timer's output drives LED1 via transistor TR1. The LED indicates output activity, but is quite dim when using a low voltage supply and is constantly lit for the higher astable frequencies. The circuit avoids driving the LED directly from the timer's output because this would load the output voltage down close to the  $V_{in,high(min)}$  of some logic families.

## Rogue pulses

It is worth noting that when switched to astable, the first output pulse will be slightly longer than the succeeding ones, due to the fact that C4 is starting from a totally discharged situation.

If you are unlucky with your build, you will find that an extra odd length pulse is output when switching from astable, (when the output is low), to monostable. This is caused by switch S1a leaving position 1 slightly before S1b does, causing the trigger input to be pulled low momentarily by the low output. To eliminate this minor irritation, swap S1a with S1b, keeping the same pins for positions 1 and 2.

When switching from astable, (when the output is high), to monostable, the last pulse will be shortened or lengthened. This is because this pulse is finished off using the monostable timing resistance.

Chris Hinchcliffe, Dorset

## EPE BINDERS

**KEEP YOUR MAGAZINES SAFE –  
RING US NOW!**

This ring binder uses a special system to allow the issues to be easily removed and re-inserted without any damage. A nylon strip slips over each issue and this passes over the four rings in the binder, thus holding the magazine in place.

The binders are finished in hard-wearing royal blue PVC with the magazine logo in gold on the spine. They will keep your issues neat and tidy but allow you to remove them for use easily.

The price is £7.95 plus £3.50 and packing. If you order more than one binder add £1 postage for each binder after the initial £3.50 postage charge (overseas readers the postage is £6.00 each to everywhere except Australia and Papua New Guinea which costs £10.50 each).

Send your payment in £'s sterling cheque or PO (Overseas readers send £ sterling bank draft, or cheque drawn on a UK bank or pay by card), to:

Everyday Practical Electronics, Wimborne Publishing Ltd,  
113 Lynwood Drive, Merley, Wimborne, Dorset, BH21 1UU.  
Tel: 01202 873872. Fax: 01202 874562.  
E-mail: [editorial@epemag.wimborne.co.uk](mailto:editorial@epemag.wimborne.co.uk).  
Web site: <http://www.epemag.com>

We also accept card payments. Mastercard, Visa, or Maestro. Send your card number and card valid from and expiry date plus Maestro Issue No. and the security code on the back of the card with your order.



post




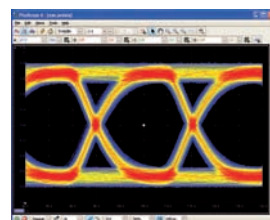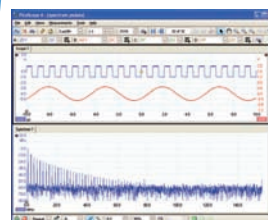
## THE HIGHEST PERFORMANCE PC OSCILLOSCOPE

PICOSCOPE 6000 SERIES



350 MHz BANDWIDTH  
5 GS/s SAMPLING  
UP TO 1 GS MEMORY



### 4 Channel oscilloscope with spectrum analyzer

Built-in arbitrary waveform generator

CAN bus decoding

Advanced triggering

Mask limit testing

Full math and measurement functions


High Speed USB connection

Easy-to-use software

SDK for major third party applications

Five-year warranty

**All included, from only £2995**

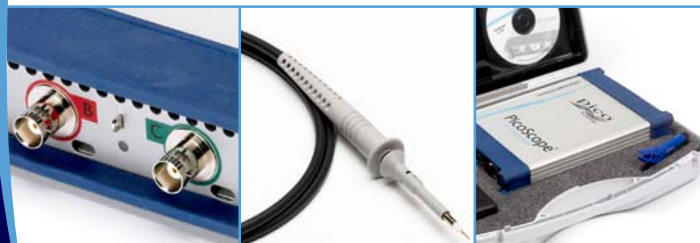


pico  
Technology

[www.picotech.com/scope2007](http://www.picotech.com/scope2007)

# EPE IS PLEASED TO BE ABLE TO OFFER YOU THESE ELECTRONICS CD-ROMS

## ELECTRONICS PROJECTS

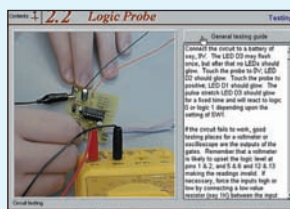


Logic Probe testing

*Electronic Projects* is split into two main sections: **Building Electronic Projects** contains comprehensive information about the components, tools and techniques used in developing projects from initial concept through to final circuit board production. Extensive use is made of video presentations showing soldering and construction techniques. The second section contains a set of ten projects for students to build, ranging from simple sensor circuits through to power amplifiers. A shareware version of Matrix's CADPACK schematic capture, circuit simulation and p.c.b. design software is included.

The projects on the CD-ROM are: Logic Probe; Light, Heat and Moisture Sensor; NE555 Timer; Egg Timer; Dice Machine; Bike Alarm; Stereo Mixer; Power Amplifier; Sound Activated Switch; Reaction Tester. Full parts lists, schematics and p.c.b. layouts are included on the CD-ROM.

## ELECTRONIC CIRCUITS & COMPONENTS V2.0

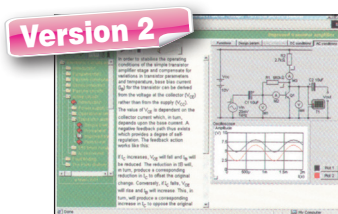


Circuit simulation screen

*Electronic Circuits & Components V2.0* provides an introduction to the principles and application of the most common types of electronic components and shows how they are used to form complete circuits. The virtual laboratories, worked examples and pre-designed circuits allow students to learn, experiment and check their understanding. Version 2 has been considerably expanded in almost every area following a review of major syllabuses (GCSE, GNVQ, A level and HNC). It also contains both European and American circuit symbols. Sections include: **Fundamentals**: units and multiples, electricity, electric circuits, alternating circuits. **Passive Components**: resistors, capacitors, inductors, transformers. **Semiconductors**: diodes, transistors, op amps, logic gates. **Passive Circuits**. **Active Circuits**. **The Parts Gallery** will help students to recognise common electronic components and their corresponding symbols in circuit diagrams.

Included in the Institutional Versions are multiple choice questions, exam style questions, fault finding virtual laboratories and investigations/worksheets.

## ANALOGUE ELECTRONICS

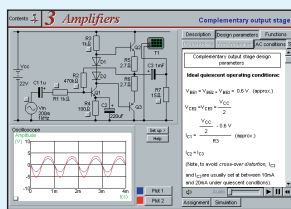


Complimentary output stage

*Analogue Electronics* is a complete learning resource for this most difficult branch of electronics. The CD-ROM includes a host of virtual laboratories, animations, diagrams, photographs and text as well as a SPICE electronic circuit simulator with over 50 pre-designed circuits.

Sections on the CD-ROM include: **Fundamentals** – Analogue Signals (5 sections), Transistors (4 sections), Waveshaping Circuits (6 sections). **Op Amps** – 17 sections covering everything from Symbols and Signal Connections to Differentiators. **Amplifiers** – Single Stage Amplifiers (8 sections), Multi-stage Amplifiers (3 sections). **Filters** – Passive Filters (10 sections), Phase Shifting Networks (4 sections), Active Filters (6 sections). **Oscillators** – 6 sections from Positive Feedback to Crystal Oscillators. **Systems** – 12 sections from Audio Pre-Amplifiers to 8-Bit ADC plus a gallery showing representative p.c.b. photos.

## DIGITAL ELECTRONICS V2.0

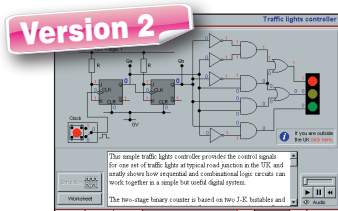

Virtual laboratory - Traffic Lights

*Digital Electronics* builds on the knowledge of logic gates covered in *Electronic Circuits & Components* (above), and takes users through the subject of digital electronics up to the operation and architecture of microprocessors. The virtual laboratories allow users to operate many circuits on screen.

Covers binary and hexadecimal numbering systems, ASCII, basic logic gates, monostable action and circuits, and bistables – including JK and D-type flip-flops. Multiple gate circuits, equivalent logic functions and specialised logic functions. Introduces sequential logic including clocks and clock circuitry, counters, binary coded decimal and shift registers. A/D and D/A converters, traffic light controllers, memories and microprocessors – architecture, bus systems and their arithmetic logic units. Sections on Boolean Logic and Venn diagrams, displays and chip types have been expanded in Version 2 and new sections include shift registers, digital fault finding, programmable logic controllers, and microcontrollers and microprocessors. The Institutional versions now also include several types of assessment for supervisors, including worksheets, multiple choice tests, fault finding exercises and examination questions.

## ANALOGUE FILTERS



Filter synthesis

*Analogue Filters* is a complete course in designing active and passive filters that makes use of highly interactive virtual laboratories and simulations to explain how filters are designed. It is split into five chapters: **Revision** which provides underpinning knowledge required for those who need to design filters. **Filter Basics** which is a course in terminology and filter characterization, important classes of filter, filter order, filter impedance and impedance matching, and effects of different filter types. **Advanced Theory** which covers the use of filter tables, mathematics behind filter design, and an explanation of the design of active filters. **Passive Filter Design** which includes an expert system and filter synthesis tool for the design of low-pass, high-pass, band-pass, and band-stop Bessel, Butterworth and Chebyshev ladder filters. **Active Filter Design** which includes an expert system and filter synthesis tool for the design of low-pass, high-pass, band-pass, and band-stop Bessel, Butterworth and Chebyshev op.amp filters. This CD-ROM is being discontinued, **only the Hobbyist/Student version is now available.**

## PRICES

Prices for each of the CD-ROMs above are:  
(Order form on third page)

Hobbyist/Student .....	£45	inc VAT
Institutional (Schools/HE/FE/Industry) .....	£99	plus VAT
Institutional 10 user (Network Licence) .....	£249	plus VAT
Site licence .....	£499	plus VAT

(UK and EU customers add VAT at 17.5% to 'plus VAT' prices)



## ROBOTICS & MECHATRONICS



### Case study of the Milford Instruments Spider

Robotics and Mechatronics is designed to enable hobbyists/students with little previous experience of electronics to design and build electromechanical systems. The CD-ROM deals with all aspects of robotics from the control systems used, the transducers available, motors/actuators and the circuits to drive them. Case study material (including the NASA Mars Rover, the Milford Spider and the Furby) is used to show how practical robotic systems are designed. The result is a highly stimulating resource that will make learning, and building robotics and mechatronic systems easier. The Institutional versions have additional worksheets and multiple choice questions.

- Interactive Virtual Laboratories
- Little previous knowledge required
- Mathematics is kept to a minimum and all calculations are explained
- Clear circuit simulations



# PICmicro TUTORIALS AND PROGRAMMING


## HARDWARE

### VERSION 3 PICmicro MCU development board

*Suitable for use with the three software packages listed below.*

This flexible development board allows students to learn both how to program PICmicro microcontrollers as well as program a range of 8, 18, 28 and 40-pin devices from the 12, 16 and 18 series PICmicro ranges. For experienced programmers all programming software is included in the PPP utility that comes with the development board. For those who want to learn, choose one or all of the packages below to use with the Development Board.

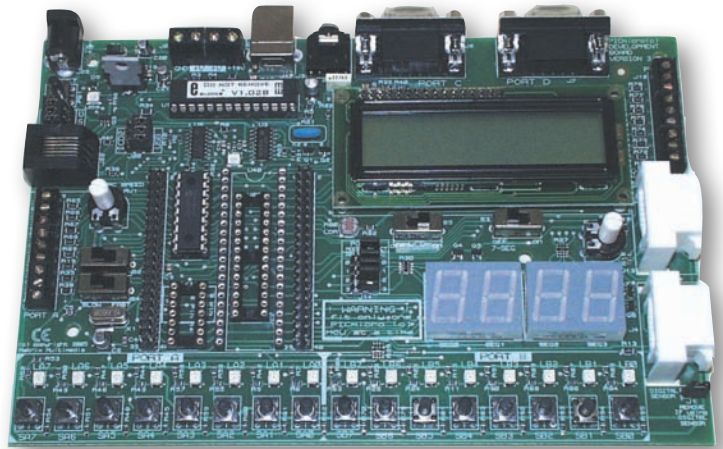- Makes it easier to develop PICmicro projects
- Supports low cost Flash-programmable PICmicro devices
- Fully featured integrated displays – 16 individual LEDs, quad 7-segment display and alphanumeric LCD display
- Supports PICmicro microcontrollers with A/D converters
- Fully protected expansion bus for project work
- USB programmable
- Can be powered by USB (no power supply required)



**£158 including VAT and postage, supplied with USB cable and programming software**

## SOFTWARE


### ASSEMBLY FOR PICmicro V3

**(Formerly PICTutor)**

Assembly for PICmicro microcontrollers V3.0 (previously known as PICTutor) by John Becker contains a complete course in programming the PIC16F84 PICmicro microcontroller from Arizona Microchip. It starts with fundamental concepts and extends up to complex programs including watchdog timers, interrupts and sleep modes.

The CD makes use of the latest simulation techniques which provide a superb tool for learning: the Virtual PICmicro microcontroller, this is a simulation tool that allows users to write and execute MPASM assembler code for the PIC16F84 microcontroller on-screen. Using this you can actually see what happens inside the PICmicro MCU as each instruction is executed, which enhances understanding.

- Comprehensive instruction through 45 tutorial sections
- Includes Vlab, a Virtual PICmicro microcontroller: a fully functioning simulator
- Tests, exercises and projects covering a wide range of PICmicro MCU applications
- Includes MPLAB assembler
- Visual representation of a PICmicro showing architecture and functions
- Expert system for code entry helps first time users
- Shows data flow and fetch execute cycle and has challenges (washing machine, lift, crossroads etc.)
- Imports MPASM files.

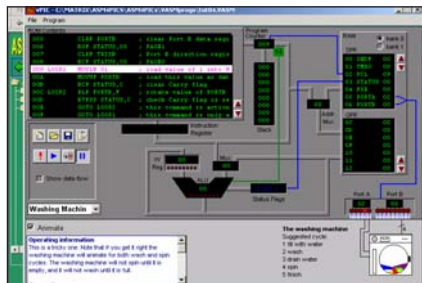


### 'C' FOR 16 Series PICmicro Version 4

The C for PICmicro microcontrollers CD-ROM is designed for students and professionals who need to learn how to program embedded microcontrollers in C. The CD-ROM contains a course as well as all the software tools needed to create Hex code for a wide range of PICmicro devices – including a full C compiler for a wide range of PICmicro devices.

Although the course focuses on the use of the PICmicro microcontrollers, this CD-ROM will provide a good grounding in C programming for any microcontroller.

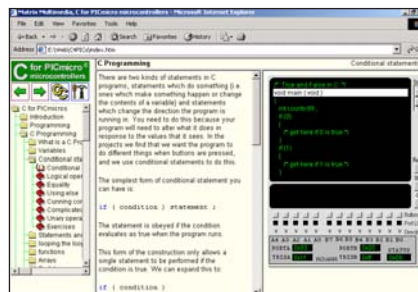- Complete course in C as well as C programming for PICmicro microcontrollers
- Highly interactive course
- Virtual C PICmicro improves understanding
- Includes a C compiler for a wide range of PICmicro devices
- Includes full Integrated Development Environment
- Includes MPLAB software
- Compatible with most PICmicro programmers
- Includes a compiler for all the PICmicro devices.



Minimum system requirements for these items: Pentium PC running, 2000, ME, XP; CD-ROM drive; 64MB RAM; 10MB hard disk space.


Flowcode will run on XP or later operating systems

### FLOWCODE FOR PICmicro V4

Flowcode is a very high level language programming system based on flowcharts. Flowcode allows you to design and simulate complex systems in a matter of minutes. A powerful language that uses macros to facilitate the control of devices like 7-segment displays, motor controllers and LCDs. The use of macros allows you to control these devices without getting bogged down in understanding the programming. When used in conjunction with the Version 3 development board this provides a seamless solution that allows you to program chips in minutes.

- Requires no programming experience
- Allows complex PICmicro applications to be designed quickly
- Uses international standard flow chart symbols
- Full on-screen simulation allows debugging and speeds up the development process.
- Facilitates learning via a full suite of demonstration tutorials
- Produces ASM code for a range of 18, 28 and 40-pin devices
- 16-bit arithmetic strings and string manipulation
- Pulse width modulation
- I2C.

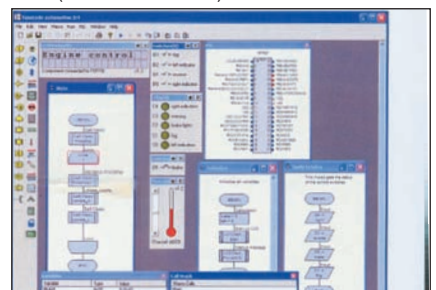New features of Version 4 include panel creator, in circuit debug, virtual networks, C code customisation, floating point and new components. The Hobbyist/Student version is limited to 4K of code (8K on 18F devices)



## PRICES

**Prices for each of the CD-ROMs above are:**  
*(Order form on next page)*

(UK and EU customers add VAT at 17.5% to 'plus VAT' prices)

Hobbyist/Student .....	£45	inc VAT
Institutional (Schools/HE/FE/Industry) .....	£99	plus VAT
Institutional/Professional 10 user (Network Licence) .....	£350	plus VAT
Site Licence .....	£699	plus VAT
Flowcode Institutional (Schools/HE/FE/Industry) .....	£149	plus VAT
Flowcode 10 user (Network Licence) .....	£399	plus VAT
Flowcode Site Licence .....	£799	plus VAT

## SPECIAL PACKAGE OFFER

### TINA Pro V7 (Basic) + Flowcode V3 (Hobbyist/Student)

#### TINA Analogue, Digital, Symbolic, RF, MCU and Mixed-Mode Circuit Simulation, Testing and PCB Design

TINA Design Suite is a powerful yet affordable software package for analysing, designing and real time testing analogue, digital, MCU, and mixed electronic circuits and their PCB layouts. You can also analyse RF, communication, optoelectronic circuits, test and debug microcontroller applications.

Enter any circuit (up to 100 nodes) within minutes with TINA's easy-to-use schematic editor. Enhance your schematics by adding text and graphics. Choose components from the large library containing more than 10,000 manufacturer models. Analyse your circuit through more than 20 different analysis modes or with 10 high tech virtual instruments. Present your results in TINA's sophisticated diagram windows, on virtual instruments, or in the live interactive mode where you can even edit your circuit during operation.

Customise presentations using TINA's advanced drawing tools to control text, fonts, axes, line width, colour and layout. You can create, and print documents directly inside TINA or cut and paste your results into your favourite word-processing or DTP package.

TINA includes the following Virtual Instruments: Oscilloscope, Function Generator, Multimeter, Signal Analyser/Bode Plotter, Network Analyser, Spectrum Analyser, Logic Analyser, Digital Signal Generator, XY Recorder.


**Flowcode V3 (Hobbyist/Student)** – For details on Flowcode, see the previous page.

This offer gives you two separate CD-ROMs – the software will need registering (FREE) with Designsoft (TINA) and Matrix Multimedia (Flowcode), details are given within the packages.

**Get TINA + Flowcode for a total of just £68, including VAT and postage.**

**£68.00  
inc. VAT  
and p&p**

## DIGITAL WORKS 3.0

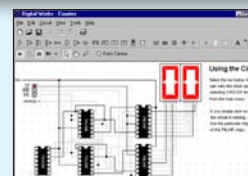

### Counter project

Digital Works Version 3.0 is a graphical design tool that enables you to construct digital logic circuits and analyze their behaviour. It is so simple to use that it will take you less than 10 minutes to make your first digital design. It is so powerful that you will never outgrow its capability ● Software for simulating digital logic circuits ● Create your own macros – highly scalable ● Create your own circuits, components, and i.c.s ● Easy-to-use digital interface ● Animation brings circuits to life ● Vast library of logic macros and 74 series i.c.s with data sheets ● Powerful tool for designing and learning.

**Hobbyist/Student £45 inc. VAT.**

**Institutional £99 plus VAT.**

**Institutional 10 user £249 plus VAT.**

**Site Licence £599 plus VAT.**

## PROJECT DESIGN WITH CROCODILE TECHNOLOGY

### An Interactive Guide to Circuit Design

An interactive CD-ROM to guide you through the process of circuit design. Choose from an extensive range of input, process and output modules, including CMOS Logic, Op-Amps, PIC/PICAXE, Remote Control Modules (IR and Radio), Transistors, Thyristors, Relays and much more. Click Data for a complete guide to the pin layouts of i.c.s, transistors etc. Click More Information for detailed background information with many animated diagrams.

Nearly all the circuits can be instantly simulated in Crocodile Technology\* (not included on the CD-ROM) and you can customise the designs as required.

#### WHAT'S INCLUDED


Light Modules, Temperature Modules, Sound Modules, Moisture Modules, Switch Modules, Astables including 555, Remote Control (IR & Radio), Transistor Amplifiers, Thyristor, Relay, Op-Amp Modules, Logic Modules, 555 Timer, PIC/PICAXE, Output Devices, Transistor Drivers, Relay Motor Direction & Speed Control, 7 Segment Displays, Data sections with pinouts etc., Example Projects, Full Search Facility, Further Background Information and Animated Diagrams.

#### Runs in Microsoft Internet Explorer

\*All circuits can be viewed, but can only be simulated if your computer has Crocodile Technology version 410 or later. A free trial version of Crocodile Technology can be downloaded from: [www.crocodile-clips.com](http://www.crocodile-clips.com).

Animated diagrams run without Crocodile Technology.

**Over 150 pages  
Over 600 images**

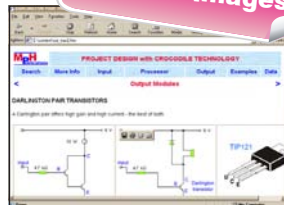

## ELECTRONIC COMPONENTS PHOTOS

A high quality selection of over 200 jpg images of electronic components. This selection of high resolution photos can be used to enhance projects and presentations or to help with training and educational material. They are royalty free for use in commercial or personal printed projects, and can also be used royalty free in books, catalogues, magazine articles as well as worldwide web pages (subject to restrictions – see licence for full details). Now contains Irfan View image software for Windows, with quick-start notes included.

Price **£19.95** inc. VAT



Minimum system requirements for these CD-ROMs: Pentium PC, CD-ROM drive, 32MB RAM, 10MB hard disk space. Windows 2000/ME/XP, mouse, sound card, web browser.

## Please send me: CD-ROM ORDER FORM

- ☐ Electronic Projects
- ☐ Electronic Circuits & Components V2.0
- ☐ Analogue Electronics
- ☐ Digital Electronics V2.0
- ☐ Analogue Filters (Hobbyist/Student Only)
- ☐ Electronics CAD Pack
- ☐ Robotics & Mechatronics
- ☐ Assembly for PICmicro V3
- ☐ 'C' for 16 Series PICmicro V4
- ☐ Flowcode V4 for PICmicro
- ☐ Digital Works 3.0

#### Version required:

- ☐ Hobbyist/Student
- ☐ Institutional
- ☐ Institutional/Professional 10 user
- ☐ Site licence

**Note:** The software on each version is the same, only the licence for use varies.

- ☐ PICmicro Development Board V3 (hardware)

- ☐ TINA Pro V7 Basic + Flowcode V3 Hobbyist/Student
- ☐ Electronic Components Photos; Version 1.1
- ☐ Project Design – Single User
- ☐ Project Design – Multiple User (under 500 students)
- ☐ Project Design – Multiple User (over 500 students)

Full name: .....

Address: .....

Post code: ..... Tel. No: .....

Signature: .....

☐ I enclose cheque/PO in £ sterling payable to WIMBORNE PUBLISHING LTD for £ .....

☐ Please charge my Visa/Mastercard/Maestro: £ .....

Valid From: ..... Card expiry date: .....

Card No: ..... Maestro Issue No. ....

Card Security Code ..... (The last 3 digits on or just under the signature strip)



## ORDERING ALL PRICES INCLUDE UK POSTAGE

Student/Single User/Standard Version price includes postage to most countries in the world EU residents outside the UK add £5 for airmail postage per order

**Institutional, Multiple User and Deluxe Versions** – overseas readers add £5 to the basic price of each order for airmail postage (**do not add VAT** unless you live in an EU (European Union) country, then add 17.5% VAT or provide your official VAT registration number).

**Send your order to:**  
**Direct Book Service**  
**Wimborne Publishing Ltd**  
**113 Lynwood Drive, Merley, Wimborne,**  
**Dorset BH21 1UU**  
 To order by phone ring  
**01202 873872. Fax: 01202 874562**  
 Goods are normally sent within seven days  
**E-mail: [orders@wimborne.co.uk](mailto:orders@wimborne.co.uk)**  
**Online shop:**  
**[www.epemag.com](http://www.epemag.com)**





# Max's Cool Beans

By Max The Magnificent

## So much to do, so little time...

I don't know about you, but my days are full to bursting with 'stuff' to do. In the last couple of weeks as I pen these words, for example, I've presented to NASA and been involved in an on-stage debate at the *Embedded Systems Conference (ESC)* in Silicon Valley.

## NASA and the JPL

First, I flew out to the Jet Propulsion Laboratory (JPL) in Pasadena, California, to give a presentation to a bunch of NASA/JPL folks about the state-of-the-art in FPGA technologies, including devices and design and verification tools.

As soon as I'd been checked in through security at JPL (which was about five minutes before I somehow managed to lose my security badge), the first thing I saw was a picture of myself plastered on a video screen accompanying an announcement of my talk. (My mother will 'dine out' at her hairdressers for weeks on this.)

Truth to tell, I was a wee bit nervous about giving this talk because the folks at JPL are all super-clever and you always worry that you are going to make a bosh of the whole thing. In the event, however, my presentation seemed to go down rather well, and it's spawned some interesting projects that I will discuss in a future column.

Following my talk, the folks at the JPL were kind enough to give me a guided tour, and I got to see all sorts of mega-cool things, such as the laboratory in which they are assembling and testing the next-generation Mars Rover.

Compared to previous rovers, this one is going to be a monster (about the size of a small car). This means that they can't land it the way they did the previous rovers (surrounding them in balloons and bouncing them along the surface of Mars until they come to a halt). So they showed me a simulation of the solution they've decided upon.

The idea is that everything is packed in a large capsule that hurls in through the atmosphere. Once things have slowed down sufficiently, the heat shield is dumped and a parachute is deployed. This is where things start to get really interesting. As the capsule nears the ground the parachute is discarded and a rocket system fires up. The rocket flies around until it decides on the best landing location, and then the rover is lowered to the ground on cables with the rocket still firing. Once the rover is on the ground, the cables disengage and the rocket flies off and lands itself somewhere close by.

## The Embedded conference

This year is turning out to be a big one for yours truly with regard to the *Embedded Systems Conference (ESC)*. Actually, this is a series of conferences. The one I just attended was in Silicon Valley. There's another one in Bangalore, India, in July (I'll be presenting a couple of papers there), yet another one later on in the year in Boston, and quite possibly others of which I'm not currently aware.

There were a couple of items of interest to me personally with regard to *ESC* Silicon Valley. First, the keynote presentation was given by Dr Michio Kaku, who is a theoretical physicist specialising in string field theory (this is like string theory, but more complicated). Dr Kaku is also a futurologist, an author, and a radio and TV personality who is incredibly good at explaining science to the masses in general, and to me in particular.

After Dr Kaku's very amusing and interesting presentation, I was fortunate enough to be taken backstage to meet the man himself. In fact, I gave him an autographed copy of my book *Bebop to the Boolean Boogie (An Unconventional Guide to Electronics)*. He told me that he was sure he would enjoy reading it and I replied that I would be asking him questions later (I wonder if he did actually read it).

In addition to numerous meetings with various companies in which I saw next-generation technology demonstrations that made me squeal like a schoolgirl, I also took part in a live debate with microprocessor expert Jim Turley. This turned out to be a very popular event – the *ESC* Theatre was packed, and it was standing room only at the back (admittedly it wasn't a very big Theatre, but still...).

To be honest, I was a little nervous by the start of the debate. This was largely due to the fact that folks had been coming up to me all day assuring me that they were planning on attending, and telling me things about Jim like: 'He's incredibly clever' and 'He's a great speaker' and 'He's really very funny' ... and then they would pat me on the shoulder and say something like: 'Of course, you're very good as well, Max' (in an unconvincing sort of way).

Jim was arguing that if you are building an embedded system, your best option is to use an off-the-shelf microcontroller. By comparison, my position was that a large proportion of today's embedded systems include a field-programmable gate array (FPGA), in which case you are better off using some of the FPGA fabric to implement your microcontroller. The debate swung back and forth, with points being scored on both sides, but I held my own and – in fact – I actually think that I may have come out on top.

## It doesn't slow down

I wish I had a *Dr Who* TARDIS so that I could go away for a month to catch up (taking only a few minutes in elapsed time here in my office). But of course, there's no such luck, so now I'm back in the fray desperately trying to keep my nose above the water line. In addition to real work (ugh), I now have only a little over a week to create my slides and associated papers for *ESC* India and send them off to the folks in charge. (Although the conference isn't until July, they need the slides and papers early so as to add them into the conference proceedings.)

I'll be giving two presentations – the shorter one will be only 75 minutes, but the longer one is a full-day affair, in which I'll be speaking for over five hours. The result is that I'm going to require several hundred slides. And the real problem is that I only actually started work on this a few evenings ago (there's no time to do it in the day), so the sands of time are really starting to race through the cosmic hourglass. I'm too young for all of this... Stop the world, I want to get off! Oh well, until next time, have a good one!

**Check out 'The Cool Beans Blog' at [www.epemag.com](http://www.epemag.com)**

***Catch up with Max and his up-to-date topical discussions***



# READOUT

Email: [editorial@wimborne.co.uk](mailto:editorial@wimborne.co.uk)

Matt Pulzer addresses some of the general points readers have raised. Have you anything interesting to say? Drop us a line!

All letters quoted here have previously been replied to directly



**WIN AN ATLAS LCR ANALYSER WORTH £79**  
An Atlas LCR Passive Component Analyser, kindly donated by Peak Electronic Design Ltd, will be awarded to the author of the Letter Of The Month. The Atlas LCR automatically measures inductance from 1mH to 10H, capacitance from 1pF to 10,000µF and resistance from 1Ω to 2MΩ with a basic accuracy of 1%. [www.peakelec.co.uk](http://www.peakelec.co.uk)

## ★ LETTER OF THE MONTH ★

### Hells Bells and Decibels!

Dear Editor

Congratulations to Ian Bell on yet another terrifically informative article, 'Hells Bells and Decibels' (EPE May 2010), in his excellent *Circuit Surgery* series.

There are, however, I think, a couple of small errors in the penultimate paragraph of this article. In this paragraph, Ian calculates a value, in dBu, equal to the level of the dBV reference level, (1 volt), but calculated with respect to the dBu reference level (0.775V). Ian writes, '1dBV is equal to 2.2dBu'. This should actually read '0dBV is equal to 2.2dBu.' This is because 0dBV (and not 1dBV) is equal to 1V, which is the voltage level that, in this case, is being compared

to the reference level of 0.775V (0dBu), leading to the equation  $20 \times \log_{10}(1/0.775)$  which gives a result of 2.2dBu. Actually,  $1\text{dBV} = 1.122\text{V} = 3.2\text{dBu}$ , but this is an arbitrary signal level of no particular significance. Similarly, later in the same paragraph, '1dBu is equal to -2.2dBV' should, by similar reasoning, actually read '0dBu is equal to -2.2dBV.'

These are only minor errors when compared to the amount of technically accurate information in Ian's article, but I feel it is worth clarifying the issue, as it could be potentially quite confusing for an electronics enthusiast who is trying to get to grips with the concepts of dBu, dBV etc, which can be confusing enough when you first start trying to understand them!

It may be the case that these errors have been carried over from the EPE

March 09 *Circuit Surgery* article, entitled Interconnecting Audio Equipment, which states the same equivalences.

**Chris Hinchcliffe,  
Dorset, by email**

*Ian Bell replies... Thanks Chris, for pointing out this error, and for your positive comments about Circuit Surgery.*

*Interestingly, this error is widespread and appears in what should be reliable sources. After only a quick Internet search, I found two instruction manuals for profession audio equipment with the statement '1dBV equals +2.2dBu'.*

*Converting from dBu to dBV is straightforward; just subtract 2.218 from the dBu value. Similarly, add 2.218 to a dBV value to get the dBu equivalent.*

### Giving cold callers the cold shoulder

Dear Editor

I would like to offer a project suggestion for one of your readers or a commercial company.

I am an OAP, and I'm having a lot of trouble from 'cold calling' telephone calls (especially international ones). This is very annoying if callers ring when I am having an afternoon snooze; by the time I get to the phone it has gone off. The caller display usually says 'international call' or 'number withheld'. I have contacted British Telecom and registered for caller preference to stop cold calling, but they say they cannot stop international calls.

It should be possible to make a device to stop all calls ringing unless the number is listed on a personal call list, in which case the call would be passed through to ring as usual. If the number is not on the list, then it should be diverted to a telephone answer machine with no external ringing. The machine could say, 'This is a possible nuisance call filtering machine. Please leave your name and number and I will call back.' If you ring back and the original call was genuine, then the number could be

added to your personal list for future use. If no number is left, then the nuisance is solved.

There should also be a button to delete a number from your personal list if it is no longer required. It would be useful if the machine could take SIM cards, thereby saving a lot of retyping of a mobile phone list.

While it may take some time to enter all acceptable numbers, it would be time well spent if it cuts out all the nuisance calls. I feel there could be a big market for such a device.

**John Eley, Glenfield, Leics**

*I'm sure there is a fortune out there for the right design that screens out these pests – see the TrueCall unit available from Amazon for around £80. I've lost count of the number of times I've been offered the chance to clear my credit cards or take advantage of a unique opportunity to... what a waste of time.*

### Software annotation and explanation

Dear Editor

As someone who once programmed for a living, I can say with some authority that one

of the best ways to learn programming is to systematically work through someone else's documented code.

Now that so many designs incorporate PIC processors, and you have articles on how to program PICs, isn't it a pity that a design such as the *High-Accuracy Digital LC Meter* (Mar '10) provides downloadable code, but not a run through of the code that is inherent to the function of this device.

I would argue that in the case of a hybrid piece of hardware and software, it is meaningless to discuss the components of the circuit design unless you are also willing to go through the software programme.

Conversely, if you are willing to treat the software as a 'black box', why bother to describe the circuit? Why not just say, 'buy this kit, be careful that you solder the right components in the right place in the right orientation, and it should just work'.

To examine the circuit diagram implies that the reader wishes to understand it, perhaps with a view to designing hardware for him/herself. Unless s/he understands how to program, options will be limited.

Please consider providing at least an annotated listing with perhaps a flowchart and verbal description of the major control and decision points in the code.



It would be a major benefit to build something like this and then be able to understand what is happening inside the controller.

I realise the example that I mentioned may be a special case, where references are given to the originators of the code, but I meant to make a general point for all big projects like it.

**Brian Williams, by email**

*Brian, you make a good point and, ideally, if we had space we would give greater prominence to the software side of projects. Unfortunately, the complexity and size of many of the programs built into projects mean that space restrictions do seriously limit what is possible in a printed magazine.*

*We do have the 'unlimited' space of the Internet, and we will seriously consider your suggestion, at least for home-grown projects. However, we are not always able to publish documented code, as many contributors wish to protect their work from commercial exploitation.*

*Of course, we do cover software and programming elsewhere in EPE, and work hard to teach techniques and skills, particularly with respect to PICs.*

*When it comes to descriptions of the circuit, we give quite detailed explanations of operation, and I hope that rather than viewing the PIC as a 'black box' readers do understand that these devices are interfaced in a particular way and that the software performs tasks in a particular order and in a certain timeframe – perhaps a 'grey box'?!*

*I appreciate your observation, and where possible I will encourage authors to at least provide a flow chart and/or a bird's-eye-view annotation of relevant code.*

## Cheap routers

Dear Editor

I was glad to read, in April's *Net Work* column that Alan resolved his WLAN problems. I too have experienced cheap routers having a tendency to die after a couple of years in service – sometimes less.

I believe that as the devices are intended for home use, the manufacturers can make them cheaper by designing them on the assumption that they will not be kept powered up and running continuously from the day that they are bought. In contrast, more expensive commercial routers are designed to be always-on units, and so more attention is paid to factors like heat dissipation and component quality.

There is, however, a happy medium. I have a Linksys WRT54G at home that has been powered up and under fairly heavy load for nearly six years, with only the occasional weekend power down when the house is empty and maybe a week in the summer. So far, the only sign of wear is some discolouring of the PSU label from the constant heat. I guess the PSU may go one day, but it's a standard power connector, so not hard to replace.

The WRT54G is an excellent router, but it lacks an ADSL modem. When I moved to a non-cable area just over three years ago, this became a problem. The only decent router I could find that supported ADSL2+ was the Netgear DG834G, and I have to say, this is also an excellent router and

has been in constant use for almost three years (with the Linksys one still in service elsewhere).

The moral of the story is that you get what you pay for. Netgear and Linksys (a Cisco company) both make quality products for a reasonable price. Alan is right when he says you could pay up to £70 for one of these, but they can be found for much less, and when you consider they are far less likely to 'go pop' a year after the warranty expires, they work out good value.

Both of the mentioned routers have custom firmware available from the 'Open Source' community, which allows the more experimentally inclined to put them to some very imaginative uses.

Finally, could I beg anyone considering using mains-borne networking devices to visit [www.rsgb.org/plt](http://www.rsgb.org/plt). These devices work by injecting RF into the mains wiring in your house, effectively turning it into a large antenna.

This wasn't a problem once upon-a-time, when projects in magazines like *EPE* let you send a few bytes of information down the mains, but in order to get the tens of megabytes per second of data throughput that the market now demands, a very wideband RF signal is required, which inevitably interferes with the reception of weak or distant radio signals and threatens hobbies like short wave listening and amateur radio, as well as many, more important uses of our radio spectrum.

**Simon Alderson, by email**

PS. I picked up *EPE* for the first time in a couple of years after being reminded of it while searching out the link for Alan's excellent soldering tutorial for a friend. It was great to see lots of interesting projects in recent issues, well done team. I think I might have to re-subscribe again...

*Alan Winstanley replies... Many thanks for your comments and interest in Net Work.*

*Simon makes a valid point – consumer-grade routers (like most equipment these days) are made very much to a price, which shows in the number of hardware failures that I have seen, especially of plug-in switched-mode power supplies. I am quite alarmed sometimes by the temperature that routers reach during operation, and I view the meagre ventilation slots with suspicion. Thermal cyclical stresses affect reliability, so turning them on and off can reduce their life, but like you, I'm not convinced these devices are designed with always-on operation in mind.*

*It's certainly wise to shop around when sourcing new peripherals. The point I made in April's Net Work was that less well known makes, such as the Tenda W300D cost typically half the retail price of shrink-wrapped brands, but they needn't be ruled out merely because of their lower brand awareness.*

*Actually, I started my broadband life with a Linksys WRT54G stacked with a matching hub. I was impressed with its robustness, but various network issues arose after a while. A replacement Belkin WiFi router finished its life being powered from a spare PSU from Maplin before developing the ADSL fault I described in*

*Net Work. The latest Tenda is humming away on the desk as I type: there is plenty to like about it, and if it only lasts a couple of years I won't mind due to the low price.*

*Thank you also for reminding us that router firmware can be flash-upgraded by visiting the maker's website; but do remember that open-source flash upgrades should be chosen with great care.*

## USB power supply for hard drives

Dear Editor

The backed-up data on the external hard drive (as powered by the *USB Power Injector* circuit in the April '10 article) is presumably valuable or even irreplaceable. For the sake of a few extra cheap components, I'd protect the drive by a crowbar over-voltage limiter on the output of the supply. When the output volts exceed a threshold, a thyristor fires and blows the preceding fuse, shorting the power input to the hard drive in 'semiconductor time.'

Should the mains 'plugpack' supply fail, it could easily put a high voltage on the regulator in your circuit, exceeding its limits and causing it to go open-circuit.

As I often remind naive computer users, the hardware is replaceable. The data isn't – and is, hence, the most valuable part of your system.

**Godfrey Manning, Edgware, by email**

*Wise words Godfrey – reminds me of a good piece of advice I was once given: 'There are only two kinds of hard drive; ones that have failed, and ones that are going to fail!' Keep that in mind and take appropriate precautions with irreplaceable data*

## Desoldering advice

Dear Editor

I particularly enjoy Julian Edgars' *Recycle It!* feature. There is something very satisfying in rescuing usable bits 'n' bobs from something that would ordinarily be sent to a rubbish dump.

I was recently given a malfunctioning PC printer, from which I extracted the stepper motors, switches and various connectors. Understanding how to use the switch-mode power supply was beyond me, so I resorted to removing the large capacitors and dismantling the small transformers for the enamelled copper wire – good for experimenting with home made electric motors!

There were other useful components on the circuit board, but even after years of handling a soldering iron I've always found desoldering difficult. Any chance of an article on desoldering methods? I'm sure you and your team have learned many ways to do this.

Thanks for a great magazine.

**Simon Moore**

*Your wish is not only our command, but has been anticipated and met in full! Please see EPE online editor Alan Winstanley's excellent soldering (and desoldering) guide at: [www.epemag.wimborne.co.uk/solderfaq.htm](http://www.epemag.wimborne.co.uk/solderfaq.htm).*

# Net Work

Alan Winstanley



## A 3D view

Last month, I highlighted how Google Street View had soft-launched the remaining map coverage of the UK and other countries, making it possible to take a motorist's view of most of Britain's towns and 238,000 miles of trunk roads and country lanes. I showed a typical Street View scene with a car and caravan parked in the front yard of a home: the licence plate was clearly visible along with some items that might attract caravan thieves or inquisitive burglars. I duly 'reported a privacy problem' and succeeded in having the number plate blurred, but Google's reporting criteria means that only the householders themselves could tackle Google if the rest of their privacy was being compromised.

Just before my column went to press last month, the 3D Google Street View option had been withdrawn. Happily it has now been restored – just press 'T' on your keyboard to toggle 3D mode, or right-click on a Street View scene and choose 3D mode. Plastic 3D glasses can be bought from eBay for just a few pounds, but the effect is very modest.

If you would like to explore the world of 3D images, then sporting your 3D glasses, websites such as SkyTopia.com offer a freeware Windows program (untested by the writer) to create anaglyphs at: [www.skytopia.com/software/stereoptical/](http://www.skytopia.com/software/stereoptical/). YouTube also has many 3D anaglyph tutorials and videos, and [http://en.wikipedia.org/wiki/Anaglyph\\_image](http://en.wikipedia.org/wiki/Anaglyph_image) has more background information and history for anyone interested.

## The sound of beating TomToms

Google hasn't finished with us yet: back in the May issue I touched on the likelihood of in-car/on-bike satellite navigation based on Google Maps and Street View, and Google Maps Navigation Beta has been released right on cue (as reported in last month's *Everyday News*). It integrates its search engine with Satellite view, Maps and Street View, and is designed for Google's Android-based mobile phones with GPS. Hence, you need a data tariff (GPRS, 3G) to download data or maps from the Internet while on the move, so it is only usable when there is a suitable signal. A demo of Google Navigation on YouTube is at: [www.youtube.com/watch?v=tGXXK4jKN\\_jY](http://www.youtube.com/watch?v=tGXXK4jKN_jY).

Google's search algorithms come into their own when inputting waypoints: instead of laboriously typing a specific address (eg National Exhibition Centre, Birmingham) you could 'navigate to the In-Focus photography exhibition in Birmingham' and Google Navigation will figure out the rest. You can search by name – just speak or type in a business and Google Maps Navigation will, hopefully, find it and navigate there (hence the importance of businesses being listed in Google Local Business Centre). In the US, Google already offers live traffic flow data in selected cities, and it seems inevitable that they will do the same in the UK. They promise green, yellow or red routes that reflect the traffic congestion ahead.

Google is an incurable advertising junkie, and it probably won't be long before advertisements pop up on your Google Navigation display or (heaven forbid) speak to you, imploring you to divert into a nearby pizzeria – maybe the canny pizzeria owner will have bid more to win a higher ad placement than the nearby fish and chip shop in Google's advertising rankings.

The biggest attraction of Google Navigation is, of course, that it's free, unlike satnav systems such as TomTom, which lock their users into buying updates: a new TomTom map today is £40 (\$60) or you can subscribe to updates at about £20 (\$30) per year. Speed camera and traffic updates add £30 (\$45) to the annual bill.

I can't decide which will be better for the driver or biker. It remains to be seen how frequently Google's maps and street views will be updated, and there is still something to be said for pre-loading an entire map into a TomTom 'at leisure' and tracking your position using GPS, rather than hoping Google Navigation can stream tons of live data via a mobile GPRS/3G connection while on the move. Mobile Internet data is still a problem; I can drive for 10 or 15 miles without a TomTom traffic update because there is no signal available for my HTC mobile (which refreshes the TomTom wirelessly via Bluetooth). As network coverage improves this disparity will vanish, but I would not write off a self-contained satnav just yet.

## Too much information

For many travellers, Google Navigation will probably be the perfect solution, and Google's advertisers will ultimately agree.


This technology is a prime example of 'disruptive innovation', the term coined by Clayton Christensen (see [www.claytonchristensen.com/disruptive\\_innovation.html](http://www.claytonchristensen.com/disruptive_innovation.html)) to describe any technology that finds favour with users who are currently frustrated by a market's existing offerings. The 'new' upstart then evolves until current market players (present-day satnav suppliers) must either adapt or be squeezed out of existence. Digital cameras are a perfect example of how disruptive technology destroyed the 35mm camera market. TomTom has never stood still though, so an interesting technological battle is about to get under way.

While Google can place ever more free data at our disposal, it may become bloated by more options and advertising 'noise' as time goes by. Google Navigation will undoubtedly disrupt and eventually polarise the market between those running Google apps on an Android or iPhone, or those preferring to subscribe to a fully supported, paid-for satnav unit instead. – You know, a proper satnav.

You can Email the author at: [alan@epemag.demon.co.uk](mailto:alan@epemag.demon.co.uk) or share your views with the Editor at: [editorial@epemag.wimborne.co.uk](mailto:editorial@epemag.wimborne.co.uk).



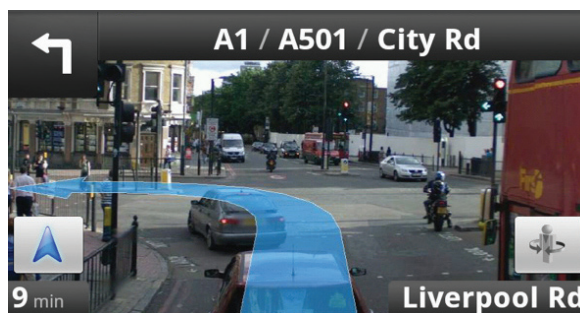A 3D Google Street View anaglyph of a Heroes & Villains Party held at a Shetlands Island pub. (Courtesy [streetviewsightings.co.uk](http://streetviewsightings.co.uk))



Google Navigation will superimpose your route onto Street View in real time – if your Android mobile phone can receive an adequate data signal



## Electronics Teach-In CD-ROM

### Mike Tooley

A broad-based introduction to electronics – find out how circuits work and what goes on inside them. The CD-ROM contains the whole Teach-In 2006 series (originally published in *EP&E*) in PDF form, plus interactive quizzes to test your knowledge, TINA circuit simulation software (a limited version – plus a specially written TINA Tutorial), together with simulations of the circuits in the Teach-In series, plus Flowcode (a limited version) a high level programming system for PIC microcontrollers based on flowcharts.

The Teach-In series covers everything from Electric Current through to Microprocessors and Microcontrollers and each part includes demonstration circuits to build on breadboards or to simulate on your PC. There is also a MW/LW Radio project in the Teach-In series.

CD-ROM

Order code ETI CDROM £8.50

### THE AMATEUR SCIENTIST 3-0 CD-ROM

The complete collection of The Amateur Scientist articles from *Scientific American* magazine. Over 1,000 classic science projects from a renowned source of winning projects. All projects are rated for cost, difficulty and possible hazards.

Plus over 1,000 pages of helpful science techniques that never appeared in *Scientific American*.


Exciting science projects in: Astronomy; Earth Science; Biology; Physics; Chemistry; Weather... and much more! The most complete resource ever assembled for hobbyists, and professionals looking for novel solutions to research problems.

Suitable for Mac, Windows, Linux or UNIX. 32MB RAM minimum, Netscape 4.0 or higher or Internet Explorer 4.0 or higher.

Over 1,000 projects

CD-ROM

Order code ASICD-ROM £19.95

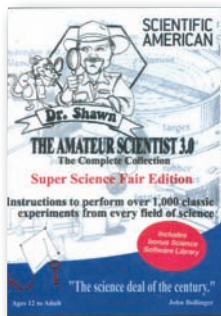

## PROJECT CONSTRUCTION

### IC 555 PROJECTS

E. A. Parr

Every so often a device appears that is so useful that one wonders how life went on before without it. The 555 timer is such a device. Included in this book are over 70 circuit diagrams and descriptions covering basic and general circuits, motor car and model railway circuits, alarms and noise makers as well as a section on 556, 558 and 559 timers. (Note. No construction details are given.) A reference book of invaluable use to all those who have any interest in electronics, be they professional engineers or designers, students or hobbyists.

167 pages

Order code BP44 £5.49

### HOW TO USE OSCILLOSCOPES AND OTHER TEST EQUIPMENT

R. A. Penfold

This book explains the basic function of an oscilloscope, gives a detailed explanation of all the standard controls, and provides advice on buying. A separate chapter deals with using an oscilloscope for fault finding on linear and logic circuits, plenty of example waveforms help to illustrate the control functions and the effects of various fault conditions. The function and use of various other pieces of test equipment are also covered, including signal generators, logic probes, logic pulser and crystal calibrators.

104 pages

Order code BP267 £5.49

# DIRECT BOOK SERVICE

The books listed have been selected by *Everyday Practical Electronics* editorial staff as being of special interest to everyone involved in electronics and computing. They are supplied by mail order direct to your door. Full ordering details are given on the last book page.

FOR A FURTHER SELECTION OF BOOKS AND CD-ROMS SEE  
THE UK SHOP ON OUR WEBSITE – [www.epemag.com](http://www.epemag.com)

All prices include UK postage

### ELECTRONIC PROJECT BUILDING FOR BEGINNERS

R. A. Penfold

This book is for complete beginners to electronic project building. It provides a complete introduction to the practical side of this fascinating hobby, including the following topics:

Component identification, and buying the right parts; resistor colour codes, capacitor value markings, etc; advice on buying the right tools for the job; soldering; making easy work of the hard wiring; construction methods, including stripboard, custom printed circuit boards, plain matrix boards, surface mount boards and wire-wrapping; finishing off, and adding panel labels; getting "problem" projects to work, including simple methods of fault-finding.

In fact everything you need to know in order to get started in this absorbing and creative hobby.

135 pages

Order code BP392 £5.99

### TEST EQUIPMENT CONSTRUCTION

R. A. Penfold

This book describes in detail how to construct some simple and inexpensive but extremely useful, pieces of test equipment. Stripboard layouts are provided for all designs, together with wiring diagrams where appropriate, plus notes on construction and use.

The following designs are included:-

AF Generator, Capacitance Meter, Test Bench Amplifier, AF Frequency Meter, Audio Multivoltmeter, Analogue Probe, High Resistance Voltmeter, CMOS Probe, Transistor Tester, TTL Probe. The designs are suitable for both newcomers and more experienced hobbyists.

104 pages

Order code BP248 £4.49

## COMPUTING

### COMPUTING FOR THE OLDER GENERATION

Jim Gatenby

Especially written for the over 50s, using plain English and avoiding technical jargon. Large clear type for easy reading.

Among the many practical and useful ideas for using your PC that are covered in this book are: Choosing, setting up and understanding your computer and its main components. Writing letters, leaflets, invitations, etc., and other word processing jobs. Keeping track of your finances using a spreadsheet. Recording details of holidays and other ideas using a database. Using the Internet to find useful information, and email to keep in touch with family and friends. Making 'back-up' copies of your work and checking for viruses. How to use Windows XP to help people with impaired vision, hearing or mobility.

Provides the basic knowledge so you can gain enough confidence to join the local computer class.

308 pages

Order code BP601 £8.99

### THE INTERNET FOR THE OLDER GENERATION

Jim Gatenby

Especially written for the over 50s. Uses only clear and easy-to-understand language. Larger type size for easy reading. Provides basic knowledge to give you confidence to join the local computer class.

This book explains how to use your PC on the Internet and covers amongst other things: Choosing and setting up your computer for the Internet. Getting connected to the Internet. Sending and receiving emails, photographs, etc., so that you can keep in touch with family and friends all over the world. Searching for and saving information on any subject. On-line shopping and home banking. Setting up your own simple web site.

228 pages

Order code BP600 £8.99

## RADIO


### SETTING UP AN AMATEUR RADIO STATION

I. D. Poole

The aim of this book is to give guidance on the decisions which have to be made when setting up any amateur radio or short wave listening station. Often the experience which is needed is learned by one's mistakes, however, this can be expensive. To help overcome this, guidance is given on many aspects of setting up and running an efficient station. It then proceeds to the steps that need to be taken in gaining a full transmitting licence.

Topics covered include: The equipment that is needed; Setting up the shack; Which aerials to use; Methods of construction; Preparing for the licence.

Temporarily out of print

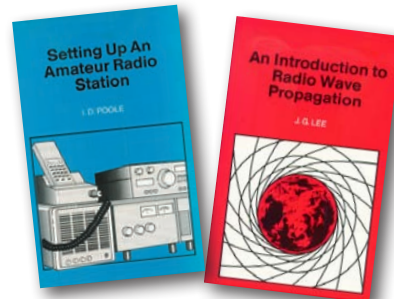

### 25 SIMPLE INDOOR AND WINDOW AERIALS

E. M. Noll

Many people live in flats and apartments or other types of accommodation where outdoor aerials are prohibited, or a lack of garden space etc. prevents aerials from being erected. This does not mean you have to forgo shortwave-listening, for even a 20-foot length of wire stretched out along the skirting board of a room can produce acceptable results. However, with some additional effort and experimentation one may well be able to improve performance further.

This concise book tells the story, and shows the reader how to construct and use 25 indoor and window aerials that the author has proven to be sure performers.

50 pages

Order code BP136 £2.25

### AN INTRODUCTION TO RADIO WAVE PROPOGATION

J.G. Lee

Radio wave propagation is one of the more important discoveries made in the early 20th century. Although technology lagged behind early experimenters pursued this newly discovered phenomenon eagerly for, in understanding the physics of propagation, they were discovering more about our Universe and its workings.

Radio wave propagation has its origins in the world of solar physics. The Sun's radiation provides the mechanism for the formation of the ionosphere. How the ionosphere is formed, and how it provides long-distance communication, is carefully explained. Non-ionospheric propagation, including 'moonbounce' or satellite communications, is covered as well.

This book has been written with the average electronic hobbyist in mind. Technical language and mathematics have been kept to a minimum in order to present a broad, yet clear, picture of the subject. The radio amateur, as well as the short-wave listener, will find explanations of the propagation phenomena which both experience in their pursuit of communications enjoyment.

116 pages

Order code BP293 £4.45

## THEORY AND REFERENCE

### BEBOP TO THE BOOLEAN BOOGIE

Second Edition


Clive (call me Max) Maxfield

This book gives the "big picture" of digital electronics. This in-depth, highly readable, guide shows you how electronic devices work and how they're made. You'll discover how transistors operate, how printed circuit boards are fabricated, and what the innards of memory ICs look like. You'll also gain a working knowledge of Boolean Algebra and Karnaugh Maps, and understand what Reed-Muller logic is and how it's used. And there's much, MUCH more. The author's tongue-in-cheek humour makes it a delight to read, but this is a REAL technical book, extremely detailed and accurate.

Contents: Fundamental concepts; Analog versus digital; Conductors and insulators; Voltage, current, resistance, capacitance and inductance; Semiconductors; Primitive logic functions; Binary arithmetic; Boolean algebra; Karnaugh maps; State diagrams, tables and machines; Analog-to-digital and digital-to-analog; Integrated circuits (ICs); Memory ICs; Programmable ICs; Application-specific integrated circuits (ASICs); Circuit boards (PWBs and DWBs); Hybrids; Multichip modules (MCMs); Alternative and future technologies.

470 pages

Order code BEB1 £35.99

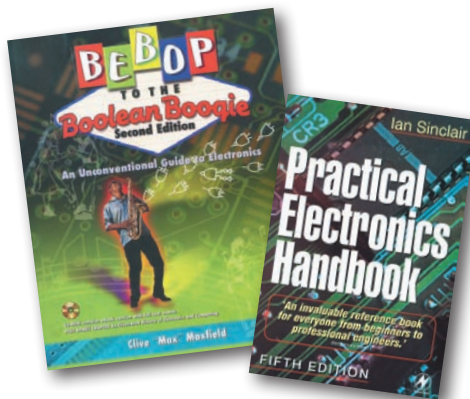

### INTERFACING PIC MICROCONTROLLERS

Martin Bates

An essential guide to PIC interfacing techniques, using circuit simulation to aid learning.

Explore in detail microcontroller interfacing techniques using the popular PIC 16F877. Work through step-by-step examples interactively using circuit simulation software, supplied as assembly source code.

Interfacing PIC Microcontrollers provides a thorough introduction to interfacing techniques for students, hobbyists and engineers looking to take their knowledge of PIC application development to the next level. Each chapter ends with suggestions for further applications, based on the examples given, and numerous line drawings illustrate application of the hardware.

Step-by-step examples in assembly language are used to illustrate a comprehensive set of interfaces, and these can be run interactively on circuit simulation software, used to aid understanding without the need to build real hardware.

A companion website includes all examples in the text which can be downloaded together with a free version of Proteus's ISIS Lite.

298 pages

Order code NE48 £30.99

### GETTING THE MOST FROM YOUR MULTIMETER

R. A. Penfold

This book is primarily aimed at beginners and those of limited experience of electronics. Chapter 1 covers the basics of analogue and digital multimeters, discussing the relative merits and the limitations of the two types.

In Chapter 2 various methods of component checking are described, including tests for transistors, thyristors, resistors, capacitors and diodes. Circuit testing is covered in Chapter 3, with subjects such as voltage, current and continuity checks being discussed.

In the main little or no previous knowledge or experience is assumed. Using these simple component and circuit testing techniques the reader should be able to confidently tackle servicing of most electronic projects.

102 pages

Order code BP239 £5.49

### DIGITAL GATES AND FLIP-FLOPS

Ian R. Sinclair

This book, intended for enthusiasts, students and technicians, seeks to establish a firm foundation in digital electronics by treating the topics of gates and flip-flops thoroughly and from the beginning.

No background other than a basic knowledge of electronics is assumed, and the more theoretical topics are explained from the beginning, as also are many working practices. The book concludes with an explanation of microprocessor techniques as applied to digital logic.

200 pages

Order code PC106 £9.95

### OPERATIONAL AMPLIFIER USER'S HANDBOOK

R. A. Penfold

The first part of this book covers standard operational amplifier based "building blocks" (integrator, precision rectifier, function generator, amplifiers, etc), and considers the ways in which modern devices can be used to give superior performance in each one. The second part describes a number of practical circuits that exploit modern operational amplifiers, such as high slew-rate, ultra low noise, and low input offset devices. The projects include: Low noise tape preamplifier, low noise RIAA preamplifier, audio power amplifiers, d.c. power controllers, opto-isolator audio link, audio millivolt meter, temperature monitor, low distortion audio signal generator, simple video fader, and many more.

120 pages

Order code BP335 £5.45

### PRACTICAL ELECTRONICS HANDBOOK -

Fifth Edition, Ian Sinclair

Provides a practical and comprehensive collection of circuits, rules of thumb and design data for professional engineers, students and enthusiasts, and therefore enough background to allow the understanding and development of a range of basic circuits.

Contents: Passive components, Active discrete components, Circuits, Linear I.C.s, Energy conversion components, Digital I.C.s, Microprocessors and microprocessor systems, Transferring digital data, Digital-analogue conversions, Computer aids in electronics, Hardware components and practical work, Micro-controllers and PLCs, Digital broadcasting, Electronic security.

440 pages

Order code NE21 £32.50

### BEBOP BYTES BACK (and the Bebop Computer Simulator) CD-ROM

Clive (Max) Maxfield

and Alvin Brown

This follow-on to Bebop to the Boolean Boogie is a multimedia extravaganza of information about how computers work. It picks up where "Bebop I" left off, guiding you through the fascinating world of computer design... and you'll have a few chuckles, if not belly laughs, along the way. In addition to over 200 megabytes of mega-cool multimedia, the CD-ROM contains a virtual microcomputer, simulating the motherboard and standard computer peripherals in an extremely realistic manner. In addition to a wealth of technical information, myriad nuggets of trivia, and hundreds of carefully drawn illustrations, the CD-ROM contains a set of lab experiments for the virtual microcomputer that let you recreate the experiences of early computer pioneers. If you're the slightest bit interested in the inner workings of computers, then don't dare to miss this!

Over 800 pages in Adobe Acrobat format

CD-ROM

Order code BEB2 CD-ROM £21.95



## MUSIC, AUDIO AND VIDEO

### QUICK GUIDE TO DIGITAL AUDIO RECORDING

Ian Waugh

Covers:

- What computer system you need
- Sound and digital audio essentials
- What to look for in a sound card
- What effects to use
- The art of mixing
- How to burn your music to CD
- How to post your songs on the Web

All modern music recordings use digital audio technology. Now everyone with a computer can produce CD-quality recordings and this book shows you how. Written in a clear and straightforward style, it explains what digital audio recording is, how to use it, the equipment you need, what sort of software is available and how to achieve professional results.

Computer-based recording is the future of music and this book shows how you can join the revolution now.

208 pages

Order code PC121 £7.95

### QUICK GUIDE TO MP3 AND DIGITAL MUSIC

Ian Waugh


MP3 files, the latest digital music format, have taken the music industry by storm. What are they? Where do you get them? How do you use them? Why have they thrown record companies into a panic? Will they make music easier to buy? And cheaper? Is this the future of music?

All these questions and more are answered in this concise and practical book which explains everything you need to know about MP3s in a simple and easy-to-understand manner. It explains:

How to play MP3s on your computer; How to use MP3s with handheld MP3 players; Where to find MP3s on the Web; How MP3s work; How to tune into Internet radio stations; How to create your own MP3s; How to record your own CDs from MP3 files; Other digital audio music formats.

60 pages

Order code PC119 £7.45

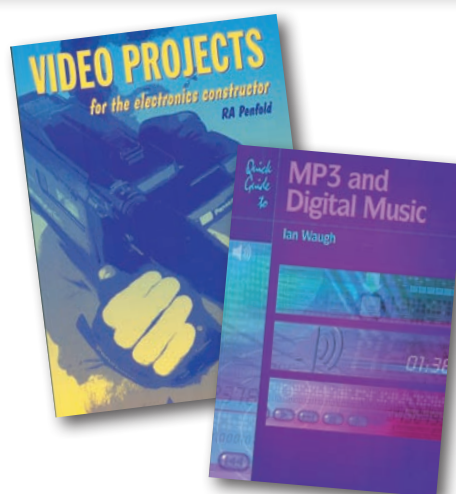

### ELECTRONIC PROJECTS FOR VIDEO ENTHUSIASTS

R. A. Penfold

This book provides a number of practical designs for video accessories that will help you get the best results from your camcorder and VCR. All the projects use inexpensive components that are readily available, and they are easy to construct. Full construction details are provided, including stripboard layouts and wiring diagrams. Where appropriate, simple setting up procedures are described in detail; no test equipment is needed.

The projects covered in this book include: Four channel audio mixer, Four channel stereo mixer, Dynamic noise limiter (DNL), Automatic audio fader, Video faders, Video wipers, Video crispener, Mains power supply unit.

109 pages

Order code BP356 £5.45

### VIDEO PROJECTS FOR THE ELECTRONICS CONSTRUCTOR

R. A. Penfold

Written by highly respected author R. A. Penfold, this book contains a collection of electronic projects specially designed for video enthusiasts. All the projects can be simply constructed, and most are suitable for the newcomer to project construction, as they are assembled on stripboard.

There are faders, wipers and effects units which will add sparkle and originality to your video recordings, an audio mixer and noise reducer to enhance your soundtracks and a basic computer control interface. Also, there's a useful selection on basic video production techniques to get you started.

Complete with explanations of how the circuit works, shopping lists of components, advice on construction, and guidance on setting up and using the projects, this invaluable book will save you a small fortune.

Circuits include: video enhancer, improved video enhancer, video fader, horizontal wiper, improved video wiper, negative video unit, fade to grey unit, black and white keyer, vertical wiper, audio mixer, stereo headphone amplifier, dynamic noise reducer, automatic fader, pushbutton fader, computer control interface, 12 volt mains power supply.

Temporarily out of print

**ALL PRICES INCLUDE  
UK POST & PACKING**



# FAULT FINDING, CIRCUITS AND DESIGN

## PIC BASIC PROJECTS – 30 PROJECTS USING PICBASIC AND PICBASIC PRO

**Dogan Ibrahim**  
Covering the PICBASIC and PICBASIC PRO compilers, this thoroughly revised edition, previously entitled PICBASIC Programming and Projects, provides an easy-to-use toolkit for developing applications with PICBASIC. Numerous simple projects give clear and concrete examples of how PICBASIC can be used to develop electronics applications, while larger and more advanced projects describe program operation in detail and give useful insights into developing more involved microcontroller applications.

Packed with simple and advanced projects which show how to programme a variety of interesting electronic applications using PICBASIC. Covers the PIC16F627 and PIC16F73, and the popular PIC16F84 and PIC16F877 models. The CDROM includes program source files, HEX code, data sheets of devices, sensors and schematics of the circuits used in the book.

358 pages

Order code NE44 £26.00

## HOW ELECTRONIC THINGS WORK – AND WHAT TO DO WHEN THEY DON'T

**Robert Goodman**  
You never again have to be flummoxed, flustered or taken for a ride by a piece of electronics equipment. With this fully illustrated, simple-to-use guide, you will get a grasp on the workings of the electronic world that surrounds you – and even learn to make your own repairs.

You don't need any technical experience. This book gives you: Clear explanations of how things work, written in everyday language. Easy-to-follow, illustrated instructions on using test equipment to diagnose problems. Guidelines to help you decide for or against professional repair. Tips

**BOOK + CD-ROM**

on protecting your expensive equipment from lightning and other electrical damage, lubrication and maintenance suggestions.

Covers: colour TVs, VCRs, radios, PCs, CD players, printers, telephones, monitors, camcorders, satellite dishes, and much more!

394 pages

Order code MGH3 £21.99

## PIC IN PRACTICE (2nd Edition)

**David W. Smith**

A graded course based around the practical use of the PIC microcontroller through project work. Principles are introduced gradually, through hands-on experience, enabling hobbyists and students to develop their understanding at their own pace. The book can be used at a variety of levels.

Contents: Introduction to the PIC microcontroller; Programming the 16F84 microcontroller; Introductory projects; Headers, porting code – which micro?; Using inputs; Keypad scanning; Program examples; The 16C54 microcontroller; Alphanumeric displays; Analogue to digital conversion; Radio transmitters and receivers; EEPROM data memory; Interrupts; The 12 series 8-pin microcontroller; The 16F87X microcontroller; The 16F62X microcontroller; Projects; Instruction set, files and registers; Appendices; Index.

308 pages

Order code NE39 £24.99

## PRACTICAL ELECTRONIC FAULT FINDING AND TROUBLESHOOTING

**Robin Pain**

To be a real fault finder, you must be able to get a feel for what is going on in the circuit you are examining. In this book Robin Pain explains the basic techniques needed to be a fault finder.

Simple circuit examples are used to illustrate principles and concepts fundamental to the process of fault finding. This is not a book of theory, it is a book of practical tips, hints and rules of thumb, all of which will equip the reader to tackle any job. You may be an engineer or technician in search of information and guidance, a college student, a hobbyist building a project from a magazine, or simply a keen self-taught amateur who is interested in electronic fault finding but finds books on the subject too mathematical or specialised.

The fundamental principles of analogue and digital fault finding are described (although, of course, there is no such thing as a "digital fault" – all faults are by nature analogue). This book is written entirely for a fault finder using only the basic fault-finding equipment: a digital multimeter and an oscilloscope. The treatment is non-mathematical (apart from Ohm's law) and all jargon is strictly avoided.

274 pages

Order code NE22 £41.99

## A BEGINNERS GUIDE TO CMOS DIGITAL ICs

**R. A. Penfold**

Getting started with logic circuits can be difficult, since many of the fundamental concepts of digital design tend to seem rather abstract, and remote from obviously useful applications. This book covers the basic theory of digital electronics and the use of CMOS integrated circuits, but does not lose sight of the fact that digital electronics has numerous "real world" applications.

The topics covered in this book include: the basic concepts of logic circuits; the functions of gates, inverters and other logic "building blocks"; CMOS logic i.e. characteristics, and their advantages in practical circuit design; oscillators and monostables (timers); flip/flops, binary dividers and binary counters; decade counters and display drivers.

119 pages

Order code BP333 £5.45

## AUDIO AMPS

### BUILDING VALVE AMPLIFIERS

**Morgan Jones**


The practical guide to building, modifying, fault-finding and repairing valve amplifiers. A hands-on approach to valve electronics – classic and modern – with a minimum of theory. Planning, fault-finding, and testing are each illustrated by step-by-step examples.

A unique hands-on guide for anyone working with valve (tube in USA) audio equipment – as an electronics experimenter, audiophile or audio engineer.

Particular attention has been paid to answering questions commonly asked by newcomers to the world of the vacuum tube, whether audio enthusiasts tackling their first build, or more experienced amplifier designers seeking to learn the ropes of working with valves. The practical side of this book is reinforced by numerous clear illustrations throughout.

368 pages

Order code NE40 £29.00

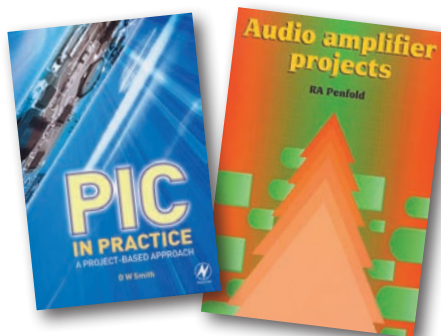

### AUDIO AMPLIFIER PROJECTS

**R. A. Penfold**

A wide range of useful audio amplifier projects, each project features a circuit diagram, an explanation of the circuit operation and a stripboard layout diagram. All constructional details are provided along with a shopping list of components, and none of the designs requires the use of any test equipment in order to set up properly. All the projects are designed for straightforward assembly on simple circuit boards.

Circuits include: High impedance mic preamp, Low impedance mic preamp, Crystal mic preamp, Guitar and GP preamplifier, Scratch and rumble filter, RIAA preamplifier, Tape preamplifier, Audio limiter, Bass and treble tone controls, Loudness filter, Loudness control, Simple graphic equaliser, Basic audio mixer, Small (300mW) audio power amp, 6 watt audio power amp, 20/32 watt power amp and power supply, Dynamic noise limiter.

A must for audio enthusiasts with more sense than money!

116 pages

Order code PC113 £10.95 £5.45

### VALVE AMPLIFIERS

**Second Edition. Morgan Jones**

This book allows those with a limited knowledge of the field to understand both the theory and practice of valve audio amplifier design, such that they can analyse and modify circuits, and build or restore an amplifier. Design principles and construction techniques are provided so readers can devise and build from scratch, designs that actually work.

The second edition of this popular book builds on its main strength – exploring and illustrating theory with practical applications. Numerous new sections include: output transformer problems; heater regulators; phase splitter analysis; and component technology. In addition to the numerous amplifier and preamplifier circuits, three major new designs are included: a low-noise single-ended LP stage, and a pair of high voltage amplifiers for driving electrostatic transducers directly – one for headphones, one for loudspeakers.

288 pages

Order code NE33 £40.99

## BOOK ORDERING DETAILS

**All prices include UK postage.** For postage to Europe (air) and the rest of the world (surface) please add £3 per book. For the rest of the world airmail add £4 per book. CD-ROM prices include VAT and/or postage to anywhere in the world. Send a PO, cheque, international money order (£ sterling only) made payable to **Direct Book Service** or card details, Visa, Mastercard, or Maestro to: **DIRECT BOOK SERVICE, WIMBORNE PUBLISHING LIMITED, 113 LYNWOOD DRIVE, MERLEY, WIMBORNE, DORSET BH21 1UU.**

Books are normally sent within seven days of receipt of order, but please allow 28 days for delivery – more for overseas orders. Please check price and availability (see latest issue of *Everyday Practical Electronics*) before ordering from old lists.

For a further selection of books see the next two issues of *EPE*.  
Tel 01202 873872 Fax 01202 874562. E-mail: [dbs@wimborne.co.uk](mailto:dbs@wimborne.co.uk)  
Order from our online UK shop at: [www.epemag.com](http://www.epemag.com)

## BOOK ORDER FORM

Full name: .....

Address: .....

.....

.....

..... Post code: ..... Telephone No: .....

Signature: .....

☐ I enclose cheque/PO payable to DIRECT BOOK SERVICE for £ .....

☐ Please charge my card £ ..... Card expiry date: .....

Card Number ..... Maestro Issue No. ....

Valid From Date ..... Card Security Code ..... (the last three digits on or just below the signature strip)

Please send book order codes: .....

.....

Please continue on separate sheet of paper if necessary

# PCB SERVICE

Printed circuit boards for most recent *EPE* constructional projects are available from the *PCB Service*, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. Double-sided boards are **NOT plated through hole** and will require 'vias' and some components soldering to both sides. All prices include VAT and postage and packing. Add £1 per board for airmail outside of Europe. Remittances should be sent to **The PCB Service, Everyday Practical Electronics, Wimborne Publishing Ltd., 113 Lynwood Drive, Merley, Wimborne, Dorset BH21 1UU.** Tel: 01202 873872; Fax 01202 874562; Email: [orders@epemag.wimborne.co.uk](mailto:orders@epemag.wimborne.co.uk). On-line Shop: [www.epemag.com](http://www.epemag.com). Cheques should be crossed and made payable to *Everyday Practical Electronics* (Payment in £ sterling only).

**NOTE:** While 95% of our boards are held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery – overseas readers allow extra if ordered by surface mail. Back numbers or photocopies of articles are available if required – see the Back Issues page for details. **WE DO NOT SUPPLY KITS OR COMPONENTS FOR OUR PROJECTS.**

Please check price and availability in the latest issue.  
A large number of older boards are listed on, and can be ordered from, our website.

Boards can only be supplied on a payment with order basis.

PROJECT TITLE	ORDER CODE	COST
<b>JUNE '09</b>		
★ Spectacular Bike Wheel POV Display (double-sided)	711 (set of 3)	£23.73
★ Remote Volume Control & Preamplifier Module		
– Main Board	714	} set £9.20
– Display Board	715	
– Power Supply Board	716	
<b>JULY '09</b>		
★ Solar Water Heating System Controller		
– Main Board	712	} set £15.00
– Display Board	713	
★ PIC Probe (double-sided)	717	£9.50
★ Simple Data-Logging Weather Station		
– Main Board	718	} set £6.66
– RS232 Board	719	
<b>AUGUST '09</b>		
★ Fast Charger For NiMH Batteries	720	£6.66
★ Rolling Code Keyless Entry System		
– Main Board	721	£7.29
– Transmitter (2off)	722 (2off)	£6.18
<b>SEPTEMBER '09</b>		
PIC Programmer SOIC Converter	723	£5.07
★ Random Mains Timer	724	£9.51
<b>OCTOBER '09</b>		
1pps Driver for Quartz Clocks	725	£5.71
Minispot 455kHz Modulated Oscillator	726	£5.87
Prog. Ignition System for Cars		
– Ignition Unit	727	} set £11.10
– Ignition Coil Driver	728	
– LCD Hand Controller	729	
★ Guitar-To-MIDI System	730	£6.66
<b>NOVEMBER '09</b>		
Class-A Headphone Amplifier		
– Main (pair)	731	} set £9.99
– PSU	732	
Emergency 12V Lighting Controller	733	£7.20
★ Digital VFO With LCD Graphics Display (doubled sided)	734	£13.00
<b>DECEMBER '09</b>		
Knock Detector	735	£6.66
★ 12V/24V High-Current Motor Speed Controller		
– Main	736	} set £10.78
– Display	737	
<b>JANUARY '10</b>		
★ UHF Remote-Controlled Mains Switch	738	£7.93
★ UHF Remote Mains Switch Transmitter	739	£6.00
★ Playback Adapter For CD-ROM Drives	740	£7.61
<b>FEBRUARY '10</b>		
★ Charge Controller For 12V Lead-Acid Batteries	741	£6.66
★ Working Days Alarm Clock		
– Main (double-sided)	742	} set £25.00
– Display (double-sided)	743	
Low-cost LPT-To-I <sup>2</sup> C Interface	744	£6.30

PROJECT TITLE	ORDER CODE	COST
<b>MARCH '10</b>		
★ High-Accuracy Digital LC Meter – Main	745	} set £7.93
– Adaptor	746	
– Shorting Bar	747	
2-way Stereo Headphone Adaptor	748	£10.30
★ Shift Indicator and Rev Limiter For Cars – Main	749	} set £9.04
– Display	750	
<b>APRIL '10</b>		
USB Power Injector	597	£5.87
Alternative 12V 10A Power Supply	751	£7.16
LM3909 Replacement Module	752	£6.02
<b>MAY '10</b>		
★ Water Tank Level Meter	753	£6.66
dsPIC/PIC Programmer – Main Board	754	} set £8.56
– Adaptor	755	
<b>JUNE '10</b>		
★ PIC-Based Musical Tuning Aid	756	£8.24
★ Water Tank Level Meter – Base	757	} set £6.97
– Switch	758	
★ DSP Musiccolour	759	} set £14.99
– Display	760	
<b>JULY '10</b>		
★ ColdAlert Hypothermia Alarm	761	£6.98
★ Swimming Pool Alarm	762	£7.61

## EPE SOFTWARE

★ All software programs for *EPE* Projects marked with a star, and others previously published can be downloaded free from the Library on our website, accessible via our home page at: [www.epemag.com](http://www.epemag.com)

## PCB MASTERS

PCB masters for boards published from the March '06 issue onwards can also be downloaded from our website ([www.epemag.com](http://www.epemag.com)); go to the 'Library' section.

## EPE PRINTED CIRCUIT BOARD SERVICE

Order Code	Project	Quantity	Price
------------	---------	----------	-------

Name .....

Address .....

Tel. No. ....

I enclose payment of £ ..... (cheque/PO in £ sterling only) to:

## Everyday Practical Electronics



Card No. ....

Valid From ..... Expiry Date .....

Card Security No. .... Maestro Issue No. ....

Signature .....

**Note:** You can also order PCBs by phone, Fax or Email or via the Shop on our website on a secure server:

<http://www.epemag.com>



## EP<sup>3</sup> EVERYDAY PRACTICAL ELECTRONICS

Everyday Practical Electronics reaches more UK readers than any other UK monthly hobby electronics magazine, our sales figures prove it. We have been the leading monthly magazine in this market for the last twenty-four years.

### Versatile Programmable PIC On Screen Display System

Display text over any composite video signal




**PAL - NTSC compatible**

- Fully programmable
- I/O for sensor interfaces
- PIC 16F628A micro
- User definable fonts

Example code for MSF, cash register, 1-wire & GPS data display

**WWW.PIC-OSD.COM**

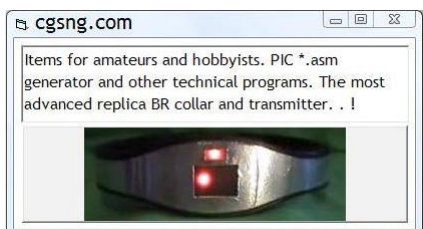

### CPS Solar

Solar panels, solar cells, and many more alternative energy products for battery charging etc, please visit our website for further info or call  
Tel: 0870 765 2334.  
**www.solarpanelsonline.co.uk**

**BTEC ELECTRONICS TECHNICIAN TRAINING**

NATIONAL ELECTRONICS  
VCE ADVANCED ICT  
HNC AND HND ELECTRONICS  
FOUNDATION DEGREES  
NVQ ENGINEERING AND IT  
DESIGN AND TECHNOLOGY

**LONDON ELECTRONICS COLLEGE**  
20 PENYVERN ROAD  
EARLS COURT, LONDON SW5 9SU  
TEL: (020) 7373 8721  
**www.lec.org.uk**

**spinvent.co.uk**

...invent with the Propeller microcontroller and Spin programming language from Parallax

**Projects & Hands-On Training for Students, Hobbyists & Professionals**

- USB Port interfacing
- Serial Port Interfacing
- C#/VB & MS-Excel Interfacing
- Microcontrollers
- Embedded C Programming
- CadSoft EAGLE Training for PCB
- KEIL uVision Training
- Building Upload/Download Sites
- Touch Typing Video Training
- C#/VB6/VB .Net School Projects

Order with confidence from any place in the world  
**www.csiLibrary.com**

**Robot Bits.co.uk**  
Robot Kits and Components  
**0845 5 191 282**

**BOWOOD ELECTRONICS LTD**  
Suppliers of Electronic Components  
Place a secure order on our website or call our sales line  
All major credit cards accepted  
Web: **www.bowood-electronics.co.uk**  
Unit 10, Boythorpe Business Park, Dock Walk, Chesterfield, Derbyshire S40 2QR. Sales: 01246 200222  
Send 60p stamp for catalogue

**CANTERBURY WINDINGS**  
UK manufacturer of toroidal transformers (10VA to 1kVA)  
All transformers made to order. No design fees. No minimum order.  
**www.canterburywindings.co.uk**  
**01227 450810**

**www.cstech.co.uk**

PIC Prototyping Kits  
PIC Programmers  
DTMF & CTCSS encoder & decoder kits

All in stock - Quality components - Low postage costs

**THIS SPACE COULD BE YOURS FOR JUST £25 plus VAT**  
Contact Stewart on 01202 873872  
**stewart.kearn@wimborne.co.uk**

**www.partridgeelectronics.co.uk**

Looking For Components To Repair Old Equipment?

**Miscellaneous**

KITS, TOOLS, COMPONENTS. S.A.E. Catalogue. SIR-KIT ELECTRONICS, 52 Severn Road, Clacton, CO15 3RB, **http://sir-kit.webs.com**

VALVES AND ALLIED COMPONENTS IN STOCK. Phone for free list. Valves, books and magazines wanted. Geoff Davies (Radio), tel. 01788 574774.



**ELECTRONICS TEACH-IN 3**

**AVAILABLE NOW FROM WH SMITH ONLY £7.99**

ALSO AVAILABLE FROM  
**DIRECT BOOK SERVICE**



# Europe's Largest Surplus Store

**20,000,000 Items on line NOW !**  
New items added daily

Established for over 25 years, UK company Display Electronics prides itself on offering a massive range of electronic and associated electro-mechanical equipment and parts to the Hobbyist, Educational and Industrial user. Many current and obsolete hard to get parts are available from our vast stocks, which include:

- ◆ 6,000,000 Semiconductors
- ◆ 5,000 Power Supplies
- ◆ 25,000 Electric Motors
- ◆ 10,000 Connectors
- ◆ 100,000 Relays & Contactors
- ◆ 2000 Rack Cabinets & Accessories
- ◆ 4000 Items of Test Equipment
- ◆ 5000 Hard Disk Drives

**We Ship Worldwide**

**Surplus Wanted**

**www.distel.co.uk**

Display Electronics  
29 / 35 Osborne Road  
Thornton Heath  
Surrey UK CR7 8PD

Telephone  
**[44] 020 8653 3333**  
Fax [44] 020 8653 8888

## Rechargeable Batteries With Solder Tags

### NIMH

AA 2000mAh .....£2.82  
C 4Ah .....£4.70  
D 9Ah .....£7.60  
PP3 150mAh .....£4.95



### NICAD

AA 650mAh .....£1.41  
C 2.5Ah .....£3.60  
D 4Ah .....£4.95
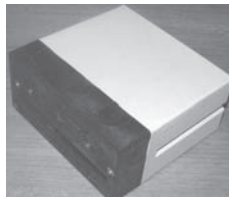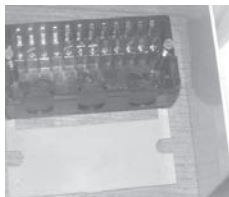
### Instrument case with edge connector and screw terminals

Size 112mm x 52mm x 105mm tall

This box consists of a cream base with a PCB slot, a cover plate to protect your circuit, a black lid with a 12 way edge connector and 12 screw terminals built in (8mm pitch) and 2 screws to hold the lid on. The cream bases have minor marks from dust and handling price £2.00 + VAT(=£2.35) for a sample or £44.00+VAT (=£51.70) for a box of 44.



866 battery pack originally intended to be used with an orbitel mobile telephone it contains 10 1.6Ah sub C batteries (42 x 22 dia. the size usually used in cordless screwdrivers etc.) the pack is new and unused and can be broken open quite easily £7.46 + VAT = **£8.77**



Please add £1.66 + VAT = £1.95 postage & packing per order

**JPG Electronics**

Shaws Row, Old Road, Chesterfield, S40 2RB.

Tel 01246 211202 Fax 01246 550959

www.JPGElectronics.com

Mastercard/Visa/Switch

Callers welcome 9.30 a.m. to 5.30 p.m. Monday to Saturday

**EPE EVERYDAY PRACTICAL ELECTRONICS**

## NEXT MONTH

### ULTRA-LD 200W POWER AMPLIFIER

A real treat for all you hifi buffs! This new amplifier module produces high power at very low distortion. In fact, as far as we are aware, it is the lowest distortion class-AB amplifier that has ever been published.

### A UV LIGHT BOX FOR MAKING PC BOARDS

The first of two articles this month devoted to making your own PCBs. Here, we show you how to make a UV Light Box with sophisticated PIC-controlled timer functions.

### PCB PRODUCTION

Next, we reveal all you need to know about actually making your boards with a primer on their production.

### DSP MUSICOLOUR PART 4: ADDING A REMOTE CONTROL

We conclude our popular series on the ultimate sound-to-light project by adding a handy low-cost, function-packed infra-red remote control.

### RECYCLE IT! – WATCHES

Making the most of discarded electronic watches.

## AUGUST '10 ISSUE – ON SALE 8 JULY

Content may be subject to change

## ADVERTISERS INDEX

BETA LAYOUT .....	21
CRICKLEWOOD .....	21
DISPLAY ELECTRONICS .....	72
ESR ELECTRONIC COMPONENTS .....	6, Cover (ii)
JAYCAR ELECTRONICS .....	4/5
JPG ELECTRONICS .....	72
LABCENTER .....	Cover (iv)
LASER BUSINESS SYSTEMS .....	45
MAGENTA ELECTRONICS .....	21
MATRIX MULTIMEDIA .....	51
MICROCHIP .....	47
MILFORD INSTRUMENTS .....	55
PEAK ELECTRONIC DESIGN .....	Cover (iii)
PICO TECHNOLOGY .....	59
QUASAR ELECTRONICS .....	2/3
SHERWOOD ELECTRONICS .....	21
STEWART OF READING .....	Cover (iii)

### ADVERTISEMENT OFFICES:

113 Lynwood Drive, Merley, Wimborne, Dorset BH21 1UU

PHONE: 01202 873872 Fax: 01202 874562

EMAIL: epeads@wimborne.co.uk

For Editorial address and phone numbers see page 7



# New Year VAT Busters

"for a limited time only..."

...we're keeping our prices at pre-VAT-increase levels"

# PEAK

electronic design ltd

## The New Atlas ESR Plus, Model ESR70

**£88.99  
inc VAT**



**NEW MODEL**

This new model of the famous **Atlas ESR** offers all the great features of the ESR60 but with extended measurement range and audible alerts.

**This is the Atlas ESR Plus!**

- Capacitance from 1uF to 22,000uF.
- ESR from 0.01 ohms to 40 ohms.
- Great for ESR and low resistance measurements (short tracing etc).
- Automatic controlled discharge function.
- Audible Alerts (for good ESR, poor ESR, open circuit and more).
- Gold plated croc clips.
- User Guide and Battery included.

## Atlas DCA - Model DCA55

The famous Peak Atlas, now with fitted premium probes. Just connect any way round to identify the type of semiconductor, pinout and lots of parameters too. Complete with battery, user guide and probes.

**£55 inc VAT**



Darlington's  
MOSFETs  
Diodes  
Transistors  
LEDs  
and more...

Look! New Probes.

## Atlas Star Pack (LCR/DCA)

**Extra VAT Busting Saver!!  
This pack saves you £25**

Includes the Atlas LCR Passive Component Analyser (model LCR40), Atlas DCA Semiconductor Analyser (model DCA55), premium padded carry case and user guides.

Complete with extra spare battery. You're ready to go!

**£125 inc VAT**



## Atlas SCR - Model SCR100

Connect Triacs or Thyristors any way round. Auto part identification and pinout display. Categorises gate from 100uA to 100mA. Load conditions regulated at 12V, 100mA, even for a dying battery. Measures gate voltage drop. Long life alkaline battery supplied. Supplied with premium probes.



**Reduced Price!  
was £97**

**£79 inc VAT**

## Atlas LCR - Model LCR40

Passive component analyser. Automatically identify and measure inductors, capacitors and resistors. Auto frequency selection. Removable probes.



**£79 inc VAT**

## Atlas ESR - Model ESR60

**Special Offer!**

Measure capacitance and ESR! Capacitance from 1uF to 22,000uF ESR from 0.01 ohms to 20 ohms Battery included + Gold plated croc clips



**£75 inc VAT**

**was £87**

Peak Electronic Design Ltd, West Road House, West Road, Buxton, Derbyshire, SK17 6HF.

tel. 01298 70012 www.peakelec.co.uk sales@peakelec.co.uk Please add £2.75 p&p per order. Prices include UK VAT. See website for overseas prices.

Special Offer prices for limited period or while stocks last.

# www.stewart-of-reading.co.uk

CHECK OUT OUR WEBSITE, 1,000's of items currently in stock



**HP53131A UNIVERSAL COUNTER WITH OPT 001 (oven)**  
Unused Boxed 3GHZ **£850**  
Unused Boxed 225MHZ **£595**  
Used 225MHZ **£495**



**HP33120A FUNCTION GENERATOR**  
100 MicroHZ - 15MHZ  
Unused Boxed **£595**



**ANRITSU MS2601A SPECTRUM ANALYSER**  
10KHZ - 2.2 GHZ 50ohm **£750**

AGILENT E4402B Spectrum Analyser 100HZ - 3GHZ with Option 1DN Tracking Gen; 1 DR Narrow Res; A4H GPIB, UKB **£5800**  
HP 8591E Spectrum Analyser 9KHZ - 1.8GHZ with Tracking Gen No Mouldings, No Handle **£1500**  
HP 35670A FFT Dynamic Signal Analyser 2 Channel. Unused in original box **£1250**  
AGILENT 83752B Synthesised Sweeper 0.01-20GHZ **£2500**  
HP83731B Synthesised 1-20GHZ with Opt IEI Attenuator, IE5 High Performance Mod Gen, IE5 High Stab TB **£7000**  
HP83711B Synthesised 1-20GHZ with Opt IEI Attenuator **£4500**  
AGILENT/HP E4431B Signal Generator 250KHZ-2GHZ Digital Modulation **£5000**  
MARCONI 2024 Signal Generator 9KHZ-2.4GHZ Opt 04 **£2750**  
MARCONI/IFR 2030 Signal Generator 10KHZ-1.35 GHZ **£1250**  
MARCONI 2032 Signal Generator 10KHZ-5.4GHZ **£995**  
MARCONI 2022E Synthesised AM/FM Signal Generator 10KHZ-1.01GHZ **£-**  
HP3580A Spectrum Analyser 5HZ-50KHZ **£500**  
Unused **£500**  
HP8566A Spectrum Analyser 100HZ-22GHZ **£1950**

HP8568A Spectrum Analyser 100HZ-1500MHZ **£1250**  
AVCOM PSA-37D Spectrum Analyser 1MHZ-4.2GHZ **£-**  
IFR 1200S Service Communication Monitor **£2000**  
HP6624A Power Supply 0-20V 0-2A Twice, 0-7V 0-5A; 0-50V 0.8A Special price **£350**  
AVO/MEGGER FT6/12 AC/DC breakdown tester **£-**

MARCONI/IFR/AEROFLEX 2025 Signal Gen 9KHZ-2.51GHZ Opt 04 High Stab Opt 11 High Power etc As New **£2500**  
SOLARTRON 1250 Frequency Response Analyser 10uHZ-20MHZ **£-**  
HP3324A Synthesised Function Generator 21MHZ **£500**  
TEKTRONIX AM503B with A6302 Probe and TM502A **£750**  
HP41800A Active Probe 5HZ-500MHZ **£750**

## EXTRA SPECIAL OFFER



## MARCONI 2945 RADIO COMMUNICATIONS TEST SET with....

**Opt 01** - 600 ohm Matching Unit - **Opt 03** - High Stability OCXO -  
**Opt 06** - Memory Card Drive with Real Time Clock - **Opt 08** - SSB Demodulator -  
**Opt 21** Demodulation Filters - **Opt 22** POCSAG Decode  
Complete with Carrying Bag **Only £2,500**

## STEWART of READING

17A King Street, Mortimer,  
Near Reading RG7 3RS  
T: (0118) 933 1111 • F: (0118) 933 2375  
9am - 5pm Monday - Friday

## Used Equipment - GUARANTEED

Most Manuals Supplied

Prices plus carriage and VAT

Please check availability before ordering or **CALLING IN.**



## GO FASTER WITH PROTEUS PCB DESIGN

The latest version of the Proteus Design Suite harnesses the power of your computer's graphics card to provide lightning fast performance. Together with unique transparency options it's now easier than ever to navigate and understand large, multi-layer boards.

### PROTEUS DESIGN SUITE Features:

- Hardware Accelerated Performance.
- Unique Thru-View™ Board Transparency.
- Over 35k Schematic & PCB library parts.
- Integrated Shape Based Auto-router.
- Flexible Design Rule Management.
- Polygonal and Split Power Plane Support.
- Board Autoplacement & Gateswap Optimiser.
- Direct CAD/CAM, ODB++ & PDF Output.
- Integrated 3D Viewer with 3DS and DXF export.
- Mixed Mode SPICE Simulation Engine.
- Co-Simulation of PIC, AVR, 8051 and ARM7.
- Direct Technical Support at no additional cost.

All levels of the **Proteus Design Suite** include a world class, fully integrated shape-based autorouter at no additional cost - prices start from just £150 exc. VAT & delivery

**labcenter**  [www.labcenter.com](http://www.labcenter.com)  
**Electronics**

Labcenter Electronics Ltd. 53-55 Main Street, Grassington, North Yorks. BD23 5AA.  
Registered in England 4692454 Tel: +44 (0)1756 753440, Email: [info@labcenter.com](mailto:info@labcenter.com)

Visit our website or  
phone 01756 753440  
for more details